

Name Sadye Gözler Number _____


Honor pledge signature Sadye

Attention :

- There are 19 Multiple choice questions plus one output wave form sketch (20 Total)
- 2 of the questions require extra (indicated by "~") drawing / sketching
- Marking the correct answer does not guarantee full credit. You need to show how you came up with that answer properly.
- Show all your calculations in a neat and clear style in order to get full credit.

BEST OF LUCK

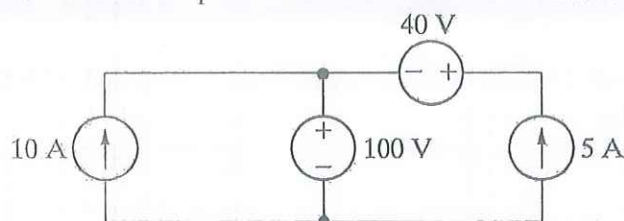1. For the Figure below calculate the power associated with the 5A source







- a) $P = -300 \text{ W}$
 b) $P = 300 \text{ W}$
 c) $P = -700 \text{ W}$
 d) $P = 700 \text{ W}$
 e) Can't be done. Connections are invalid.


2. The maximum current that a 2W , $80 \text{ k}\Omega$ resistor can safely conduct is :

- a) 160 kA b) 40 kA c) 5 mA d) $25 \mu\text{A}$ e) 25 mA

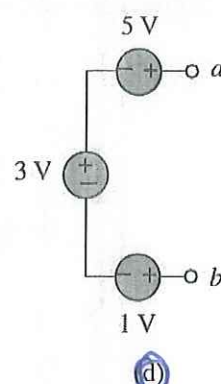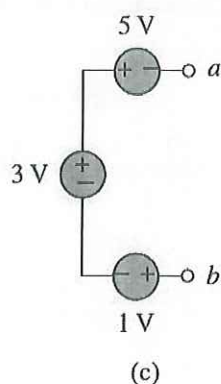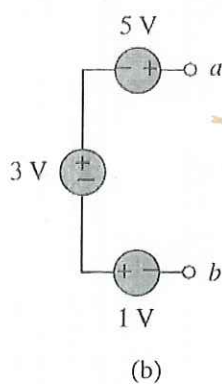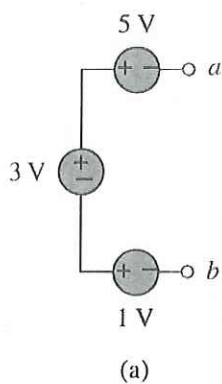3. Which of the following circuits given below would output $V_{ab} = 7\text{V}$?




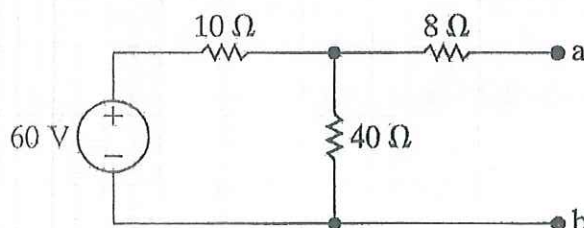4. The Norton current with respect to the terminals for the circuit given below is 3 A . What is the short circuit current ?




- a) $I_{SC} = 3\text{mA}$ b) $I_{SC} = 5\text{mA}$ c) $I_{SC} = 5\text{A}$ d) $I_{SC} = 6\text{A}$ e) None of these

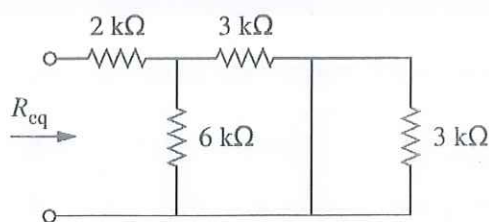5. The equivalent resistance for the circuit given below is :




- a) 4 kΩ b) 5 kΩ c) 8 kΩ d) 14 kΩ e) None of these

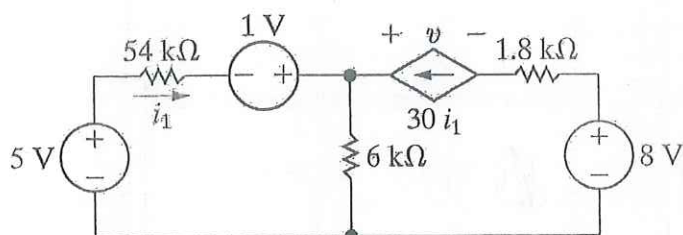6. The voltage drop, v , across the dependent current source for the circuit below is :



- a) 15.4 V b) 2 V c) -15.4 V d) 6 V e) Current sources do not have a voltage drop

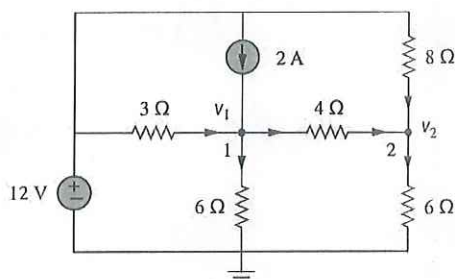7. For the circuit given below the KCL for node 1 is given as



(a) $2 + \frac{12 - v_1}{3} = \frac{v_1}{6} + \frac{v_1 - v_2}{4}$

(b) $2 + \frac{v_1 - 12}{3} = \frac{v_1}{6} + \frac{v_2 - v_1}{4}$

(c) $2 + \frac{12 - v_1}{3} = \frac{0 - v_1}{6} + \frac{v_1 - v_2}{4}$

(d) $2 + \frac{v_1 - 12}{3} = \frac{0 - v_1}{6} + \frac{v_2 - v_1}{4}$

8. For the circuit of problem 7 the KCL for node 2 is given as


(a) $\frac{v_2 - v_1}{4} + \frac{v_2}{8} = \frac{v_2}{6}$

(b) $\frac{v_1 - v_2}{4} + \frac{v_2}{8} = \frac{v_2}{6}$

(c) $\frac{v_1 - v_2}{4} + \frac{12 - v_2}{8} = \frac{v_2}{6}$

(d) $\frac{v_2 - v_1}{4} + \frac{v_2 - 12}{8} = \frac{v_2}{6}$

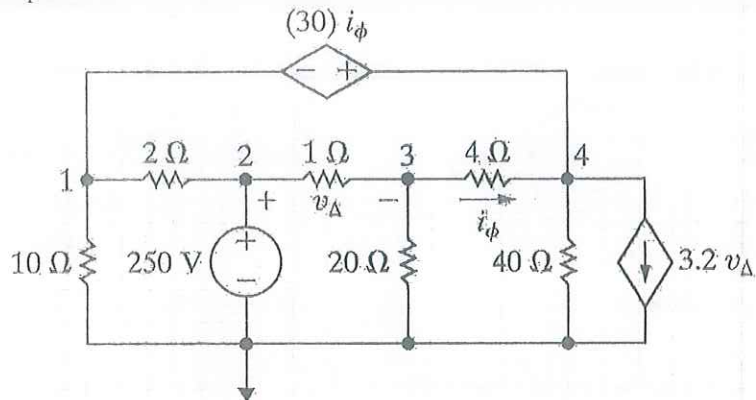
9. For the circuit given below, the essential nodes and reference node are marked. Indicate the valid nodal equation for the Supernode



- a) $\frac{V_1}{10} + \frac{V_1 - V_2}{2} - 30i_\phi = 0$
- b) $\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{1} + \frac{V_3}{20} + \frac{V_3 - V_4}{4} = 0$
- c) $24V_1 - 138V_3 + 11V_4 = -27000$
- d) $10V_1 - 20V_3 - 40V_4 = 250$
- e) There is no Supernode in the given circuit


10. For the circuit given below, determine the steady state value of V_o , with respect to ground for the given component values

$V_1 = 10V$	$V_2 = 20V$	$I_1 = 5A$	
$R_1 = 70\Omega$	$R_2 = 100\Omega$	$R_3 = 30\Omega$	$R_4 = 150\Omega$
$L_1 = 7H$	$L_2 = 0.5H$	$L_3 = 1H$	
$C_1 = 1\mu F$	$C_2 = 12\mu F$		

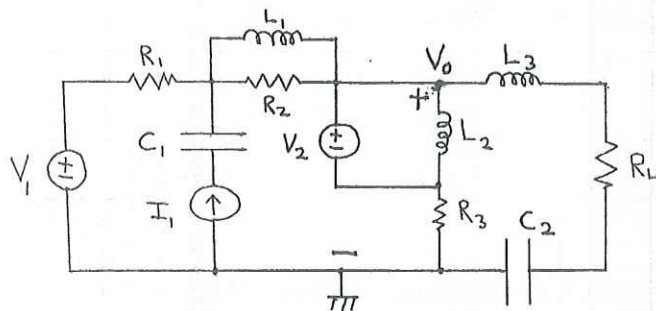

- a) Indeterminate
- b) 3 V
- c) 10 V
- d) 5 V
- e) None of the above

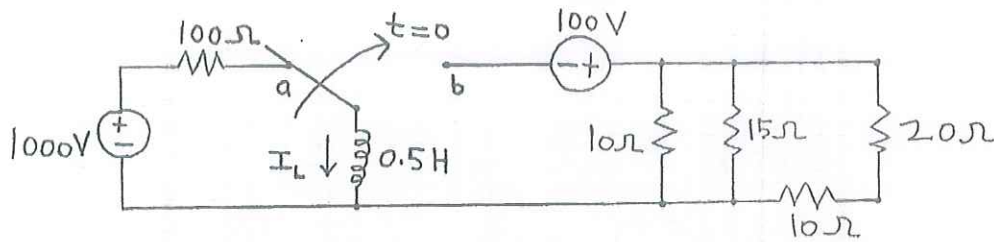11. For the circuit given below determine the time constant of the transient response for $t \geq 0$




- a) $\tau = 100ms$ b) $\tau = 50ms$ c) $\tau = 10s$ d) $\tau = 2.5s$ e) None of these

12. For the circuit given in Problem 11, the expression for $I_L(t)$ for $t \geq 0$ can be written as:

- a) $I_L(t) = 20A$
 b) $I_L(t) = 20 - 10e^{-\frac{t}{\tau}} A$
 c) $I_L(t) = -20 + 30e^{-\frac{t}{\tau}} A$
 d) $I_L(t) = 10e^{-\frac{t}{\tau}} A$
 e) None of the above

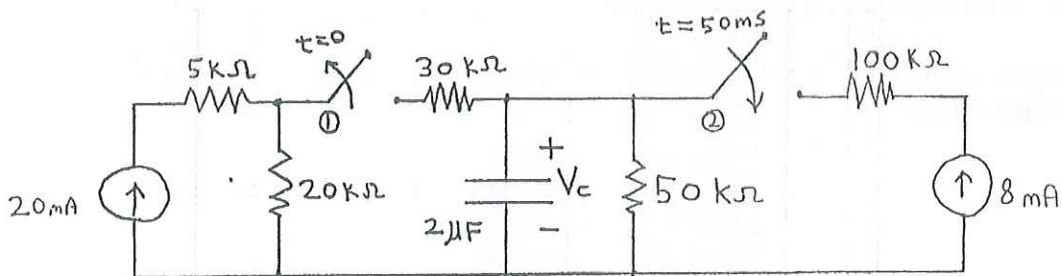13. In the circuit given below **switch 1** has been closed and **switch 2** have been open since my 16th birthday. During this exam (specifically right now), let's say at 13., **switch 1** is opened. Then at 50 ms **switch 2** is closed




Determine $V_C(t)$ valid for $0 \leq t \leq 50 ms$

- a) $V_C(t) = 200e^{-10t} V$
 b) $V_C(t) = 200e^{-6.25t} V$
 c) $V_C(t) = 400e^{-6.25t} V$
 d) $V_C(t) = 400e^{-10t} V$
 e) None of the above

14. For the circuit of Problem 13, determine the $V_C(t)$ for $t \geq 50 ms$


- a) $V_C(t) = V_C(0.005)e^{-15t} V$
 b) $V_C(t) = 400[1 - e^{-15t}] V$
 c) $V_C(t) = 121 V$
 d) $V_C(t) = V_C(0.05)e^{-10t+0.5} + 400[1 - e^{-10t+0.5}] V$
 e) None of the above

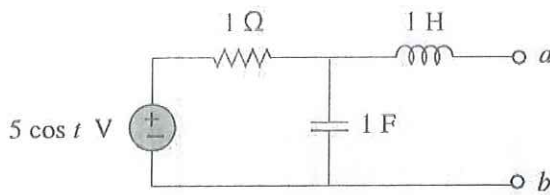15. Draw the Thevenin equivalent circuit and find the Thevenin impedance at terminals a-b for the circuit given below




- (a) 1Ω (b) $0.5 - j0.5 \Omega$
 (c) $0.5 + j0.5 \Omega$ (d) $1 + j2 \Omega$
 (e) $1 - j2 \Omega$

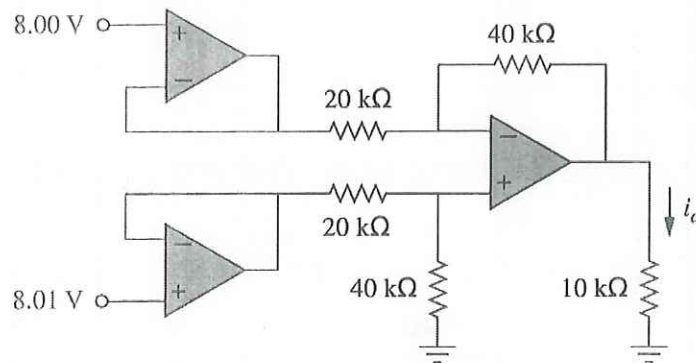16. For the instrumentation amplifier circuit given below calculate the value of the output current i_o



- a) 1.066 mA
 b) -1.066 mA
 c) 0.133 μ A
 (d) 2 μ A
 e) none of the above

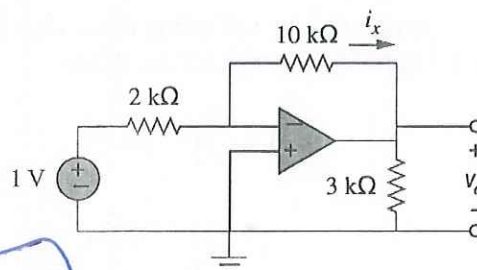17. For the op-amp circuit given below calculate the output voltage, v_o and the value of i_x




- a) -6 V, 0.6 A (b) -5 V, 0.5 A (c) -6 V, 0.5 A (d) -5 V, 0.6 A (e) None of these

E
 (B if 0.5mA given)

(b) -5 V, 0.5 A
 0.5mA

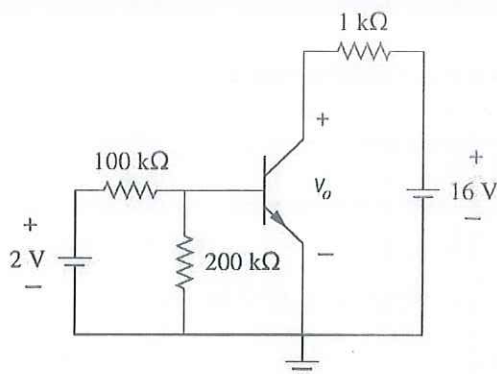
18. For the BJT circuit given below $\beta = 150$ and $V_{BE} = 0.7V$



Find the value of v_o

- a) not enough information
- b) -12 V
- c) 14.575 V
- d) 12.65 V
- e) 15.805 V

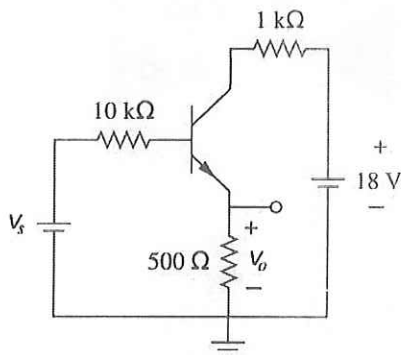19. Calculate the value of v_s for the transistor circuit given below when $v_o = 4V$, $\beta = 150$, $V_{BE} = 0.7V$



- a) 4.23 V
- b) 5.23 V
- c) 4.7 V
- d) 9.23 V
- e) not enough information

20. Sketch the output signal when the input to the following diode circuit is a sinusoidal wave with amplitude of 15 V (assume 0.6 V forward biasing voltage for diodes)

