
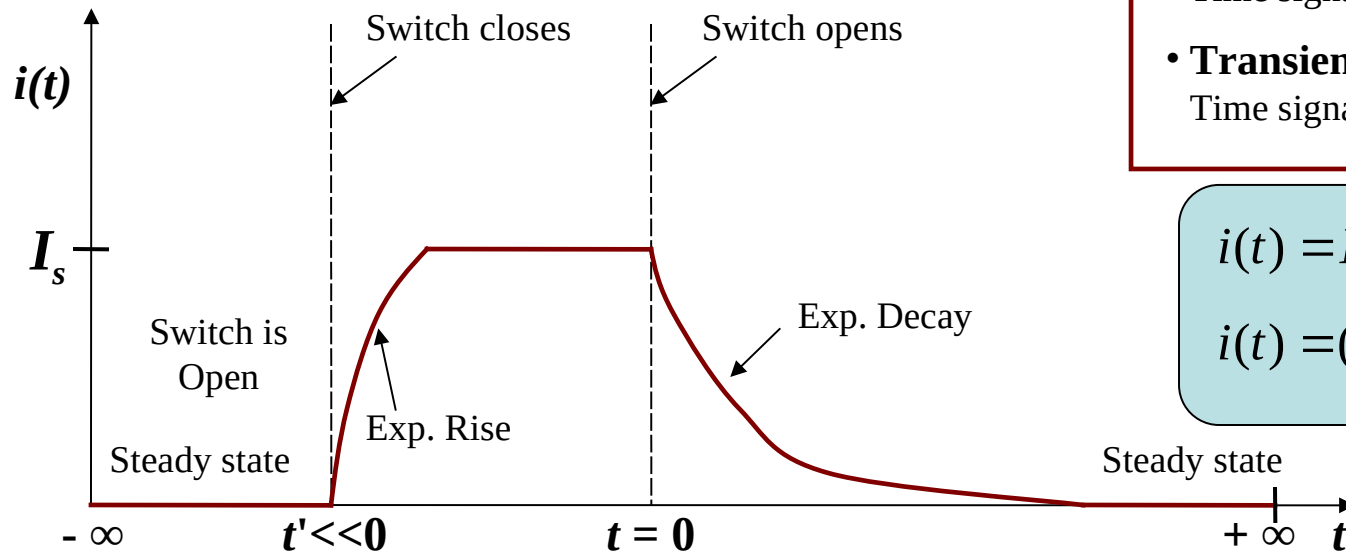


Chapter 5

1st – Order RL and RC Circuits

General Response of RL Circuits

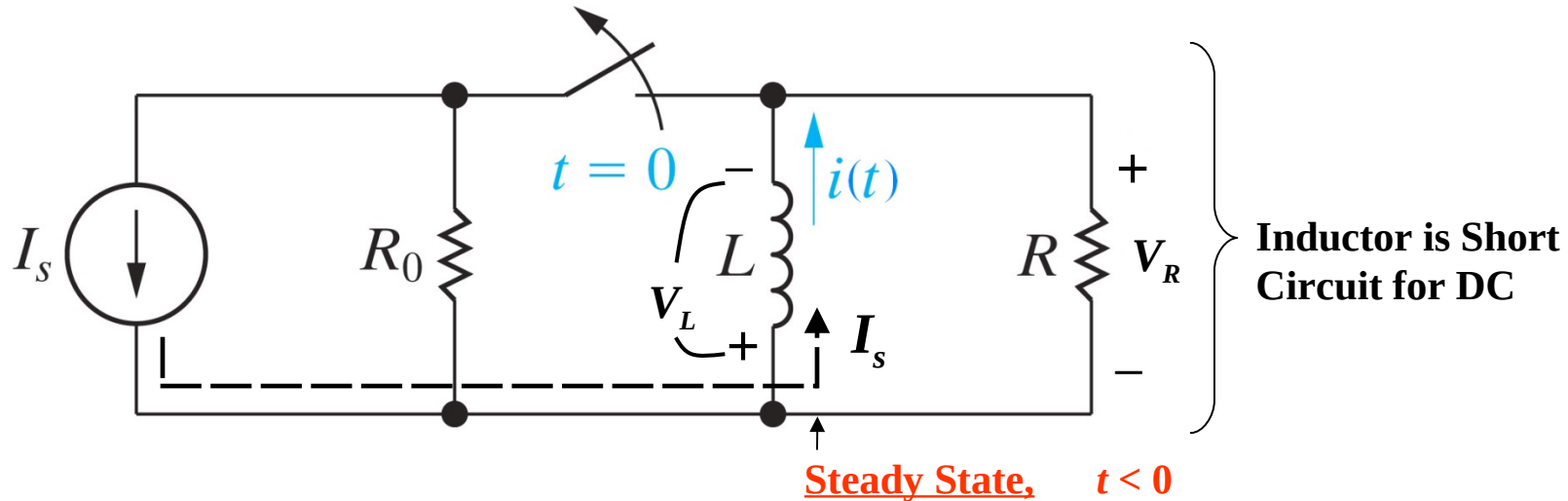

- **Steady State Solution/Response**
Time signals are constant or periodic
- **Transient Solution/Response**
Time signals are not constant or periodic

$$i(t) = I_s e^{-(R/L)t} \quad t \geq 0$$


$$i(t) = (\alpha) \left[1 - e^{-(R/L)[t-t']} \right] \quad t \leq 0$$

RL \equiv Resistor – Inductor Circuit

Natural Response

RC \equiv Resistor – Capacitor Circuit

Natural Response:

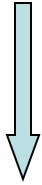

- * Response of RL or RC Circuit when dc source is abruptly disconnected.
- * Energy is released to resistive circuit
- * Recall that Energy is stored in ***L*** and ***C***.

Leaves us with:

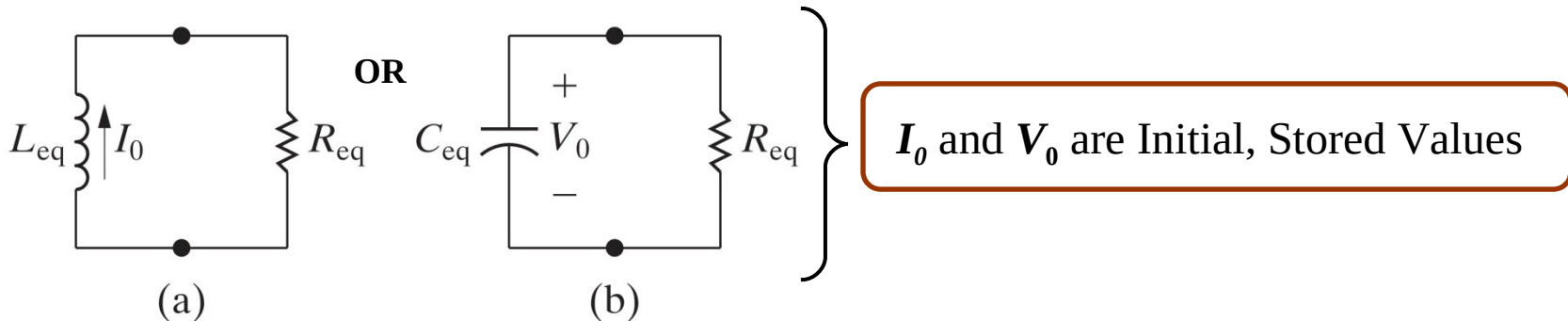


Figure: 07-01


Copyright © 2008 Pearson Prentice Hall, Inc.

1st – Order Circuits

***i* and *v* are described by 1st – Order Linear Differential Equations**

RL Circuit

Natural Response

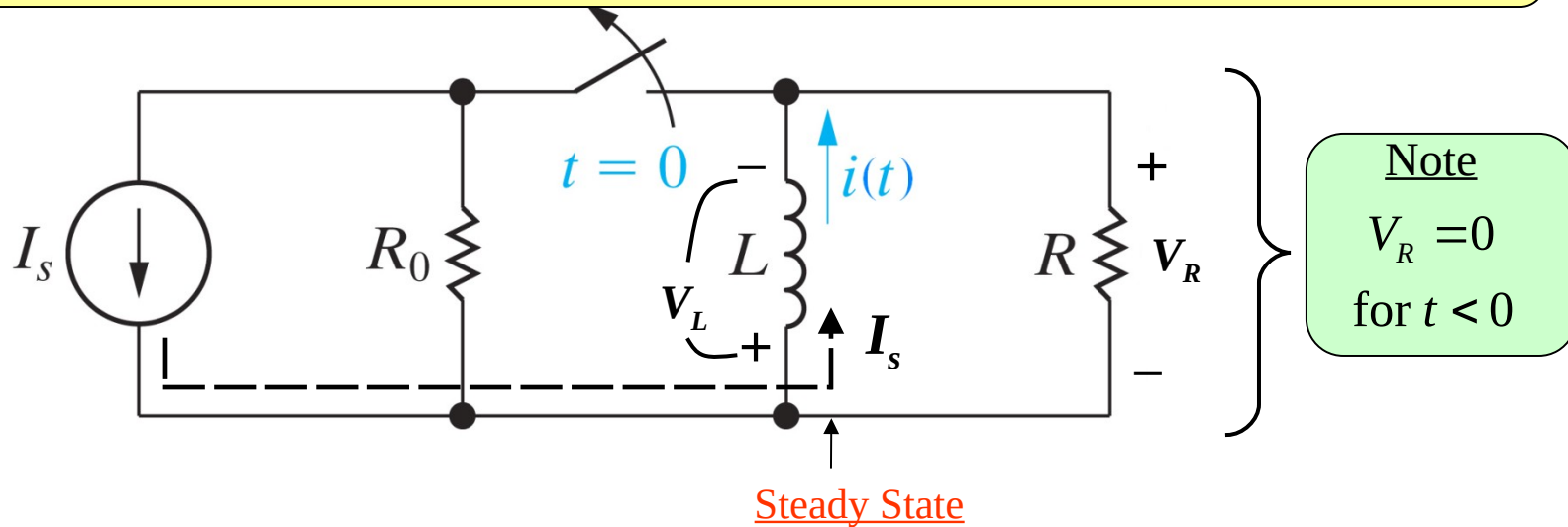

Note
 $V_R = 0$
for $t < 0$

* Assume Steady State long before $t = 0$.

* $v_L = L \frac{di}{dt} = 0$ Short

* Current = 0 in R_0 and R

* $i(0^+) = I_s$ in L


**Steady State
Conditions at t_0**

RL Circuit

Natural Response (Contd.)

At $t \geq 0$ the circuit becomes:

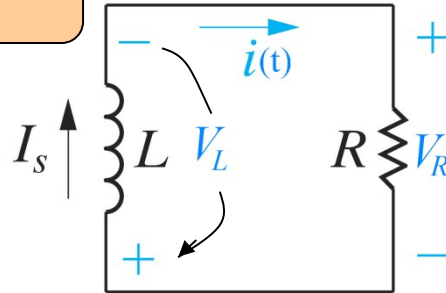At $t \geq 0$, Inductor Begins Releasing Energy



← **Note Polarities**

$$V_L + V_R = 0 \quad \left. \vphantom{V_L + V_R = 0} \right\} \text{KVL}$$

$$L \frac{di}{dt} + Ri = 0$$

$$V_L = L \frac{di}{dt}$$

$$V_R = Ri$$

1st – Order Ordinary Linear Differential Equation With Constant Coefficients

R and L don't vary with i or t $\left. \vphantom{R \text{ and } L \text{ don't vary with } i \text{ or } t} \right\} \text{Constant Coefficients}$

Two Methods: To solve above differential equation

RL Circuit

Natural Response (Contd.)

(1) Textbook's Method

$$\textcircled{1} \quad \frac{di}{dt} = - \left(\frac{R}{L} \right) i \quad \left. \vphantom{\frac{di}{dt}} \right\} \text{Simplify differential equation}$$

$$\textcircled{1} \quad \frac{di}{dt} dt = - \frac{R}{L} i dt \quad \left. \vphantom{\frac{di}{dt}} \right\} \text{Multiply by } dt$$

$$\textcircled{1} \quad \frac{di}{i} = - \frac{R}{L} dt \quad \left. \vphantom{\frac{di}{i}} \right\} \text{Separation of Variables}$$

Integrate: * Lets not be "Picky" about Variables
* \int from 0 (initial) to t (some time)

$$\int_{i(0)}^{i(t)} \frac{di}{i} = - \frac{R}{L} \int_0^t dt \quad \left. \vphantom{\int} \right\} \text{Integrate } \textcircled{1}$$

$$\ln i \Big|_{i(0)}^{i(t)} = - \frac{R}{L} t \Big|_0^t \quad \left. \vphantom{\ln} \right\} \text{Anti-derivative}$$

$$\ln i(t) - \ln i(0) = - \frac{R}{L} t \quad \left. \vphantom{\ln} \right\} \text{Plug in limits}$$

$$\ln \frac{i(t)}{i(0)} = - \frac{R}{L} t \quad \left. \vphantom{\ln} \right\} \text{ln(.) Identity}$$

[raise e to both sides]

$$i(t) = i(0) e^{-\left(\frac{R}{L}\right)t}$$



RL Circuit

Natural Response (Contd.)

Notation

$t = 0^-$ is just **Before** Switching

$t = 0^+$ is just **After** Switching

$$i(0^-) \equiv i(0^+) = I_s = I_0$$

Current can't change instantly

$$\therefore i(t) = I_0 e^{-\left(\frac{R}{L}\right)t} \quad t \geq 0$$

I_0 is initial current

or I_s } Source Current

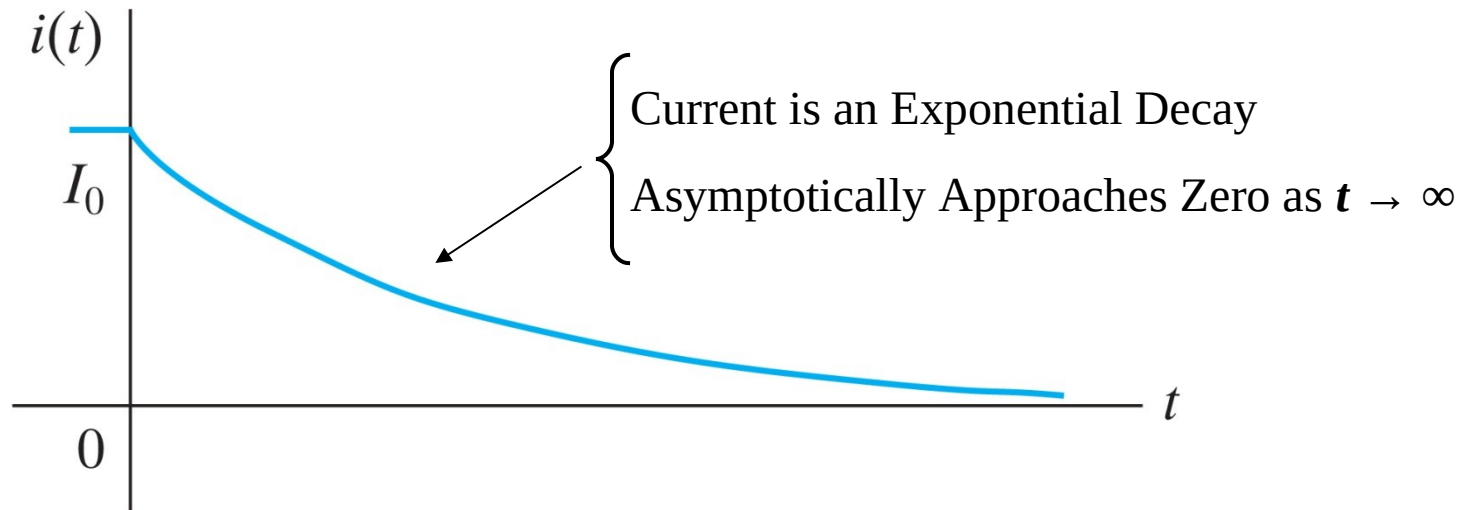


Figure: 07-05

Copyright © 2008 Pearson Prentice Hall, Inc.

(2) Alternative Method: Boundary Values

Start with: $\frac{di}{i} = -\frac{R}{L}dt$

$$\int \frac{di}{i} = - \int \frac{R}{L} dt \quad \left. \vphantom{\int \frac{di}{i} = - \int \frac{R}{L} dt} \right\} \text{Integrate}$$

$$\textcircled{1} \quad \ln i(t) = -\frac{R}{L}t + K \quad \leftarrow \text{Constant of Integration}$$

K Determined by "Initial Condition" or Boundary Value

$i(0) = I_0 \equiv I_s$ in our circuit

$$\ln i(0) = \ln I_0 = -\frac{R}{L}(0) + K \quad \left. \vphantom{\ln i(0) = \ln I_0 = -\frac{R}{L}(0) + K} \right\} \text{Substitute } t = 0$$

$$\textcircled{2} \quad K = \ln I_0$$

$$\ln i(t) = -\frac{R}{L}t + \ln I_0 \quad \left. \vphantom{\ln i(t) = -\frac{R}{L}t + \ln I_0} \right\} \text{Substitute } \textcircled{2} \text{ into } \textcircled{1}$$

$$\ln i(t) - \ln I_0 = \ln \frac{i(t)}{I_0} = -\frac{R}{L}t \quad \left. \vphantom{\ln i(t) - \ln I_0 = \ln \frac{i(t)}{I_0} = -\frac{R}{L}t} \right\} \text{Solve for } i(t)$$


$$\therefore i(t) = I_0 e^{-\left(\frac{R}{L}\right)t} \quad t \geq 0 \quad \left. \vphantom{\therefore i(t) = I_0 e^{-\left(\frac{R}{L}\right)t} \quad t \geq 0} \right\} \text{Raise to the exponential}$$

Check Solution:

1. Plug solution into diff. eqn., and see if it works
2. Is $i(t = 0) \equiv I_0$?

RL Circuit

Natural Response (Contd.)

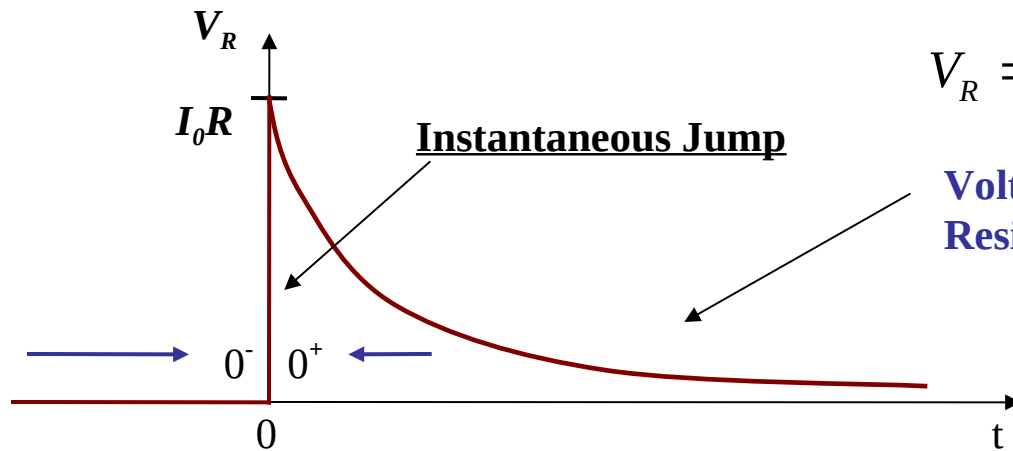

$$V_R = I_0 R e^{-\left(\frac{R}{L}\right)t}$$

Voltage across resistor (Ohm's Law)

Voltage across Resistor

$V_R(0^-) = 0$
In original circuit resistor is shorted out for $t < 0$

$$p = i^2 R = I_0^2 R e^{-2\left(\frac{R}{L}\right)t}$$

Power dissipated in Resistor

$$w(t) = \int p dt = I_0^2 R \int e^{-2\left(\frac{R}{L}\right)t} dt$$

Integrate Power to obtain Energy

$$w(t) = \frac{1}{2} L I_0^2 \left(1 - e^{-2\left(\frac{R}{L}\right)t} \right)$$

Energy Delivered to the Resistor

Conservation of Energy

All Inductor Energy Transferred to the Resistor

$$w(t \rightarrow \infty) = \frac{1}{2} L I_0^2 \equiv \text{Initial Stored Energy in Inductor}$$

RL Circuit

Time Constant Definition

Solution has the form

$$i(t) = I_0 e^{-(R/L)t}$$

for $t \geq 0$

$$e^{-(R/L)t} \equiv e^{-t/\tau} \left. \vphantom{e^{-(R/L)t}} \right\} \tau = \frac{L}{R} \quad \text{Time Constant}$$

$\tau \equiv$ Rate at which function approaches zero

$$\therefore i(t) = I_0 e^{-t/\tau} \left. \vphantom{i(t)} \right\} \tau = \frac{L}{R}$$

Think of Time Elapsed in Integral Multiples of τ

$$\therefore t = \tau \equiv 1 \text{ Time Constant} \Rightarrow e^{-\tau/\tau} = e^{-1} \equiv 0.37$$

$$i(t = \tau) = 0.37 I_0 \quad \text{after 1 Time Constant.}$$

$$t = 2\tau \equiv 2 \text{ Time Constants} \Rightarrow e^{-2\tau/\tau} = e^{-2} \equiv 0.14$$

$$i(t = 2\tau) = 0.14 I_0 \quad \text{after 2 Time Constants.}$$

$$t = 5\tau \equiv 5 \text{ Time Constants} \Rightarrow e^{-5\tau/\tau} = e^{-5} \equiv 0.0067$$

$$i(t = 5\tau) = 0.0067 I_0 \quad \text{after 5 Time Constants.}$$

**Current reduced to < 1%
of original value after 5
time constants**

Numeric Example for Time Constant

$$\left. \begin{array}{l} L = 100 \text{ mH} \\ R = 1000 \, \Omega \end{array} \right\} \text{Example Values}$$

$$\tau = \frac{L}{R} = \frac{0.1}{1000} = 0.1 \text{ (ms)}$$

$$i(t) = I_0 e^{-t/\tau} \text{ where } 5\tau = 0.5 \text{ (ms)}$$

After 0.5 (ms)
 $i(t) \cong 0$

Rule of Thumb for Time Constants

VALUES OF $e^{-t/\tau}$ FOR t EQUAL TO INTEGRAL MULTIPLES OF τ

t	$e^{-t/\tau}$	t	$e^{-t/\tau}$
τ	3.6788×10^{-1}	6τ	2.4788×10^{-3}
2τ	1.3534×10^{-1}	7τ	9.1188×10^{-4}
3τ	4.9787×10^{-2}	8τ	3.3546×10^{-4}
4τ	1.8316×10^{-2}	9τ	1.2341×10^{-4}
5τ	6.7379×10^{-3}	10τ	4.5400×10^{-5}

\approx decayed to zero.


Rule of Thumb

RC Circuit

Natural Response

Dual of RL Circuit

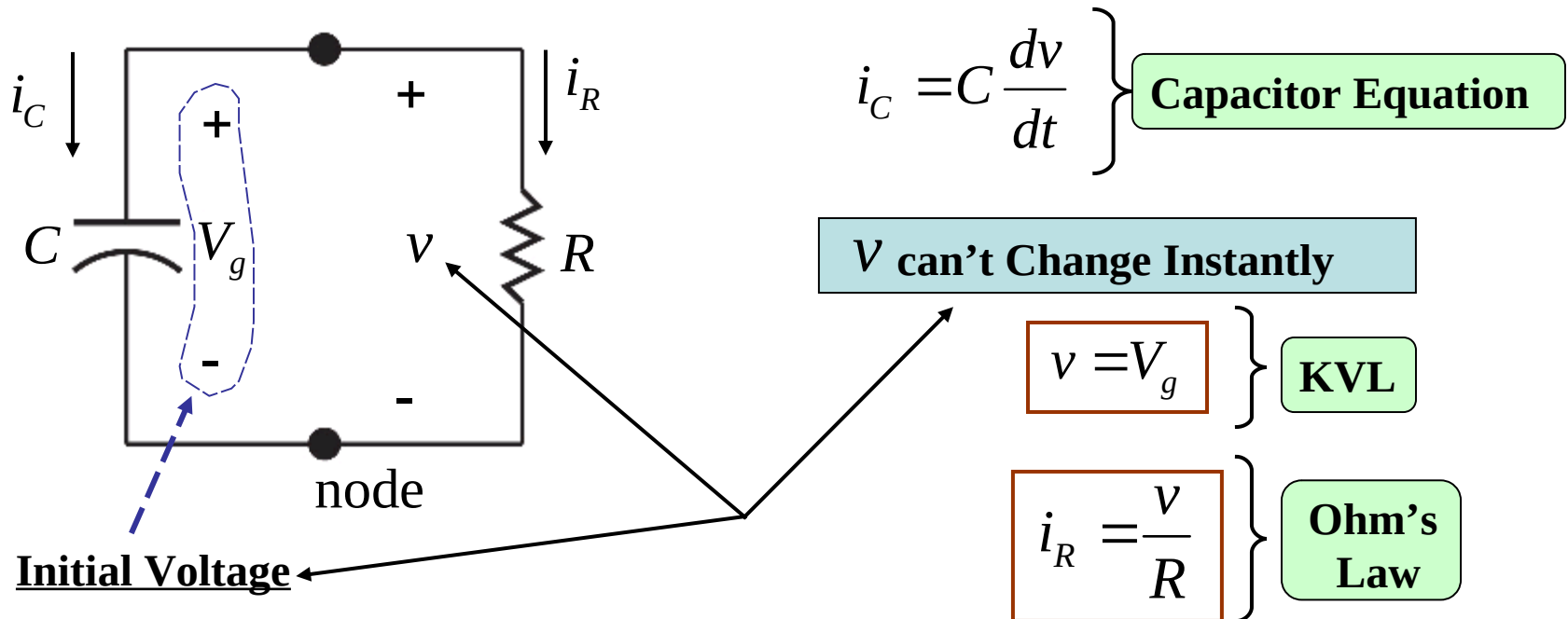- A Capacitor is charged to a Steady-State Voltage V_g at $t = 0$
- Find the time varying expression for $v(t)$ for $t \geq 0$




RC Circuit

Natural Response (Contd.)

Find differential equation for a RC Circuit

Current must be the same in this loop
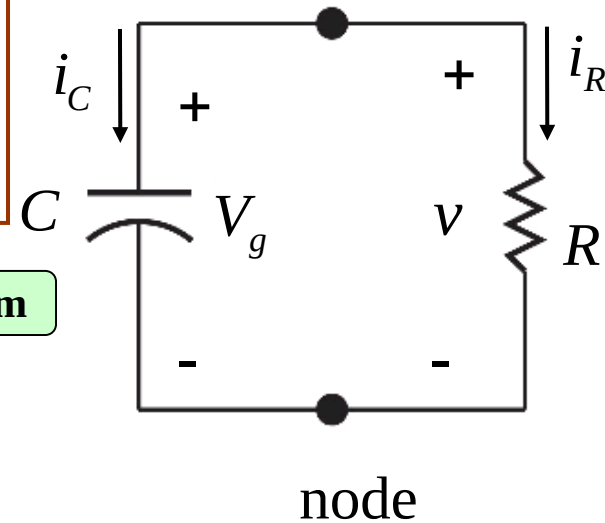
$$i_C = C \frac{dv}{dt}$$
$$i_R = \frac{v}{R}$$



KCL at Node: $i_C + i_R = 0$ } **From the Circuit Diagram**

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$
 } **Substitute for i_C and i_R**

$$\frac{dv}{dt} = \left(-\frac{1}{RC} \right) v$$
 } **Differential Equation**


$$\therefore v(t) = v(0)e^{-t/RC}$$
 } **Solution of differential equation**

Initial Condition : $v(0^-) = v(0) = v(0^+) = V_g = V_0$

(Contd.) \Rightarrow

RC Circuit

Natural Response (Contd.)

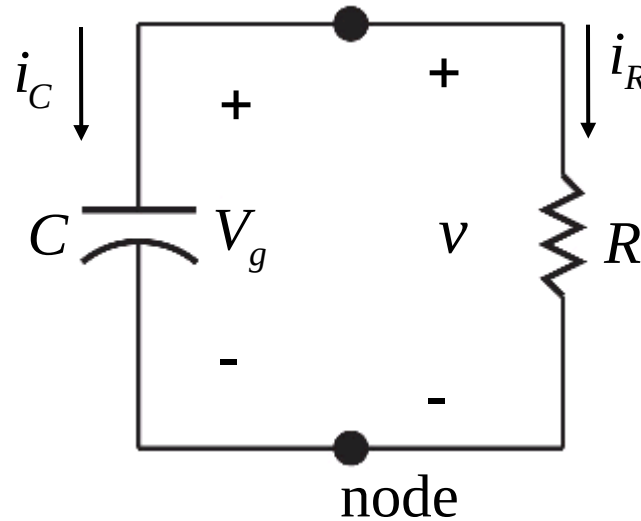

$$v(t) = V_0 e^{-t/\tau} \quad t \geq 0 \quad \left. \vphantom{v(t)} \right\} \text{Solution with } \tau = RC$$

$$i_R(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-t/\tau} \quad t \geq 0 \quad \left. \vphantom{i_R(t)} \right\} \text{Current in Resistor}$$

$$p(t) = v(t)i_R(t) = \frac{V_0^2}{R} e^{-2t/\tau} \quad t \geq 0 \quad \left. \vphantom{p(t)} \right\} \text{Power Dissipated in Resistor}$$

(Contd.) \Rightarrow

RC Circuit

Natural Response (Contd.)

$$w = \int_0^t p(t) dt = \frac{V_0^2}{R} \int_0^t e^{-2t/\tau} dt = \frac{V_0^2}{R} \left[-\frac{\tau}{2} \right] e^{-2t/\tau} \Bigg|_0^t \quad \left. \vphantom{\int_0^t} \right\} \begin{array}{l} \text{Integrate} \\ p = \frac{V_0^2}{R} e^{-2t/\tau} \\ \text{to obtain energy} \end{array}$$

$$= \frac{V_0^2}{R} \left[-\frac{RC}{2} \right] \left[e^{-2t/\tau} - 1 \right] \quad \left. \vphantom{\int_0^t} \right\} \text{Plug in the limits}$$

$$w = \frac{1}{2} C V_0^2 \left[1 - e^{-2t/\tau} \right] \quad \left. \vphantom{\int_0^t} \right\} \text{Energy Delivered to Resistor}$$


Similar to the Case of the RL Circuit

$$w(t=0) = \frac{1}{2} C V_0^2 (1 - 1) = 0 \quad \left. \vphantom{\int_0^t} \right\} \text{Initial Energy delivered to Resistor}$$


$$w(t=\infty) = \frac{1}{2} C V_0^2 (1 - 0) = \frac{1}{2} C V_0^2 \quad \left. \vphantom{\int_0^t} \right\} \text{Final Energy delivered to Resistor}$$

$$\equiv \text{Initial Energy Stored in Capacitor}$$

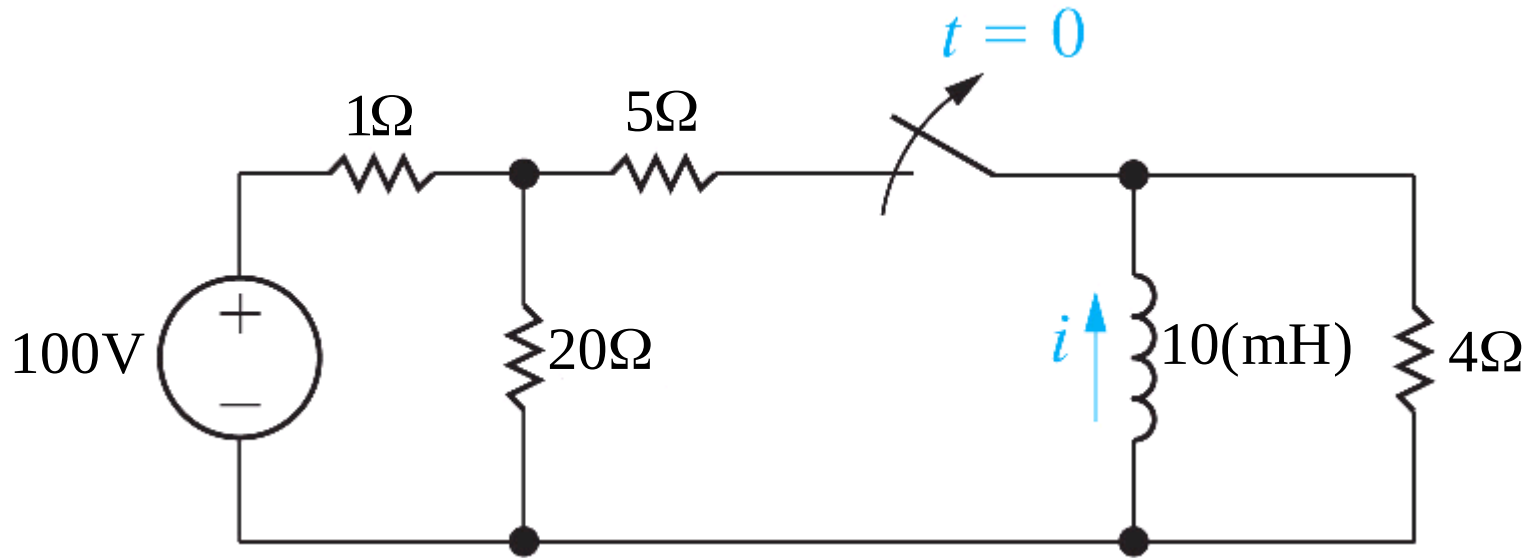Drill Exercise: Find $i(t)$ for $t \geq 0$



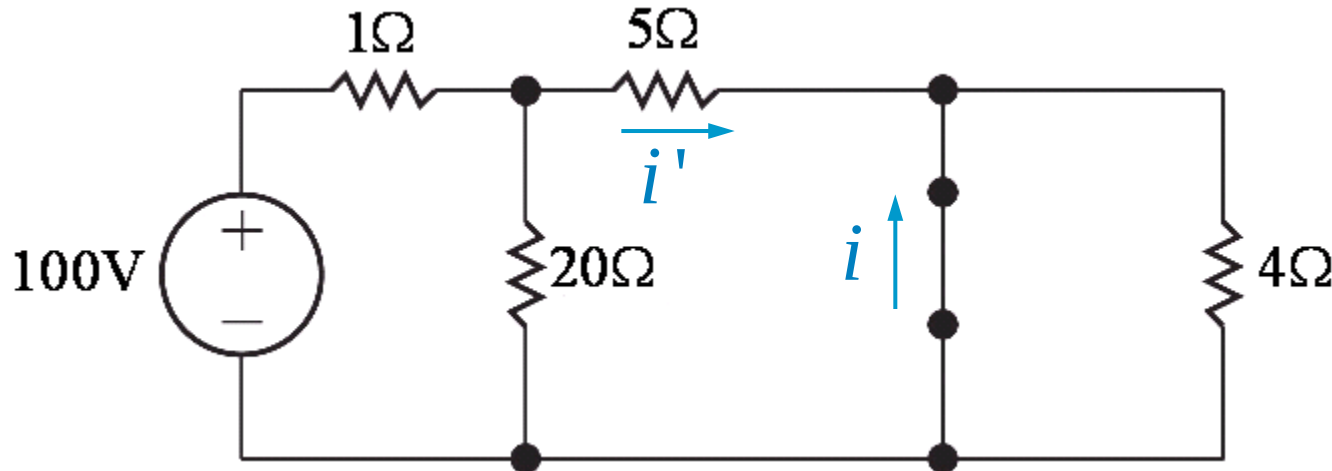a) Steady State Circuit, $t < 0$: Find $i(0^-)$




Inductor Shorted

$$i' = -i$$

No Current in 4Ω Resistor

Drill Exercise:

Find $i(0^-)$

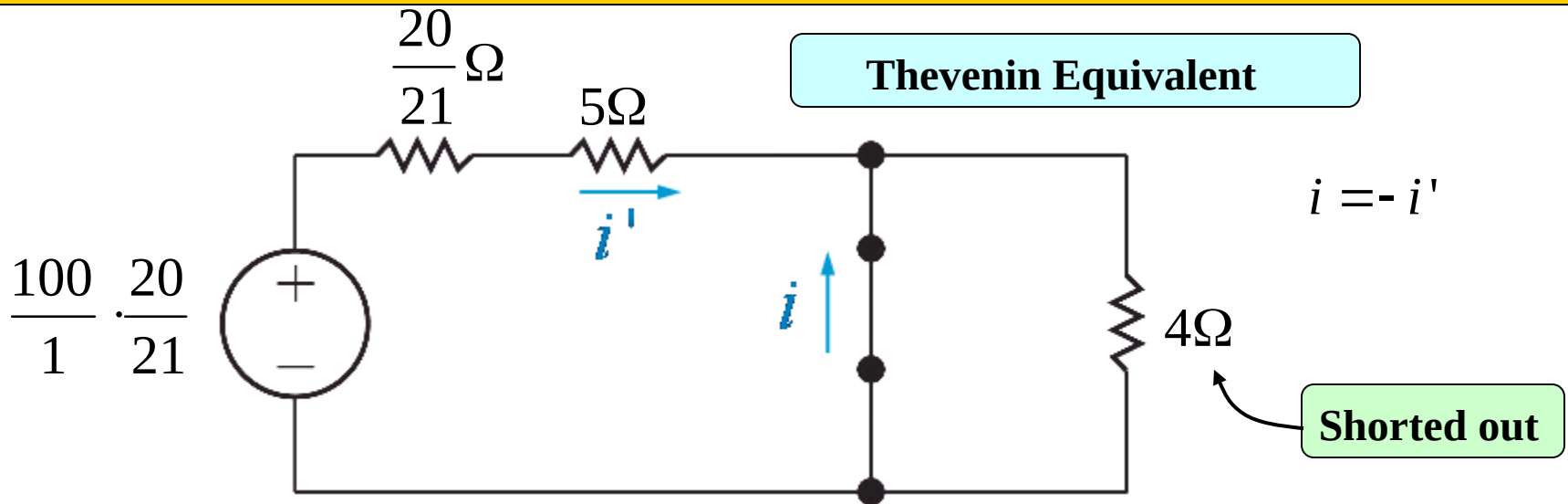

$$i' = \frac{100(20)}{21} \bigg/ \left[\frac{20}{21} + 5 \right] = 16 \text{ (A)} \quad \left. \vphantom{\frac{100(20)}{21}} \right\} \text{Ohm's Law}$$

$$\therefore i = -16 \text{ (A)} \rightarrow i(0^-) = -16 \text{ (A)} \equiv I_0 \quad \left. \vphantom{i(0^-)} \right\} \text{Initial Current in Inductor}$$

b) $w(0^-) = \frac{1}{2} Li^2(0^-) = \frac{1}{2} (0.01)(-16)^2$


$w(0^-) = 1.28 \text{ (J)}$

$\left. \vphantom{\frac{1}{2} Li^2(0^-)} \right\} \text{Initial Energy stored in Inductor}$

Drill Exercise:

Find $i(t)$ for $t \geq 0$

c) Circuit for $t \geq 0$:

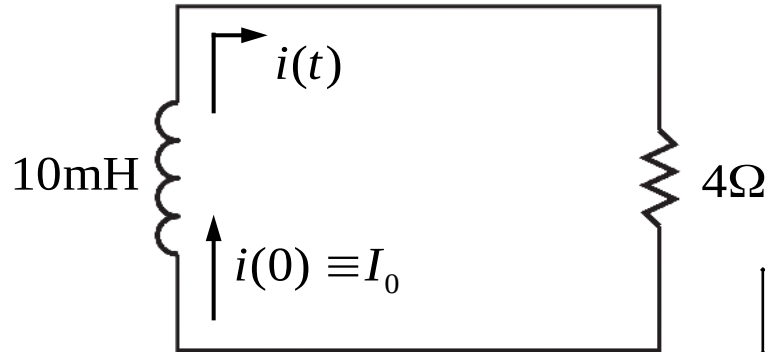

$$\tau = \frac{L}{R} = \frac{0.01}{4}$$

$$\tau = 2.5(ms)$$

$$i(0^-) = i(0) = I_0 = -16(A)$$

Inductor current
can't change
instantly

d) $i(t) = I_0 e^{-t/\tau}$ } **Solution in General**

$$i(t) = -16e^{-t/2.5 \times 10^{-3}} = -16e^{-400t} (A)$$

Plug in value for τ

e) $i(t = 5(ms)) = -16e^{-5/2.5} = -16e^{-2} = -2.17(A)$

$$\tau = 2.5(ms)$$

After 2 Time Constants

$$2 \times 2.5(ms) = 5(ms)$$

$$w(t = 5(ms)) = \frac{1}{2} Li^2(5(ms)) = \frac{1}{2} (0.01)(-2.17)^2$$

Drill Exercise

(Contd.)

$$w(t = 5\text{ms}) = 23.44\text{mJ} \quad \left. \vphantom{w(t = 5\text{ms})} \right\} \text{Energy in the inductor after 2 Time Constants}$$

$$w_{diss} = w(0^-) - w(t = 5\text{ms}) \quad \left. \vphantom{w_{diss}} \right\} \text{Energy dissipated in the inductor after 5 ms}$$


$$= 1.28 - 23.44 \times 10^{-3} \quad \left. \vphantom{= 1.28 - 23.44 \times 10^{-3}} \right\} \text{Plug in numbers}$$

$$w_{diss} = 1.2566\text{J} \quad \left. \vphantom{w_{diss}} \right\} \text{Energy dissipated in the inductor after 5 ms}$$

$$\% \text{ dissipated} = \left(\frac{1.2566}{1.28} \right) \times 100 = 98.17\% \quad \left. \vphantom{\% \text{ dissipated}} \right\} \text{After 2 Time Constants}$$


The effects of $\frac{1}{2}Li^2$ are clearly shown

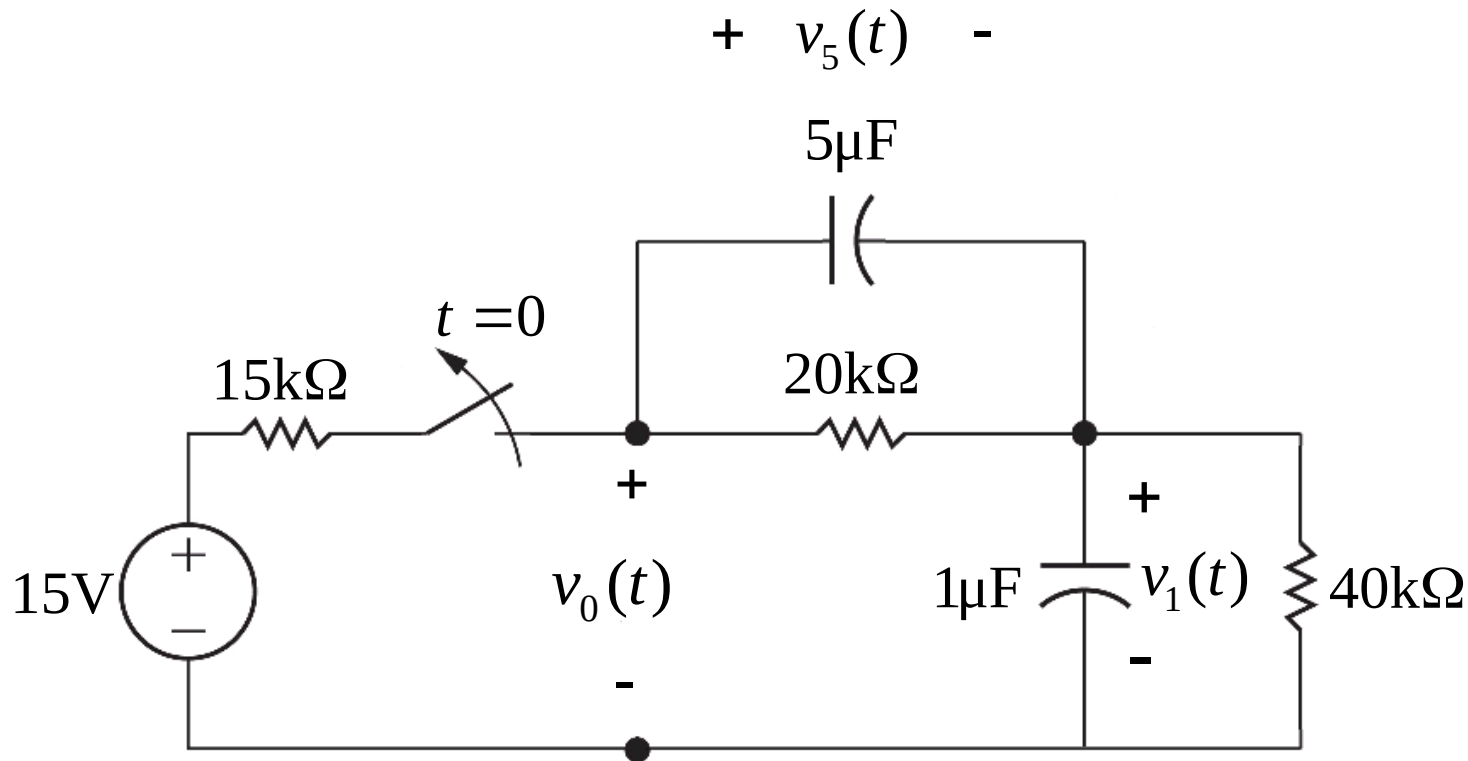Drill Exercise: Find $v_o(t)$ for $t \geq 0$



$$v_o(t) = v_5(t) + v_1(t) \quad \left. \vphantom{v_o(t)} \right\} \text{Solution has two parts}$$

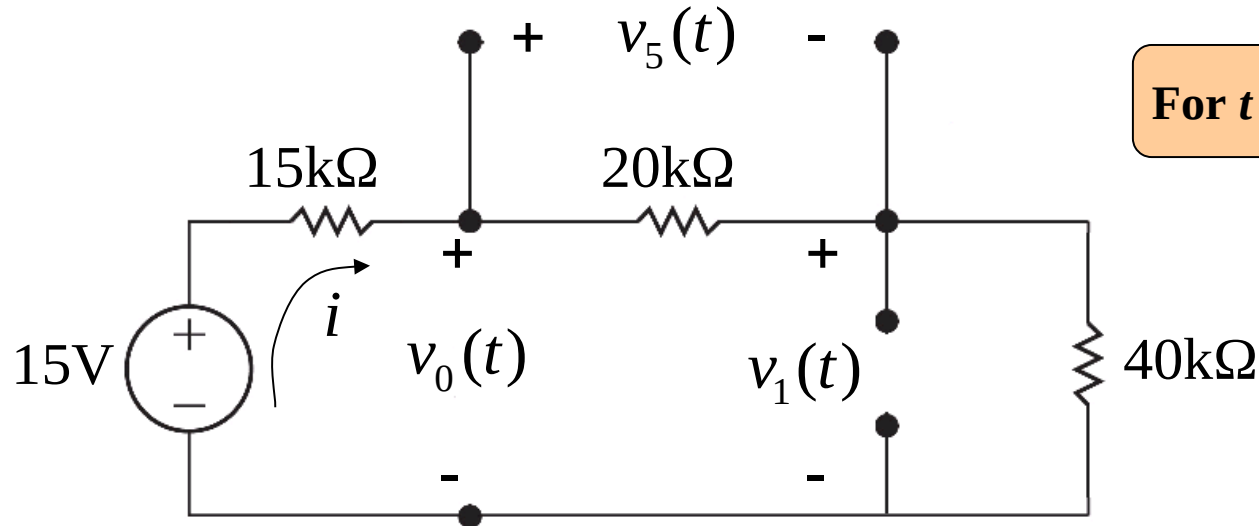Drill Exercise: Find $v_1(t)$ and $v_5(t)$ for $t \geq 0$ (Contd.)



For $t < 0$

- Steady State
- Caps Open

To Use RC Solution, We Have 2 Parts_


$$i = \frac{15}{(15 + 20 + 40)(k\Omega)} = \frac{15}{75(k\Omega)} = 0.2(mA) \quad \left. \vphantom{\frac{15}{75(k\Omega)}} \right\} \text{Ohm's Law}$$

$$\left. \begin{array}{l} \text{Ohm's Law} \end{array} \right\} \begin{cases} v_1(0^-) = 40(k\Omega) \times 0.2(mA) \longrightarrow v_1(0^-) = 8(V) \\ v_5(0^-) = 20(k\Omega) \times 0.2(mA) \longrightarrow v_5(0^-) = 4(V) \end{cases}$$

$$\left. \begin{array}{l} \text{KVL} \end{array} \right\} v_0(0) = 8 + 4 = 12(V) \longrightarrow \text{Use as a Check after we Obtain } v_0(t).$$

Drill Exercise (Contd.)

For $t \geq 0$ the circuit becomes

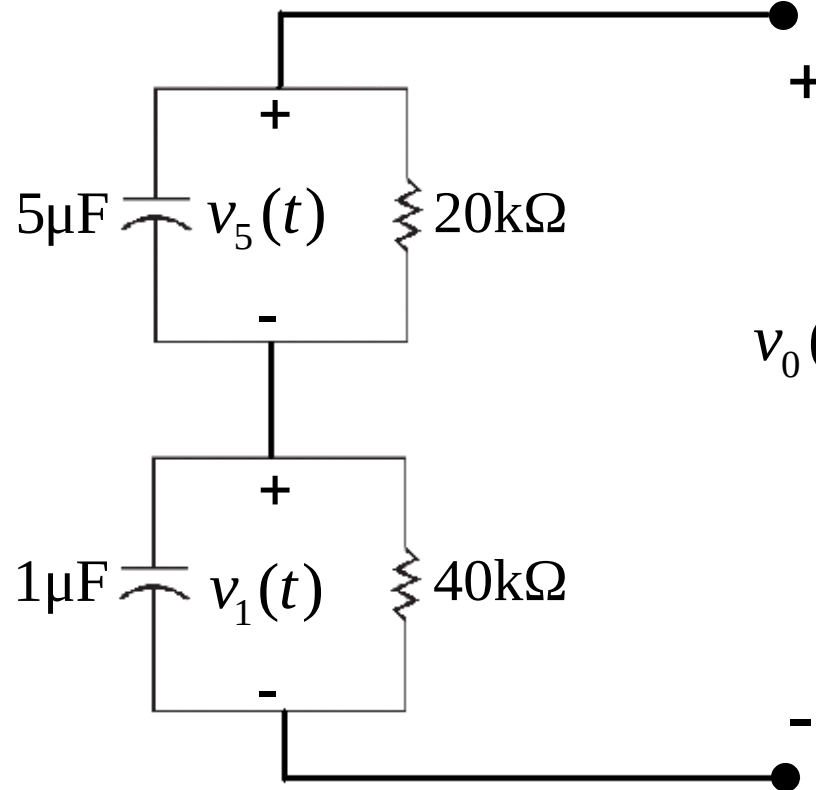

$$v_0(t) = v_1(t) + v_5(t)$$

2 RC Circuits In Series

$$\begin{aligned} \tau_1 &= RC = 40(\text{k}\Omega) \cdot 1(\mu\text{F}) \longrightarrow \tau_1 = 40(\text{ms}) \\ \tau_5 &= RC = 20(\text{k}\Omega) \cdot 5(\mu\text{F}) \longrightarrow \tau_5 = 100(\text{ms}) \end{aligned}$$

Find the Time Constants

Drill Exercise (Contd.)

$$v(t) = V_0 e^{-t/\tau} \quad \left. \vphantom{v(t)} \right\} \text{General Formula RC Parallel Circuit}$$

$$v_1(t) = v_1(0^-) e^{-t/\tau_1} = 8e^{-t/40(ms)} \quad \left. \vphantom{v_1(t)} \right\} \text{Plug in numbers}$$

$$\textcircled{1} \quad v_1(t) = 8e^{-25t} (V) \quad \left. \vphantom{v_1(t)} \right\} \text{Simplify}$$

$$v_5(t) = v_5(0^-) e^{-t/\tau_5} = 4e^{-t/100(ms)} \quad \left. \vphantom{v_5(t)} \right\} \text{Plug in numbers}$$

$$\textcircled{2} \quad v_5(t) = 4e^{-10t} (V) \quad \left. \vphantom{v_5(t)} \right\} \text{Simplify}$$

$$\textcircled{3} \quad v_0(t) = v_1(t) + v_5(t) \quad \left. \vphantom{v_0(t)} \right\} \text{KVL}$$

$$v_0(t) = [8e^{-25t} + 4e^{-10t}] (V) \quad t \geq 0 \quad \left. \vphantom{v_0(t)} \right\} \text{Substitute } \textcircled{1} \text{ and } \textcircled{2} \text{ into } \textcircled{3}$$

$$v_0(t=0) = 8 + 4 = 12(V) \quad \underline{\text{Checks}}$$

Drill Exercise (Contd.)

b) After $t = 60$ (ms), What % of Energy is Dissipated ?

→ Use $W = \frac{1}{2} C V^2$

Initial Energy Stored in Circuit :

$$w_1(0^-) = \frac{1}{2} C v_1^2(0^-) = \frac{1}{2} (1(\mu F)) (8)^2 = 32(\mu J) \quad \left\{ \text{Initial Energy in } 1\mu F \text{ Capacitor} \right\}$$

$$w_5(0^-) = \frac{1}{2} C v_5^2(0^-) = \frac{1}{2} (5(\mu F)) (4)^2 = 40(\mu J) \quad \left\{ \text{Initial Energy in } 5\mu F \text{ Capacitor} \right\}$$

$$w_{\text{Total}}(0^-) = w_1(0^-) + w_5(0^-) = 72(\mu J) \quad \left\{ \text{Total Initial Energy} \right\}$$

$$v_1(t) = 8e^{-25t} \quad v_5(t) = 4e^{-10t} \quad \left\{ \text{Analytical Expression} \right\}$$

$$v_1(60\text{ms}) = 1.79\text{V} \quad v_5(60\text{ms}) = 2.20\text{V} \quad \left\{ \text{Plug in } 60\text{ms} \text{ in Analytical Expression} \right\}$$

$$w_1(60\text{ms}) = \frac{1}{2} (1(\mu F)) (1.79)^2 = 1.59(\mu J) \quad \left\{ \text{Energy in } 1\mu F \text{ Capacitor at } 60\text{ms} \right\}$$

$$w_5(60\text{ms}) = \frac{1}{2} (5(\mu F)) (2.20)^2 = 12.05(\mu J) \quad \left\{ \text{Energy in } 5\mu F \text{ Capacitor at } 60\text{ms} \right\}$$

$$w_{\text{Total}}(60\text{ms}) = w_1(60\text{ms}) + w_5(60\text{ms}) = 13.64(\mu J) \quad \left\{ \text{Total Energy at } 60\text{ms} \right\}$$

Drill Exercise (Contd.)

$$\begin{aligned} W_{diss} &= W_{Total}(0^-) - W_{Total}(60(ms)) \quad \left\{ \text{Energy Dissipated from } t = 0 \text{ to } t = 60 \text{ ms} \right. \\ &= 72(\mu J) - 13.64(\mu J) \quad \left. \left\{ \text{Plug in the numbers} \right\} \right. \end{aligned}$$


$$W_{diss} = 58.36(\mu J) \quad \left\{ \text{Energy dissipated by the capacitors after } 60(ms) \right.$$

$$\% \text{ dissipate} = \frac{W_{diss}}{W_{Total}(0^-)} \times 100\% = \frac{58.36}{72} \times 100\% \quad \left\{ \text{Plug in the numbers} \right.$$

$$\% \text{ dissipated} = 81.056\%$$

Drill Exercise:

Find $v(t)$ for $t \geq 0$

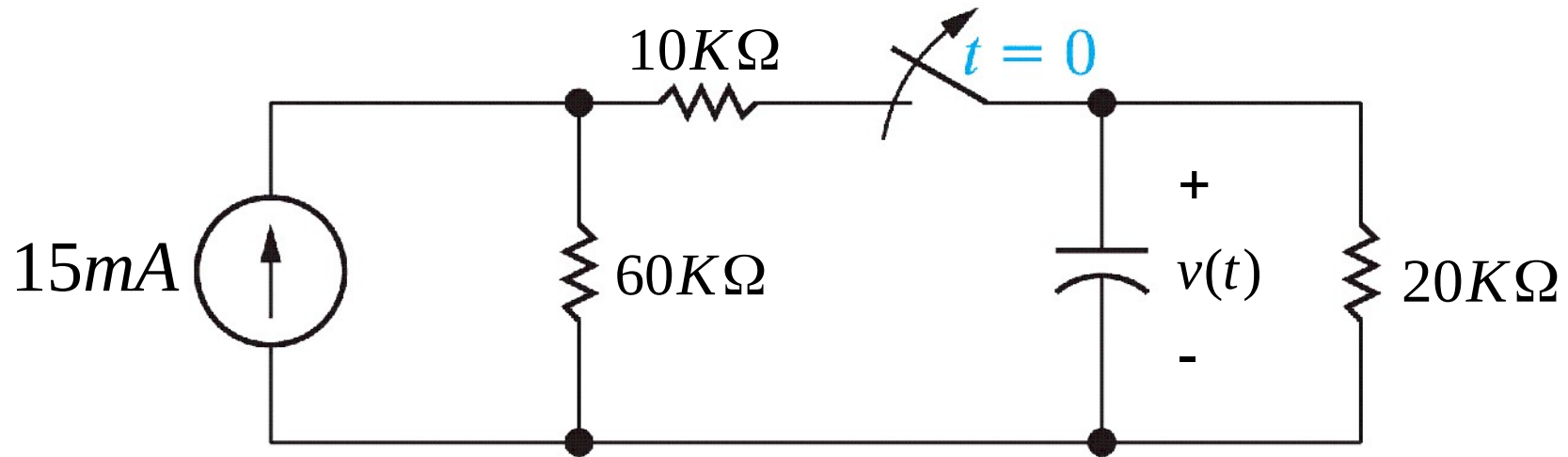


At Steady State \Rightarrow Capacitor is Open

Drill Exercise: Find $v(0)$

(Contd.)

a) For $t < 0$

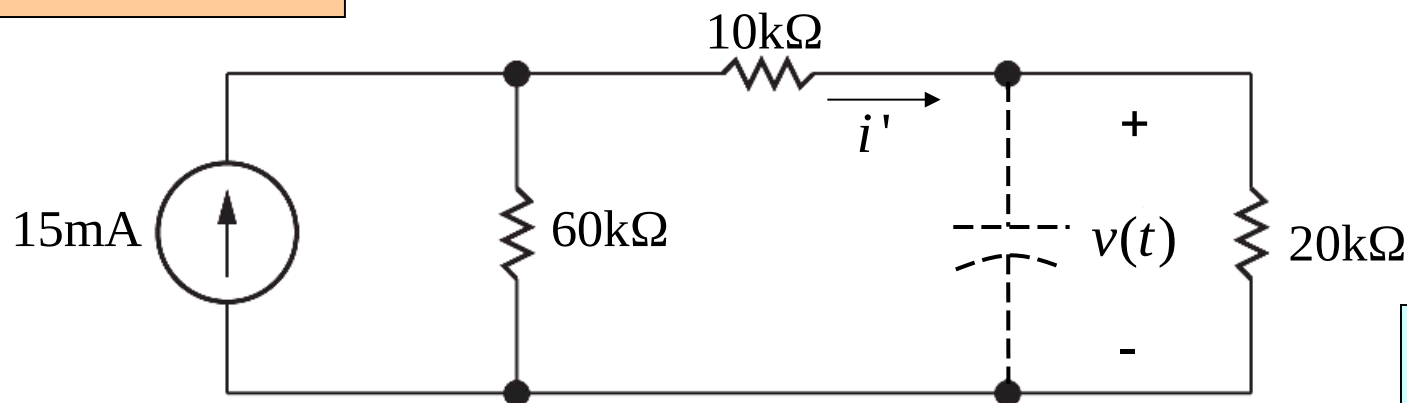

**Steady State.
Capacitor Open.**

$$\textcircled{1} \quad v(0^-) = V_0 = i' \cdot 20(k\Omega) \quad \left. \vphantom{v(0^-)} \right\} \text{Ohm's Law}$$


$$\textcircled{2} \quad i' = 15(mA) \left[\frac{60(k\Omega)}{60(k\Omega) + (10(k\Omega) + 20(k\Omega))} \right] = 10(mA) \quad \left. \vphantom{i'} \right\} \text{Current Division}$$

$$V_0 = 10(mA) \cdot 20(k\Omega) \quad \left. \vphantom{V_0} \right\} \text{Substitute } \textcircled{2} \text{ into } \textcircled{1}$$

$$V_0 = 200(V) \quad \left. \vphantom{V_0} \right\} \text{Voltage can't change instantly}$$

Drill Exercise (Contd.)

b) For $t \geq 0$ the circuit becomes

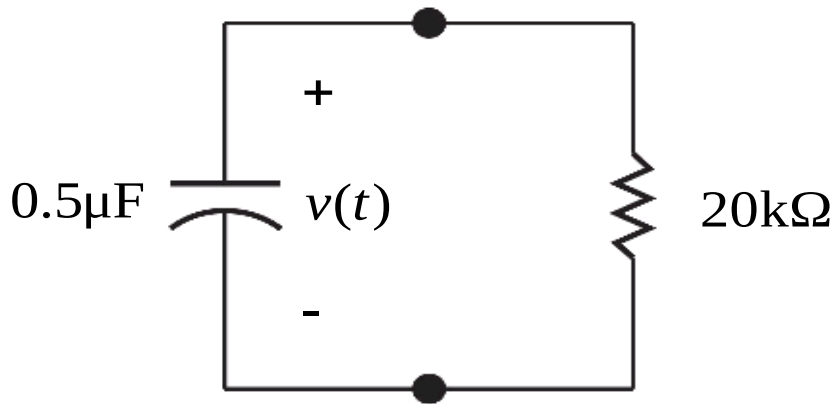

$$\tau = RC = 20(k\Omega) \cdot 0.5(\mu F)$$

$$\tau = 10(ms)$$

$$V_0 = 200(V)$$

Time
Constant
Formula

c) Analytical Expression

$$v(t) = V_0 e^{-t/\tau} = 200 e^{-t/10(ms)}$$

Plug in the numbers

$$v(t) = 200 e^{-100t} (V)$$

d) $w(0^-) = \frac{1}{2} C V_0^2 = \frac{1}{2} (0.5(\mu F)) (200(V))^2$

Calculate the Initial Energy

$$w(0^-) = 10(mJ)$$

Drill Exercise (Contd.)

How Long Does it Take for 75% of the Energy to be Dissipated?

e) Analytical Expression for the Energy

$$w(t) = \frac{1}{2} C v^2(t) = \frac{1}{2} (0.5(\mu F)) (200e^{-100t})^2 = 10e^{-200t} (mJ)$$

If 75% Dissipated,
25% is Left.



Find t' where $w(t') = 25\% w(0^-)$

25% of Initial Energy

$$w(0^-) = 10$$


$$10e^{-200t'} = 0.25 \cdot w(0) = 0.25(10) = 2.5(mJ) \quad \left. \vphantom{10e^{-200t'}} \right\} \text{Solve for } t'$$

$$\therefore t' = 6.93(ms)$$

It Takes 6.93(ms) for 75% of the Energy to be Dissipated.

RL Step Response: Charging Up

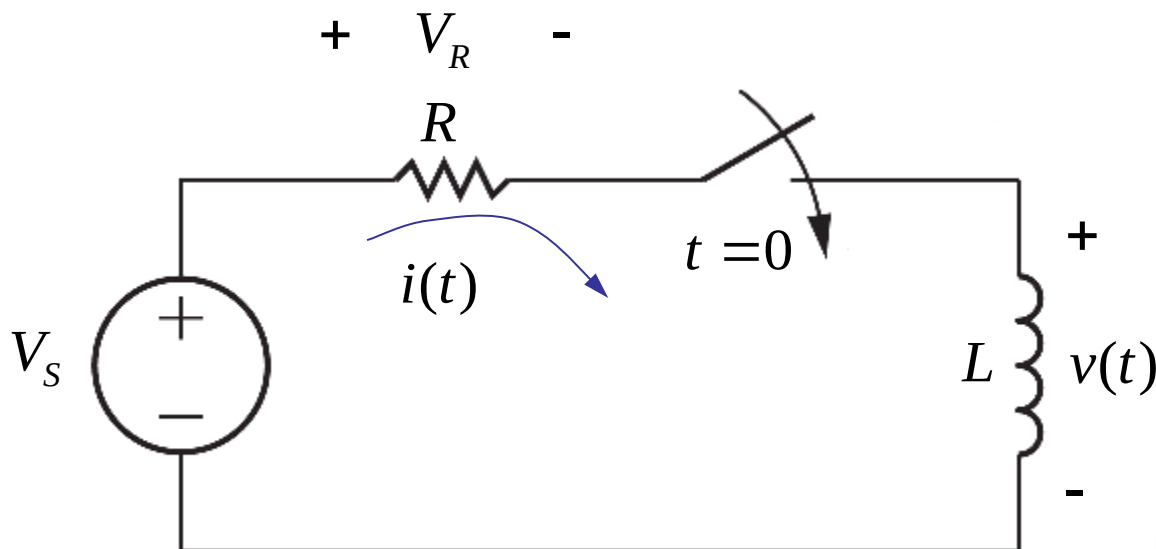Response to Sudden Application of dc I or V .



Switch Closed at $t = 0$
 L “Charges Up”

i Can't Change Instantly

For $t \geq 0_-$

KVL \rightarrow $V_S = V_R + v$ } Substitute $V_R = iR$ and $v = L \frac{di}{dt}$

$$V_S = Ri + L \frac{di}{dt}$$

Differential Equation

RL Step Response (Contd.)

Solve for $i(t)$ by Separation of Variables

$$\left. \frac{di}{dt} = \frac{V_s - Ri}{L} = -\frac{R}{L} \left[i - \frac{V_s}{R} \right] \right\} \text{Solve for } \frac{di}{dt}$$

$$\left. \frac{di}{i - \frac{V_s}{R}} = \frac{-R}{L} dt \right\} \text{Separate Differentials}$$

Integrate Both Sides

$$\int \frac{di}{i - \frac{V_s}{R}} = \int \frac{-R}{L} dt + K \leftarrow \text{Integration Constant}$$

RL Step Response (Contd.)

$$\int \frac{di}{i - \frac{V_s}{R}} = \int -\frac{R}{L} dt + K \quad \left\{ \begin{array}{l} \text{Need to integrate the LHS} \end{array} \right.$$

Integral Tables $\left\{ \int \frac{dx}{x - c} = \ln(x - c) \right\}$ where c is a constant

$$\textcircled{1} \quad \ln \left[i(t) - \frac{V_s}{R} \right] = -\frac{R}{L} t + K \quad \left\{ \begin{array}{l} \text{Use above equation to integrate} \end{array} \right.$$

$$i(t=0) \equiv i(0) = I_0 \quad \left\{ \begin{array}{l} \text{Use } i(0) \text{ to find the value of } K \end{array} \right.$$

$$\ln \left[i(0) - \frac{V_s}{R} \right] = -\frac{R}{L} (0) + \textcircled{K} \quad \left\{ \begin{array}{l} \text{Substitute } t = 0 \text{ into } \textcircled{1} \end{array} \right.$$

$$\therefore K = \ln \left[I_0 - \frac{V_s}{R} \right] \quad \left\{ \begin{array}{l} \text{After solving for } K \end{array} \right.$$

RL Step Response (Contd.)

$$\ln \left[\frac{i(t) - \frac{V_s}{R}}{I_0 - \frac{V_s}{R}} \right] = -\frac{R}{L}t$$

Substitute expression for K into ①

$$\therefore i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau} \quad t \geq 0; \quad \tau = \frac{L}{R}$$


After solving for $i(t)$

If inductor is not initially charged then $I_0 = 0$

$$\therefore i(t) = \frac{V_s}{R} \left[1 - e^{-\frac{t}{\tau}} \right] \quad t \geq 0; \quad \tau = \frac{L}{R}$$

Expression for $i(t)$ with $I_0 = 0$

Graphical Illustration of Step Response

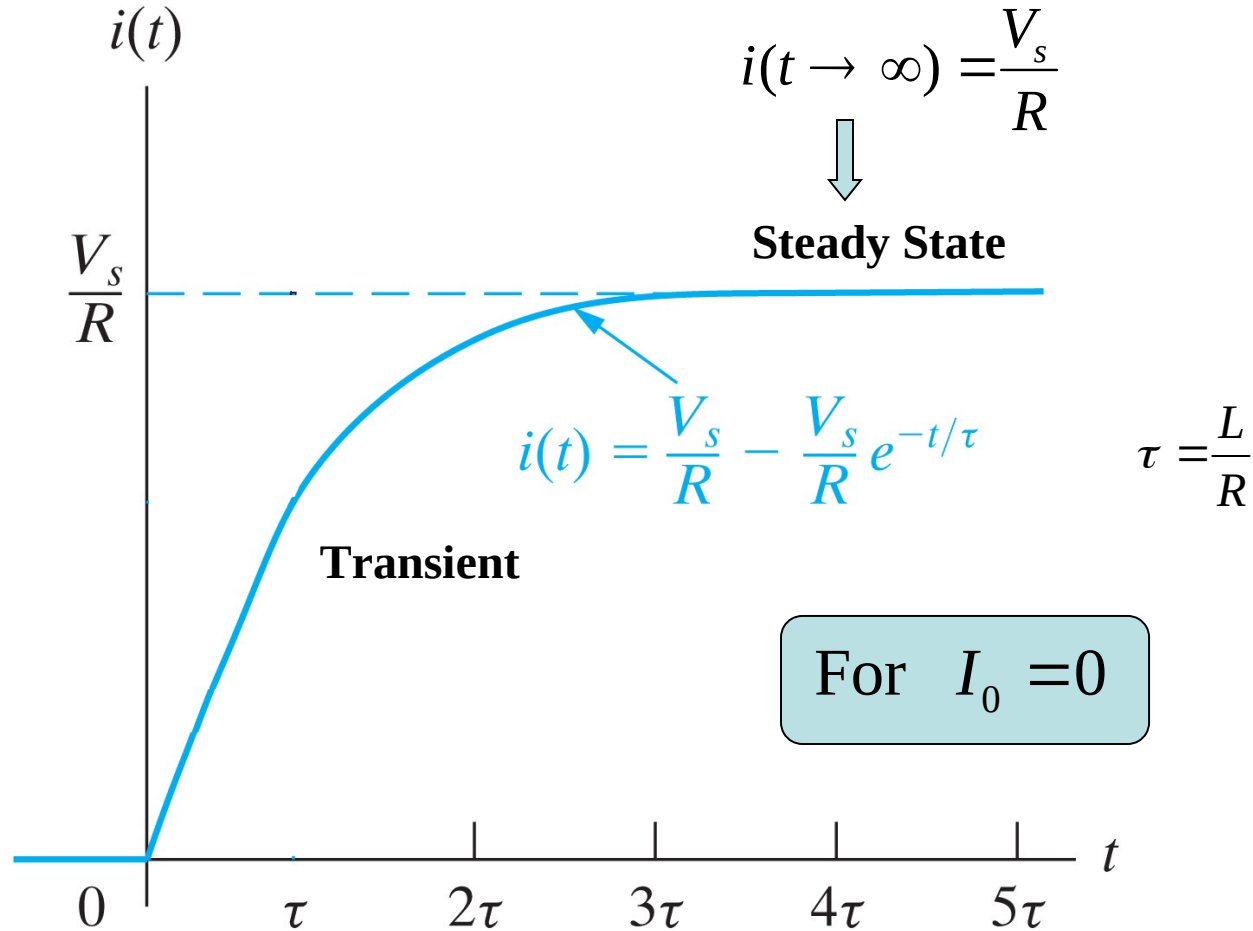

RL Step Response: Current in the Inductor

$$v(t) = L \frac{di(t)}{dt} \left\{ \text{Substitute } i(t) = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R} \right) e^{-\left(\frac{R}{L}\right)t} \right.$$

$$v(t) = (V_s - I_o R) e^{-\frac{t}{\tau}}$$

$$v(0^-) = 0 \left\{ \begin{array}{l} \text{From original circuit} \end{array} \right.$$

$$v(0) = V_s - I_o R \left\{ \begin{array}{l} \text{Step change in voltage} \end{array} \right.$$




For $I_o = 0$


$$v(t) = V_s e^{-\frac{t}{\tau}}$$

$$v(0^-) = 0$$

$$v(0) = V_s$$

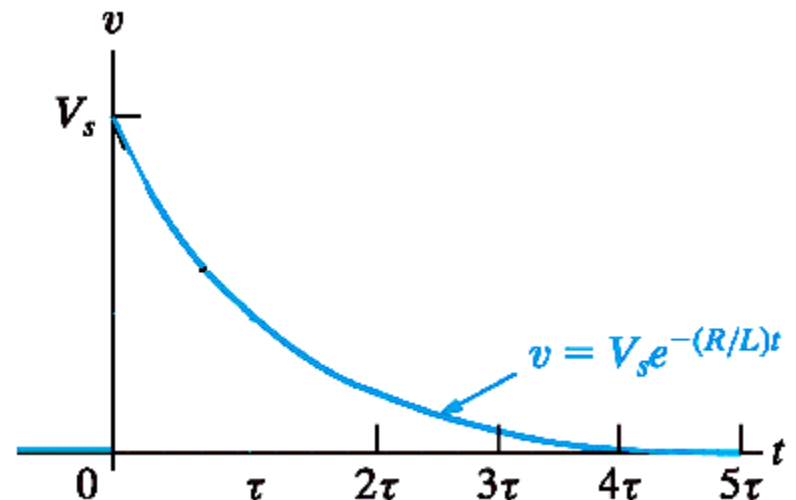

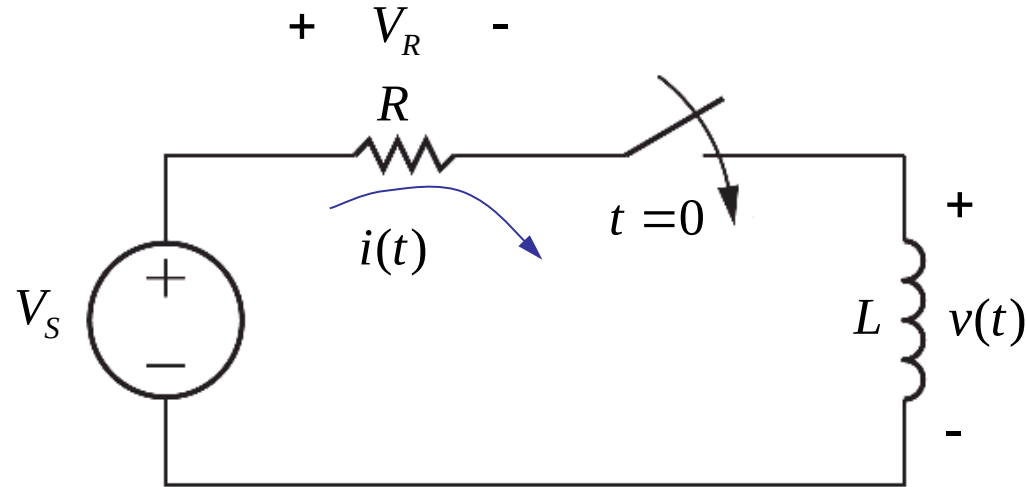RL Step Response: Voltage Across Inductor (Contd.)



Summarize Ideas ...After Switch Closes


1) $i(0^-) = 0 \quad \therefore V_R = 0 \quad \therefore v(t) = V_s$

All voltage dropped across L , since none across R .


2) $i(t)$ Increases toward $\frac{V_s}{R}$, since L is short in steady state.

$v(t)$ Decays toward zero, and all voltage is across R in Steady State.

Example: Find $v(t)$ for $t \geq 0$

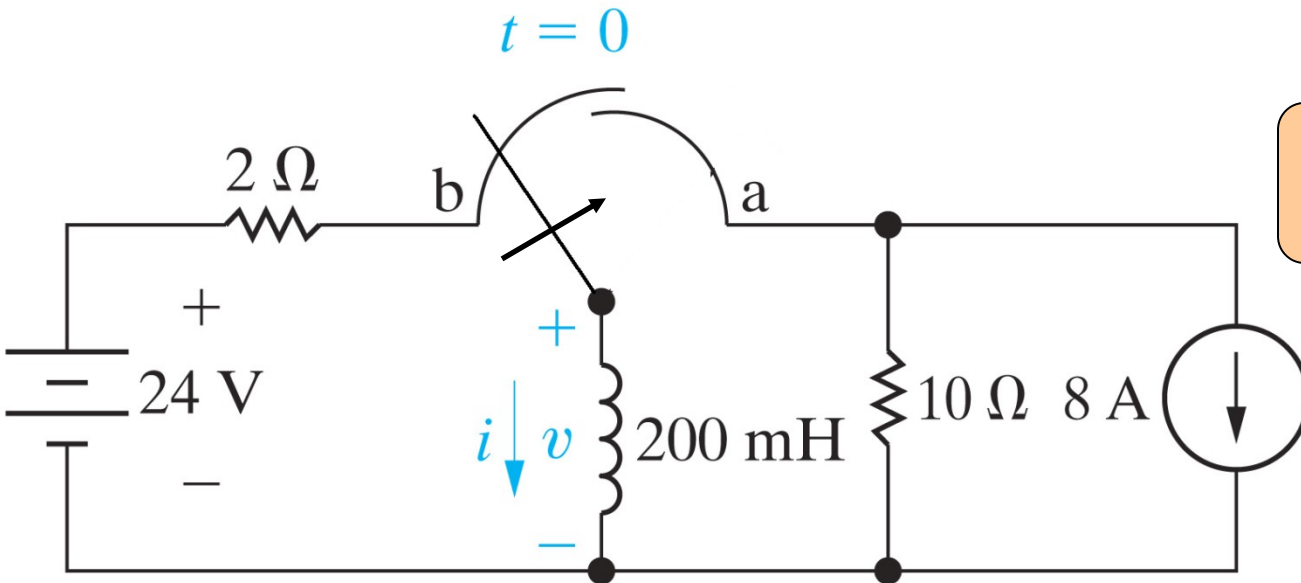

a) $t < 0$: Steady State;
 L is a short.

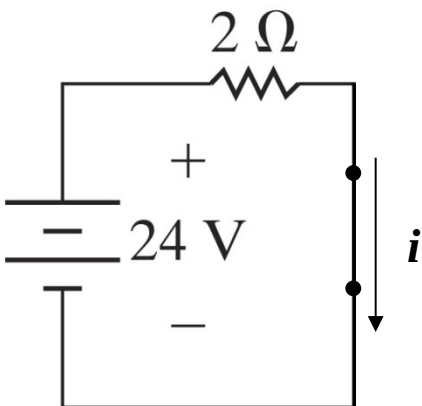


$$i(0^-) = i(0^+) = I_0 = \frac{24(V)}{2\Omega} \quad \left. \vphantom{\frac{24(V)}{2\Omega}} \right\} \text{Ohm's Law}$$


$$i(0^+) = 12(A)$$

$$v(0^-) = 0 \quad \text{because } L \text{ is a short}$$


Example (Contd.)

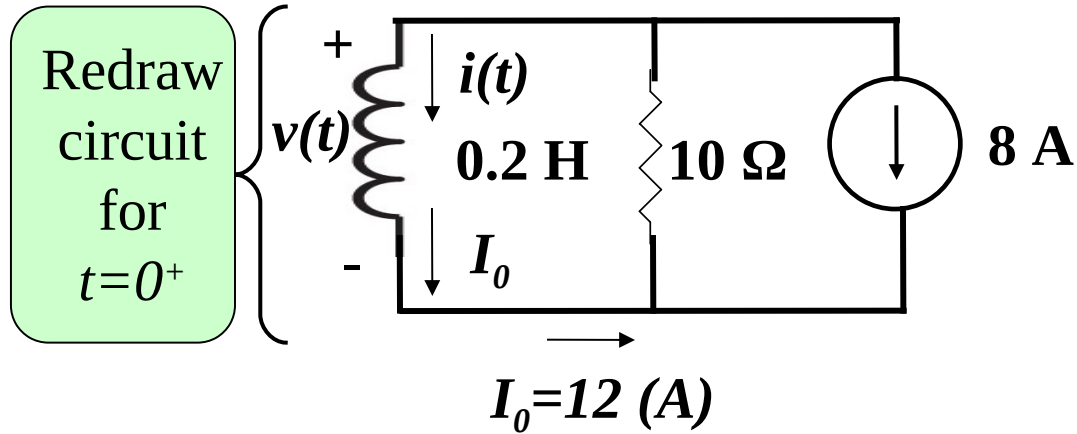

Thevenin Equivalent

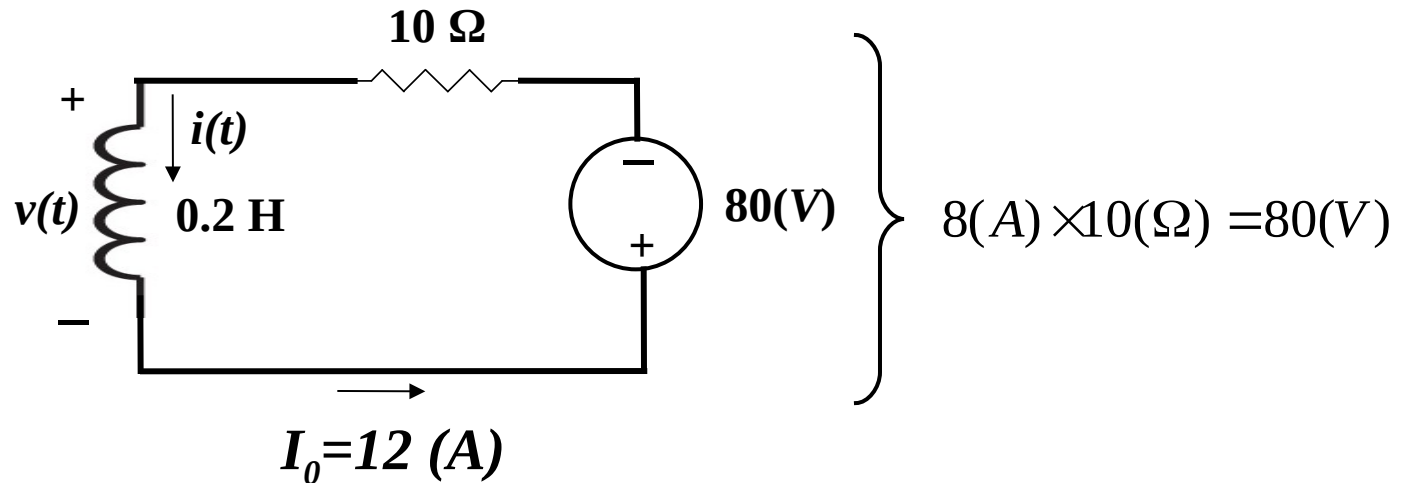

Example (Contd.)

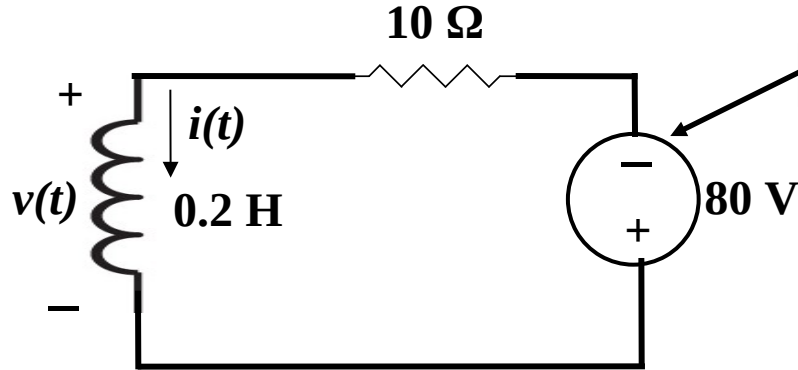

Note: V and I polarities
“opposite” to general circuit

$$i(t) = -\frac{V_s}{R} + \left(I_0 - \left[-\frac{V_s}{R} \right] \right) e^{-\frac{t}{\tau}}$$

Analytic expression for $i(t)$

$$i(t) = -\frac{80}{10} + \left(12 + \left[\frac{80}{10} \right] \right) e^{-\frac{t}{0.02}}$$

Plug in numbers

$$i(t) = (-8 + 20e^{-50t}) \text{ (A)} \quad t \geq 0$$

Time Constant

$$\tau = \frac{L}{R} = \frac{0.2(\text{H})}{10(\Omega)} = 0.02(\text{s})$$

$$\tau = 20(\text{ms})$$

$$v(t) = L \frac{di}{dt} = 0.2[0 + 20(-50)e^{-50t}] = -200e^{-50t} \text{ (V)} \quad t \geq 0$$

Find $v(t)$



Example: Plots (Contd.)

Find t' when $i(t') = 0$

$$0 = -8 + 20e^{-50t'}$$

$$\ln\left(\frac{8}{20}\right) = -50t'$$


$$\Rightarrow t' = 18.3 \text{ (ms)}$$

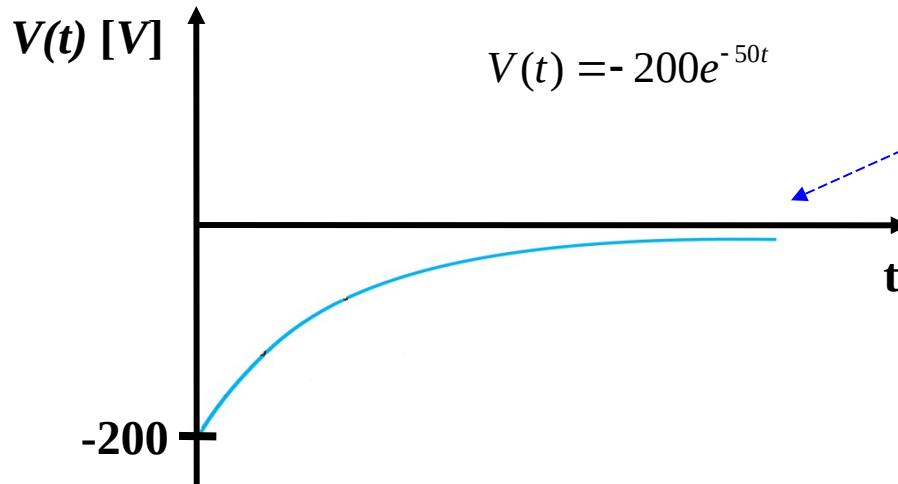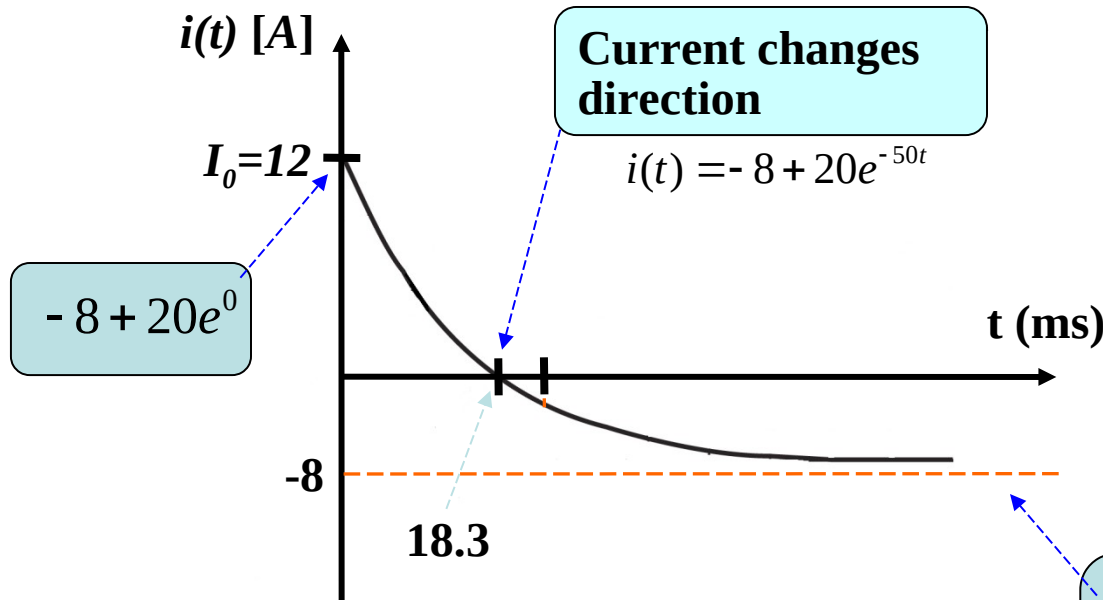

$$i(\infty) = -8 \text{ (A)}$$

$$V(\infty) = 0$$

Example: Find $i_o(t)$ for $t \geq 0$

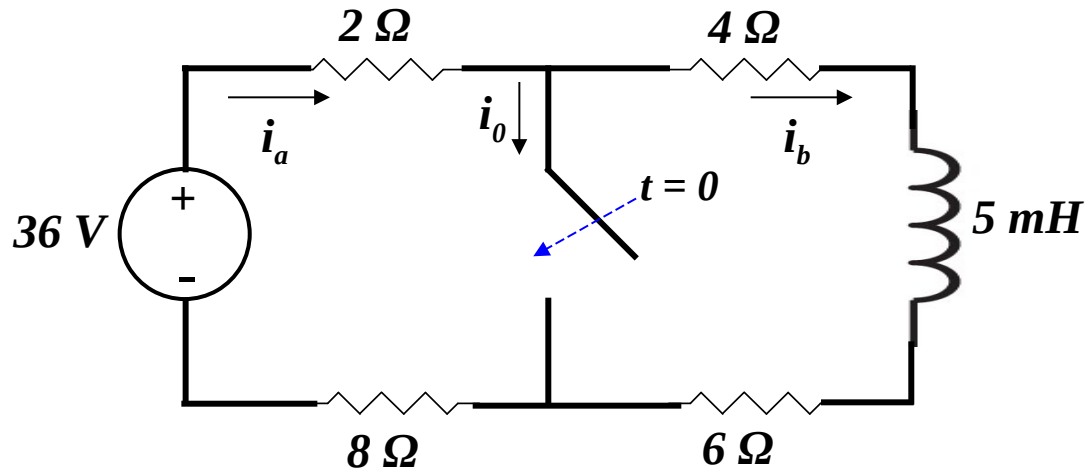

a) $-\infty \leq t < 0$ Steady State

$i_a = i_b$ } Inductor is Short


$i_a = 36(V) / (2 + 4 + 6 + 8)\Omega$ }

Ohm's Law

$i_a = 1.8(A)$

$i_o = 0 \Rightarrow i_o(0^-) = 0 \quad i_a(0^-) = i_b(0^-) = 1.8(A)$

Example (Contd.)

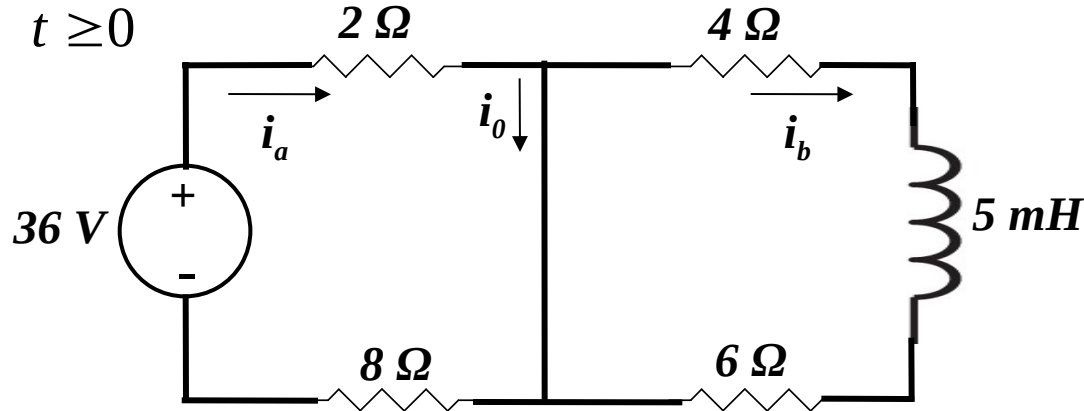

Current can't change instantly in L
Current circulating in both loops

KVL $\left\{ \begin{aligned} i_a(0) &= \frac{36V}{(2+8)\Omega} = 3.6(A) \end{aligned} \right.$

$i_a(0^-) = 1.8(A) \quad i_a(0) = 3.6(A)$

$i_b(0) = i_b(0^-) = 1.8(A)$

i_b can't change instantly

KCL $\left\{ \begin{aligned} i_0(t) &= i_a(t) - i_b(t) \end{aligned} \right.$

$i_0(0) = i_a(0) - i_b(0) = 3.6(A) - 1.8(A)$

$i_0(0) = 1.8(A)$


$i_0(0^-) = 0 \quad i_0(0) = 1.8(A)$

Example (Contd.)

The right-hand side of the circuit is shorted out for $t \geq 0$

b)

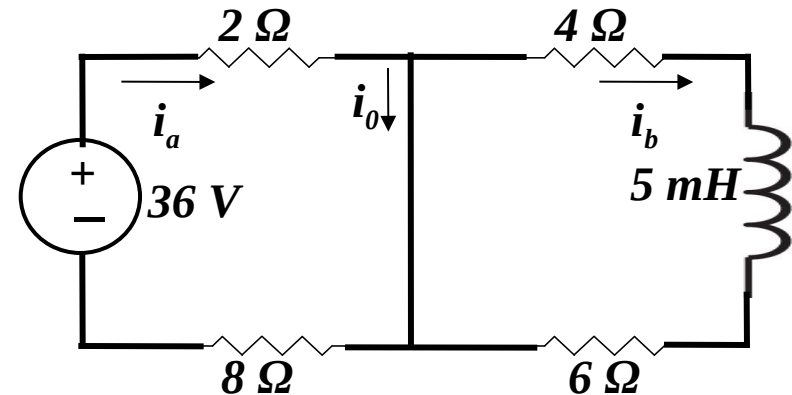RL Circuit Essentially
Isolated from the Rest of
the Circuit




$$i_b(t) = i_b(0)e^{-\frac{t}{\tau}} \quad i_b(0) = 1.8(A) \quad \left. \vphantom{i_b(t)} \right\}$$

Use analytic expression

$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3} H}{(4 + 6)\Omega} = 0.5(ms) \quad \left. \vphantom{\tau} \right\} \text{Time constant}$$

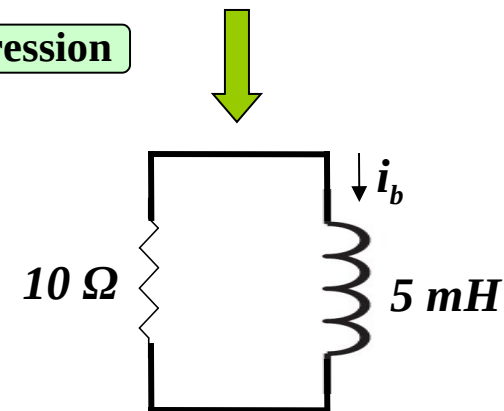
$$i_b(t) = 1.8e^{-2000t} (A) \quad t \geq 0$$



Example (Contd.)

Find $i_0(t)$ for $t \geq 0$

For $t \geq 0$

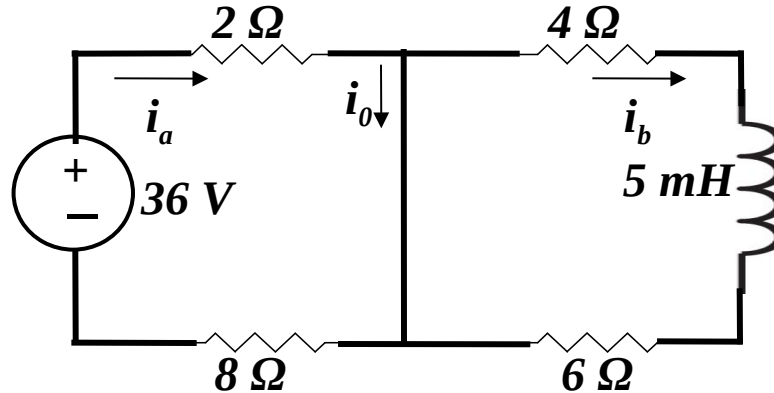

$$i_0(t) = i_a(t) - i_b(t) \quad \left\{ \text{KCL} \right.$$

$$i_a = \frac{36(V)}{(2 + 8)\Omega} = 3.6(A) \quad \left\{ \text{Ohm's Law} \right.$$


$$i_0(t) = (3.6 - 1.8e^{-2000t})(A) \quad t \geq 0 \quad \left\{ \begin{array}{l} \text{Plug in values} \\ \text{Use } i_b \text{ from} \\ \text{previous slide} \end{array} \right.$$

$$i_0(0) = 3.6 - 1.8 = 1.8(A)$$

$$i(0^-) = 0$$

i_0 changed instantly

RC Step Response

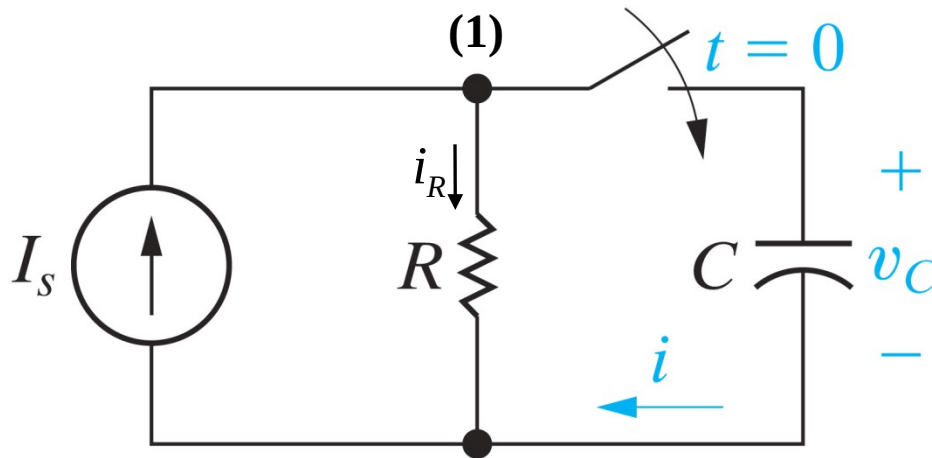

Find $i(t)$ for $t \geq 0$

Find $v_c(t)$ for $t \geq 0$

$v_c(0^-) = V_0$

$$i_R = \frac{v_c}{R} \quad \left. \vphantom{i_R = \frac{v_c}{R}} \right\} \text{Ohm's Law}$$

$$i = C \frac{dv_c}{dt} \quad \left. \vphantom{i = C \frac{dv_c}{dt}} \right\} \text{Capacitor equation}$$

$$I_s = i_R + i \quad \left. \vphantom{I_s = i_R + i} \right\} \text{KCL at (1)}$$

$$I_s = \frac{v_c}{R} + C \frac{dv_c}{dt} \quad \left. \vphantom{I_s = \frac{v_c}{R} + C \frac{dv_c}{dt}} \right\} \text{Substitute for } i_R, i_c$$

$$\frac{I_s}{C} = \frac{v_c}{RC} + \frac{dv_c}{dt} \quad \left. \vphantom{\frac{I_s}{C} = \frac{v_c}{RC} + \frac{dv_c}{dt}} \right\} \text{Divide by C}$$

Same form as for Inductor

$$V_s = Ri_L + L \frac{di_L}{dt}$$

$$\frac{V_s}{L} = \frac{R}{L} i_L + \frac{di_L}{dt}$$

Comparison between Inductor and Capacitor

Inductor

$$V_s$$

$$L$$

$$\tau = \frac{L}{R}$$

$$i_L(t)$$

$$I_0$$

Capacitor

$$I_s$$

$$C$$

$$\tau = RC$$

$$v_C(t)$$

$$V_0$$

RC Step Response

$$v_c(t) = I_s R + (V_0 - I_s R)e^{-t/RC}; \quad t \geq 0 \quad \left. \vphantom{v_c(t)} \right\} \text{Solution to differential equation}$$

$$v_c(t) = I_s R \left[1 - e^{-t/RC} \right]; \quad t \geq 0 \quad \left. \vphantom{v_c(t)} \right\} v_c(t) \text{ when } V_0 = 0$$


$$i(t) = C \frac{dv_c}{dt}; \quad t \geq 0 \quad \left. \vphantom{i(t)} \right\} \text{Find } i(t) \text{ from } v_c(t)$$

$$i(t) = \left(I_s - \frac{V_0}{R} \right) e^{-t/\tau}; \quad \tau = RC; \quad t \geq 0 \quad \left. \vphantom{i(t)} \right\} \text{After substitution for } v_c(t)$$

$$i(t) = I_s e^{-t/\tau}; \quad t \geq 0 \quad \left. \vphantom{i(t)} \right\} i(t) \text{ when } V_0 = 0$$

Drill Exercise

Find $V_A(t)$ for $t \geq 0$

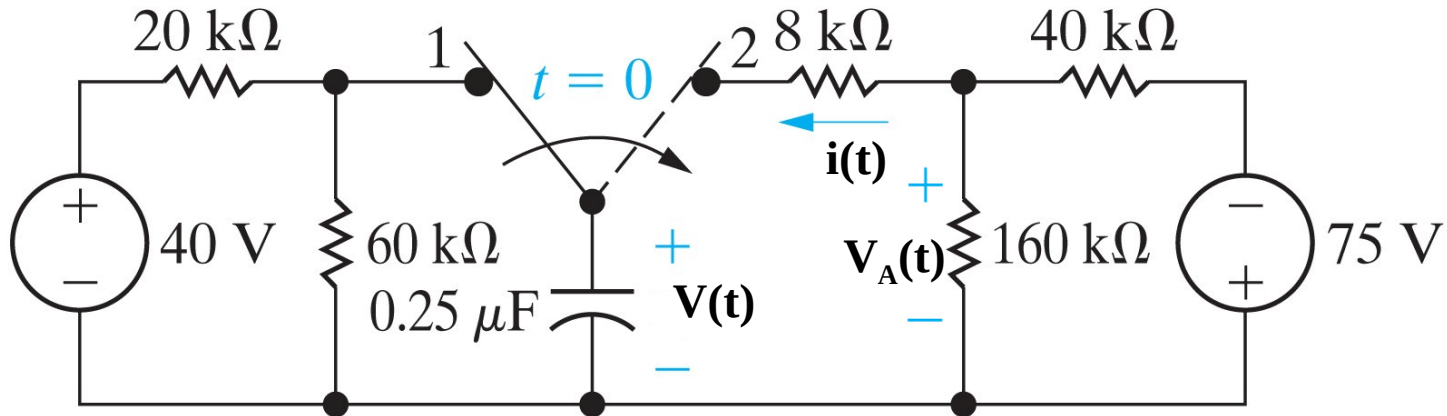


$t < 0$

$$V_A(0^-) = -\frac{160}{40 + 160} 75 = -60$$

Voltage Division


Capacitor is Open In Steady State

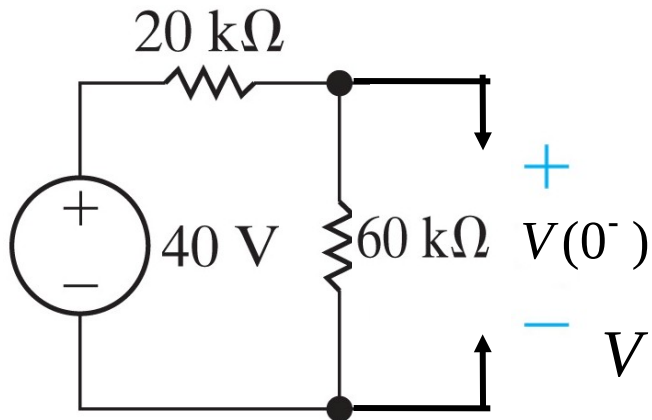


Voltage Division

$$V(0^-) = 40(V) \frac{60}{60 + 20} \Rightarrow V_0 = 30(V)$$

Drill Exercise (Contd.)

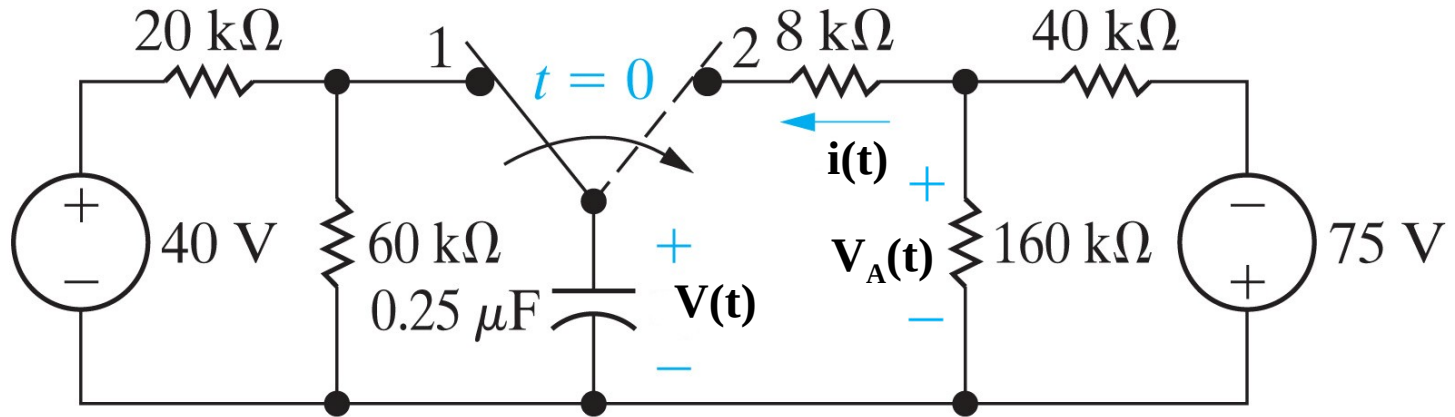

$t \geq 0$

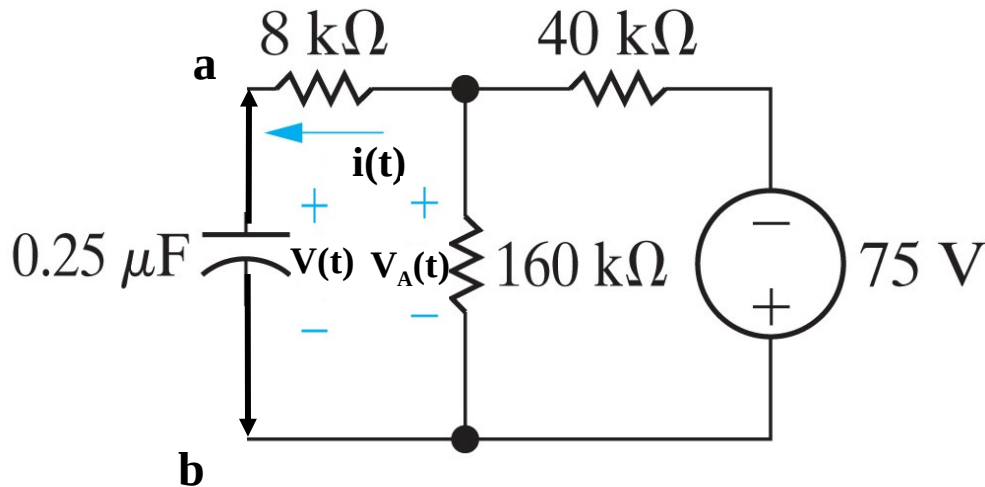

**Need Norton
Equivalent Between a-
b, to use Derived
Equations For RC
Circuits**


Drill Exercise (Contd.)

Short voltage source to obtain R_{Th}

Parallel + Series

$$R_{ab} = R_{Th} = (40K \parallel 160K) + 8K$$

$$R_{Th} = 40(K\Omega)$$

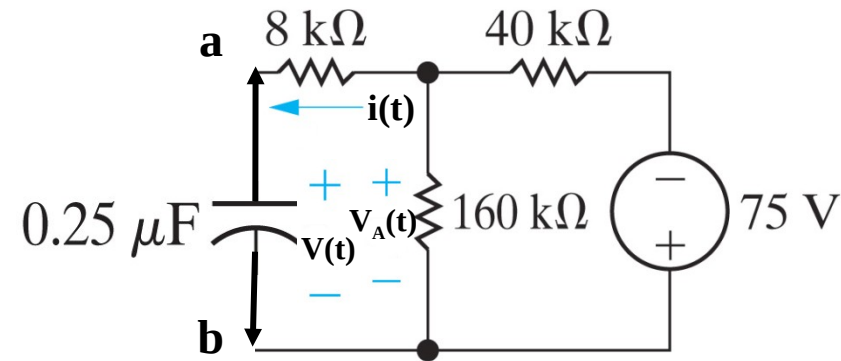

Open circuit voltage, V_{ab} , to obtain $V_{oc} = V_{Th}$

$8K$ Resistor is open, \therefore not relevant.

$$V_{oc} = V_{ab} \equiv V_{Th} = -75V \left[\frac{160K}{160K + 40K} \right] \left. \vphantom{V_{oc}} \right\} \text{Voltage Division}$$


$$V_{Th} = -60(V)$$

$$\therefore I_N = V_{Th} / R_{Th}$$

$$I_N = -60 / 40(K) = -1.5(mA)$$

Drill Exercise (Contd.)

Norton equivalent
circuit for $t \geq 0$

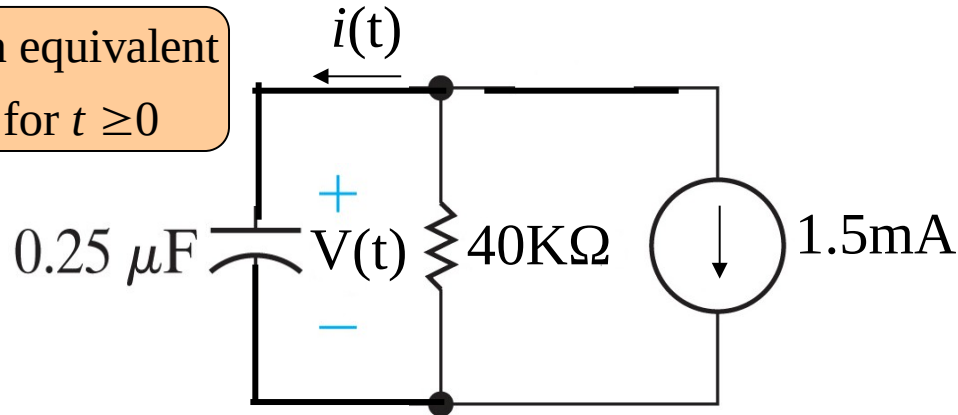

Time Constant

$$\tau = RC = 40K\Omega[0.25\mu F]$$

$$\tau = 10(ms)$$

$$V(t) = I_s R + (V_0 - I_s R)e^{-t/\tau}; \quad t \geq 0 \quad \left\} \text{Analytic solution}\right.$$

$$V(t) = (-1.5mA) 40K\Omega + (30 - [-1.5mA] 40K\Omega)e^{-t/0.01} \quad \left\} \text{Plug in numbers}\right.$$

$$= -60 + (30 + 60)e^{-100t} \quad \left\} \text{Simplify}\right.$$

$$V(t) = (-60 + 90e^{-100t})(V)$$

Note


$$V(0) = 30 (V)$$

$$V(\infty) = -60 (V)$$

$$i(t) = C \frac{dV}{dt} = 0.25\mu F[-100(90)e^{-100t}] \quad \left\} \text{Find } i(t) \text{ by using capacitor formula}\right.$$

$$i(t) = -2.25e^{-100t} (mA); \quad t \geq 0$$

Drill Exercise (Contd.)

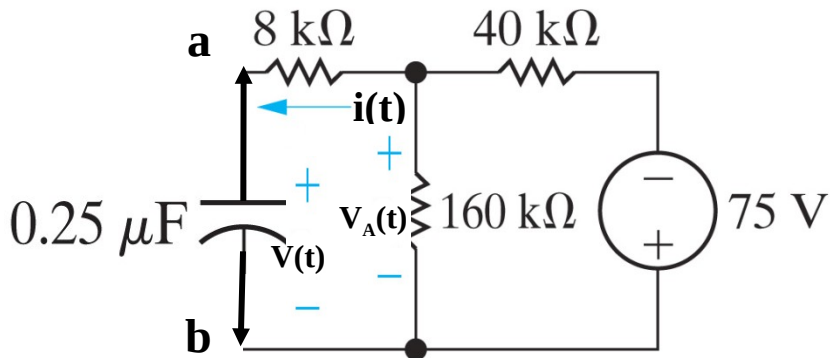

Find $V_A(t)$ for $t \geq 0^+$ } This was the original problem statement

$$V_A(t) = 8K \cdot i(t) + V(t) \} \text{ KVL}$$

$$V_A(t) = 8000 \left[-2.25e^{-100t} (mA) \right] + \left[-60 + 90e^{-100t} \right] \rightarrow \text{Substitute for } i(t)$$

$$V_A(t) = -18e^{-100t} - 60 + 90e^{-100t} \} \text{ Simplify}$$

and $V(t)$ from previous slide

$$V_A(t) = (72e^{-100t} - 60) (V) \quad t \geq 0$$

$$V_A(0) = 12 \} \text{ From the above expression}$$

$$V_A(0^-) = -60 \} \text{ From the original circuit}$$

$V_A(t)$ Changes Instantly at $t=0$, so $V_A(t)$ is discontinuous at $t=0$.

General Solution for RL & RC Circuits

Differential Equations are of the same form

Inductor

Capacitor

Natural	$\frac{di_L}{dt} + \frac{R}{L}i_L = 0$	$\frac{dv_c}{dt} + \frac{v_c}{RC} = 0$
Step	$\frac{di_L}{dt} + \frac{R}{L}i_L = \frac{V_s}{L}$	$\frac{dv_c}{dt} + \frac{v_c}{RC} = \frac{I_s}{C}$
Time-Constant	$\frac{R}{L} = \frac{1}{\tau_{RL}}$	$\frac{1}{RC} = \frac{1}{\tau_{RC}}$

General Solution for RL & RC Circuits

(Contd.)

- Let $x(t)$ be the Unknown Quantity.

$$\left. \begin{matrix} i_L, & v_L, & i_c, & v_c \end{matrix} \right\} \begin{matrix} x(t) \text{ could be any} \\ \text{of these signals} \end{matrix}$$

- Let K be a Constant.

$$\left. \begin{matrix} V_s/L, & I_s/C, & 0 \end{matrix} \right\} \begin{matrix} K \text{ could be any} \\ \text{of these constants} \end{matrix}$$

$$\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = K$$

General form of
Differential Equations

- Final Value x_f as $t \rightarrow \infty$ } Steady State

$$\left. \frac{dx(t)}{dt} \right|_{t \rightarrow \infty} = 0 \Rightarrow \frac{x_f}{\tau} = K$$

$$\therefore x_f = K\tau$$

Solve General Differential Equation

$$\frac{dx}{dt} = K - \frac{x}{\tau} = \frac{K\tau - x}{\tau} = \frac{x_f - x}{\tau} = - \frac{(x - x_f)}{\tau}$$

Rearrange differential equation where $x_f = K\tau$

$$\frac{dx}{x - x_f} = - \frac{1}{\tau} dt$$

Separate variables

Arbitrary Constant

$$\int \frac{dx}{x - x_f} = - \frac{1}{\tau} \int dt + Z$$

Integrate both sides

$$* \ln(x - x_f) = - \frac{t}{\tau} + Z$$

Find anti-derivative

Solve General Differential Equation (Contd.)

⌘ $\ln(x - x_f) = -\frac{t}{\tau} + Z$ } Find anti-derivative

1 $\ln[x(t_0) - x_f] = -\frac{t_0}{\tau} + Z$ } Substitute $t = t_0$ into ⌘ to find Z

2 $Z = \ln[x(t_0) - x_f] + \frac{t_0}{\tau}$ } Solve for Z

3 $\ln(x - x_f) = -\frac{t}{\tau} + \left(\frac{t_0}{\tau} + \ln[x(t_0) - x_f] \right)$ } Substitute
2 into ⌘

4 $\ln\left[\frac{x - x_f}{x(t_0) - x_f} \right] = -\frac{t - t_0}{\tau}$ } Simplify 3

$x(t) = x_f + [x(t_0) - x_f] e^{\frac{-(t - t_0)}{\tau}}$ } Solve 4
for $x(t)$

First Order DE for RC or RL Circuits

$$\frac{dx}{dt} + \frac{x(t)}{\tau} = K$$


Differential Equation

$$x(t) = x_f + \left[x(t_0) - x_f \right] e^{-\frac{(t-t_0)}{\tau}}$$

Solution where
 $x_f = K\tau$

- 1. Initial time; t_0
- 1. Initial Value; $x(t_0)$
- 1. Final Value; x_f
- 1. Time Constant; τ

Example: Find $v_c(t)$

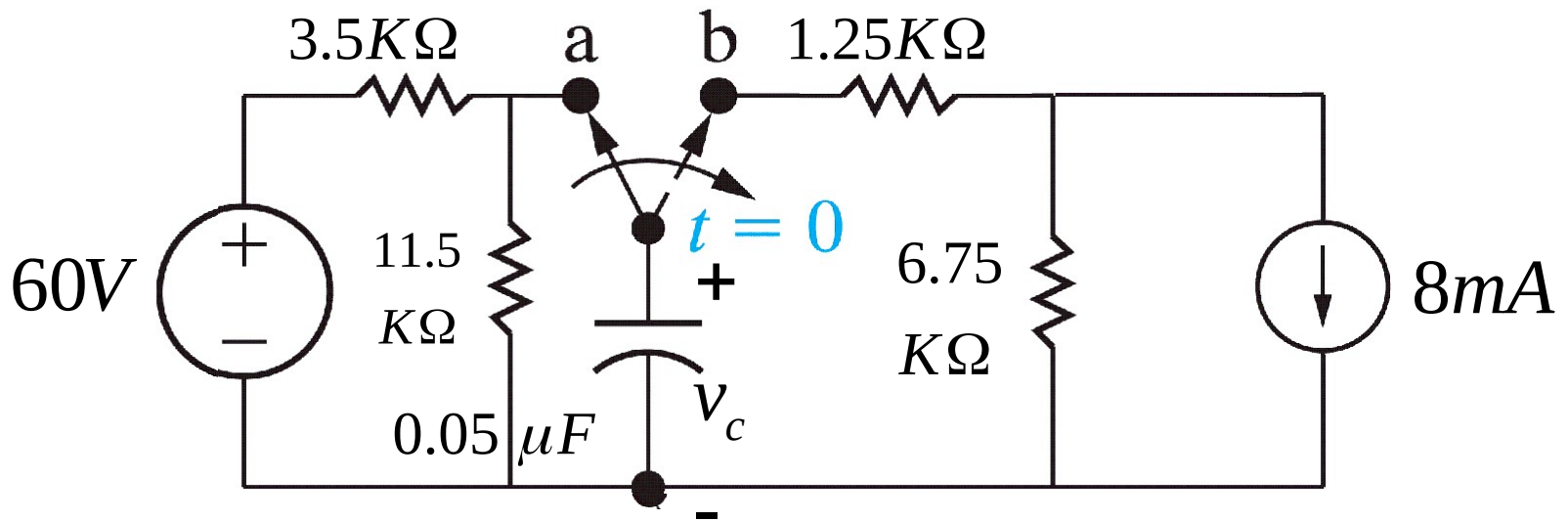

a) $t < 0$ Steady State; Capacitor is Open

Note V_c can't change Instantly


Initial Voltage

$$v_c(0^-) = v_c(0) = V_{11.5K\Omega} = 60 \frac{11.5K\Omega}{(3.5 + 11.5)K\Omega} \left. \vphantom{\frac{11.5K\Omega}{(3.5 + 11.5)K\Omega}} \right\} \text{Voltage Division}$$

$$v_c(0) = 46(V)$$

Example (Contd.)

b) Find $v_c(t)$ $t \geq 0$

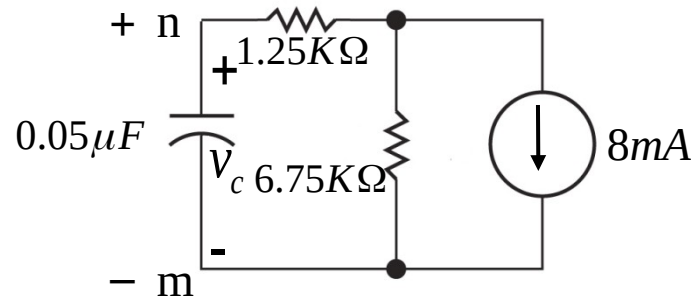

Find Norton Equivalent between n and m

$$R_{Th} = (1.25 + 6.75)K = 8K$$


Add series resistor

$$V_{Th} = -8mA(6.75K\Omega) = -54(V)$$

Ohm's Law

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{-54(V)}{8(K\Omega)} = -6.75(mA)$$

Short Circuit Current

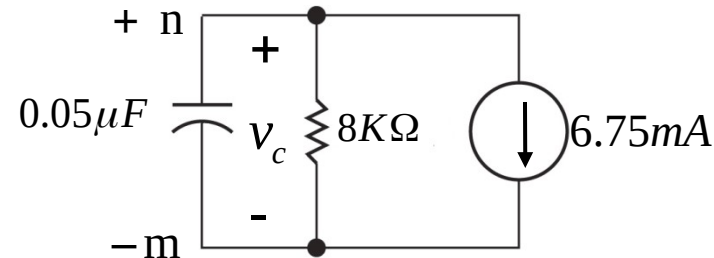

Norton Equivalent

$$v_{c(final)} = -(6.75mA)(8K\Omega) = -54(V)$$

Capacitor is open in steady state

$$\text{c) } \tau = R_{Th}C = 8K\Omega(0.05\mu F) \quad \tau = 400(\mu s)$$

Find time constant

Example (Contd.)

d) General Solution

$$v_c(t) = v_{c(final)} + \left[v_c(t_0) - v_{c(final)} \right] e^{-\frac{(t-t_0)}{\tau}}$$

Note
 $t_0 = 0$

$$\begin{aligned} \therefore v_c(t) &= -54 + \left[46 - (-54) \right] e^{-\frac{t}{400\mu s}} \text{ (V)} \\ &= -54 + 100e^{-2500t} \text{ (V)} \end{aligned}$$

**Plug in values
then simplify**

How long until $v_c(t) = 0$?

$$100e^{-2500t} = 54 \quad \left\{ \begin{array}{l} \text{Plug in } v_c(t)=0 \text{ and solve for } t \end{array} \right.$$

$$\therefore t = \frac{1}{2500} \ln \left(\frac{100}{54} \right) \Rightarrow t = 246.47(\mu s)$$

Side Note

$$v_c(0) = +46(V)$$

$$v_c(\infty) = -54(V)$$


$\therefore v_c(t)$ **Crosses
Time Axis**

Sequential Switching

When Switching Occurs More Than Once
Must Find Initial Values at each event, we then
solve for

- Inductive Currents
- Capacitive Voltages

Example: Find $v_c(t)$

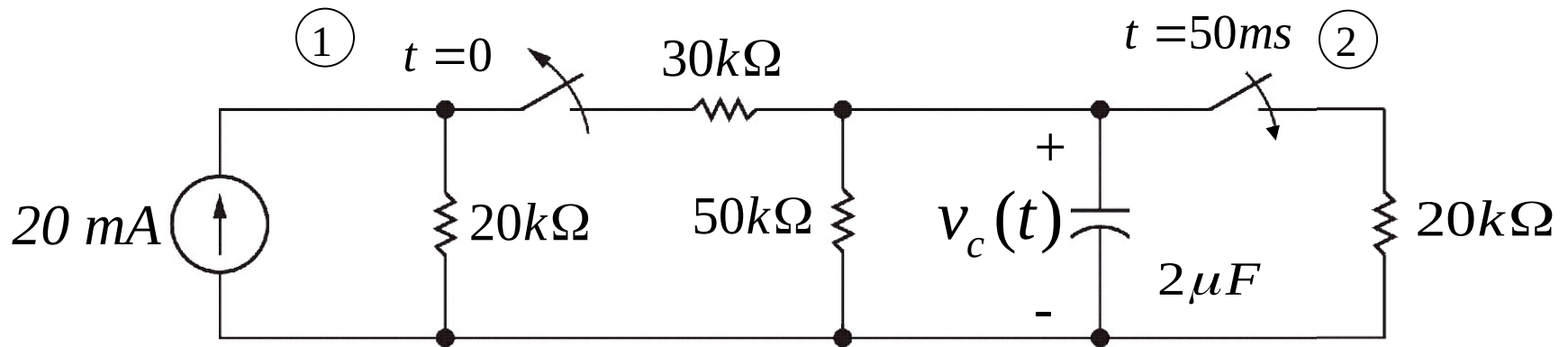


Switch 1 Has Been Closed
Switch 2 Has Been Open

}

Long Time

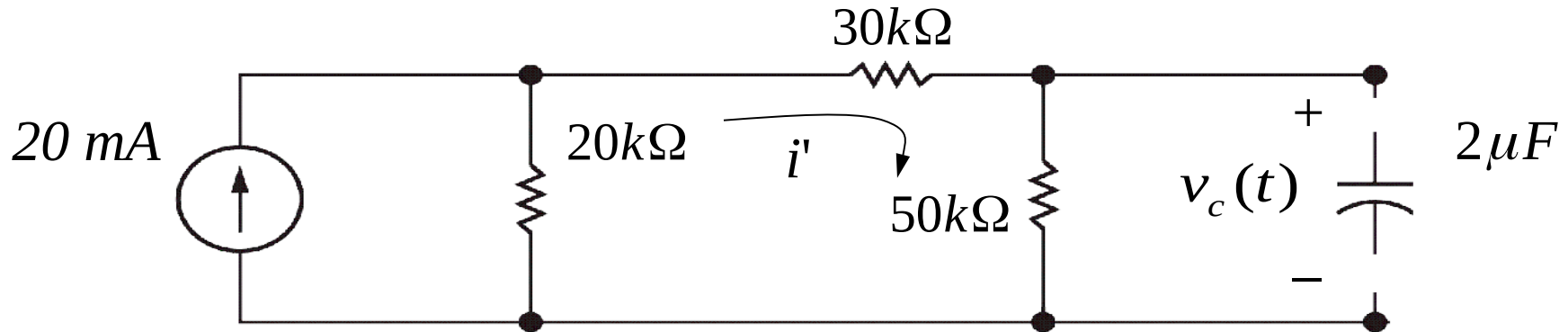Example (Contd.) For $t < 0$ Redraw Circuit



Capacitor is Open in Steady State

$$v_c(0^-) \equiv v_c(0) = v_{50K\Omega}(0^-) \left\{ \begin{array}{l} \text{Voltage can't be changed} \\ \text{Instantly across capacitor} \end{array} \right.$$


$$i' = 20\text{ mA} \frac{20\text{ K}\Omega}{(20 + 30 + 50)\text{ K}\Omega} = 4(\text{mA}) \left\{ \begin{array}{l} \text{Current Division} \end{array} \right.$$

$$v_c(0^-) = 50\text{ K}\Omega(i') = 50\text{ K}(4\text{ mA}) \left\{ \begin{array}{l} \text{Ohm's Law} \end{array} \right.$$

$$v_c(0) = 200(\text{V})$$

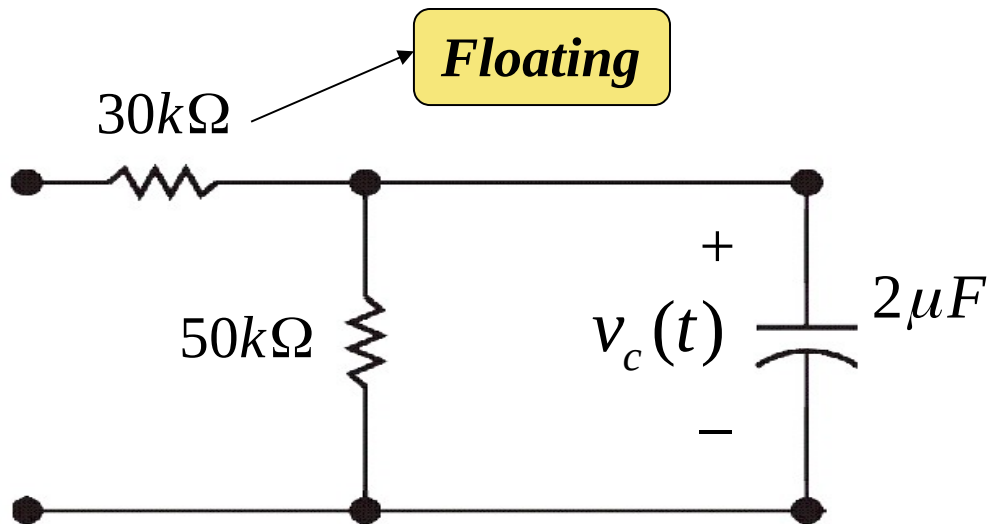Example: Find $v_c(t)$

For $0 \leq t < 50(ms)$, $v_c(0) = 200$ Switch 1 Opens



Find Time Constant

$$\tau = RC = 50K\Omega(2\mu F)$$

$$\tau = 0.1s$$

30KΩ Not Involved

Use the Natural Response formula

$$v_c(t) = v_c(0)e^{-t/\tau} = 200e^{-t/0.1}$$

$$v_c(t) = 200e^{-10(t)}(V)$$

$$0 \leq t < 50ms$$


Example (Contd.)

b) $t \geq 50ms$, Switch 2 Closes

$$v_c(t) = 200e^{-10t} \text{ for } 0 \leq t \leq 50ms$$

$$v_c(50ms) = 200e^{-10(50ms)} \left. \vphantom{v_c(50ms)} \right\} \longrightarrow$$

$$v_c(50ms) = 121.31(V)$$

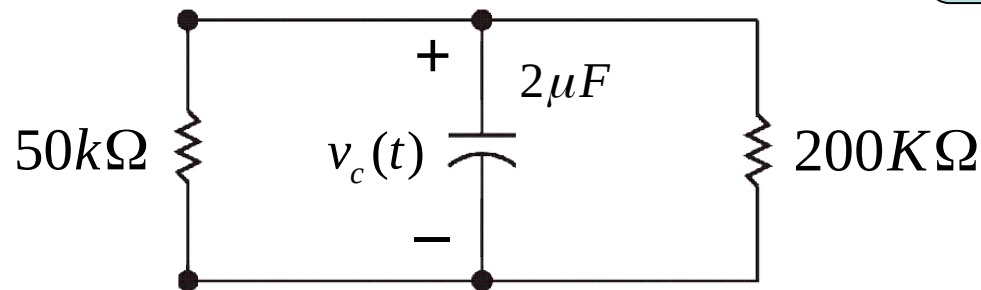

$$R_{eq} = 50K \parallel 200K = 40(K\Omega)$$

$$\tau = R_{eq} C = 40K\Omega(2\mu F) = 80(ms)$$

$$v_c(t) = v_{c(50ms)} e^{-\frac{(t-t_0)}{\tau}} = 121.31e^{-\frac{(t-50ms)}{80ms}} \left. \vphantom{v_c(t)} \right\}$$

**Use the
Natural Response formula
Note $t_0 = 50ms$**

$$v_c(t) = 121.31e^{-12.5(t-0.05)}(V) \quad t \geq 50ms$$