

The results are a close match with those of Example 4 with $I_C = 2.217 \text{ mA}$, $V_B = 2.636 \text{ V}$, $V_C = 15.557 \text{ V}$, and $V_E = 2.26 \text{ V}$.

The relatively few comments required here to permit the analysis of transistor networks is a clear indication that the breadth of analysis using Multisim can be expanded dramatically without having to learn a whole new set of rules—a very welcome characteristic of most technology software packages.

PROBLEMS

*Note: Asterisks indicate more difficult problems.

3 Fixed-Bias Configuration

1. For the fixed-bias configuration of Fig. 118, determine:

- a. I_{BQ}
- b. I_{CQ}
- c. V_{CEQ}
- d. V_C
- e. V_B
- f. V_E

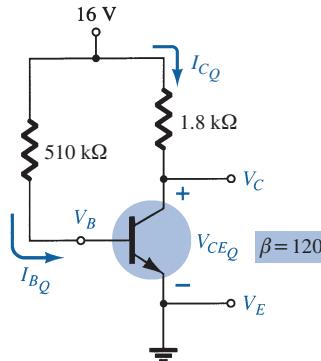


FIG. 118

Problems 1, 4, 6, 7, 14, 65, 69, 71, and 75.

2. Given the information appearing in Fig. 119, determine:

- a. I_C
- b. R_C
- c. R_B
- d. V_{CE}

3. Given the information appearing in Fig. 120, determine:

- a. I_C
- b. V_{CC}
- c. β
- d. R_B

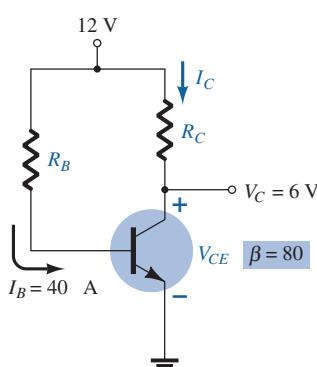


FIG. 119

Problem 2.

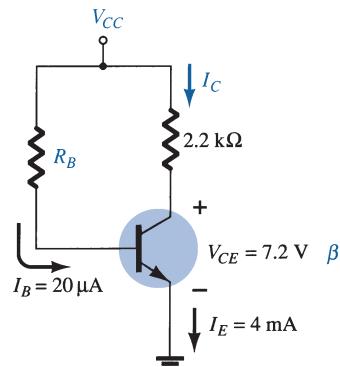


FIG. 120

Problem 3.

4. Find the saturation current ($I_{C_{sat}}$) for the fixed-bias configuration of Fig. 118.
- *5. Given the BJT transistor characteristics of Fig. 121:
- Draw a load line on the characteristics determined by $E = 21\text{ V}$ and $R_C = 3\text{ k}\Omega$ for a fixed-bias configuration.
 - Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point.
 - What are the resulting values of I_{C_Q} and V_{CE_Q} ?
 - What is the value of β at the operating point?
 - What is the value of α defined by the operating point?
 - What is the saturation current ($I_{C_{sat}}$) for the design?
 - Sketch the resulting fixed-bias configuration.
 - What is the dc power dissipated by the device at the operating point?
 - What is the power supplied by V_{CC} ?
 - Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).

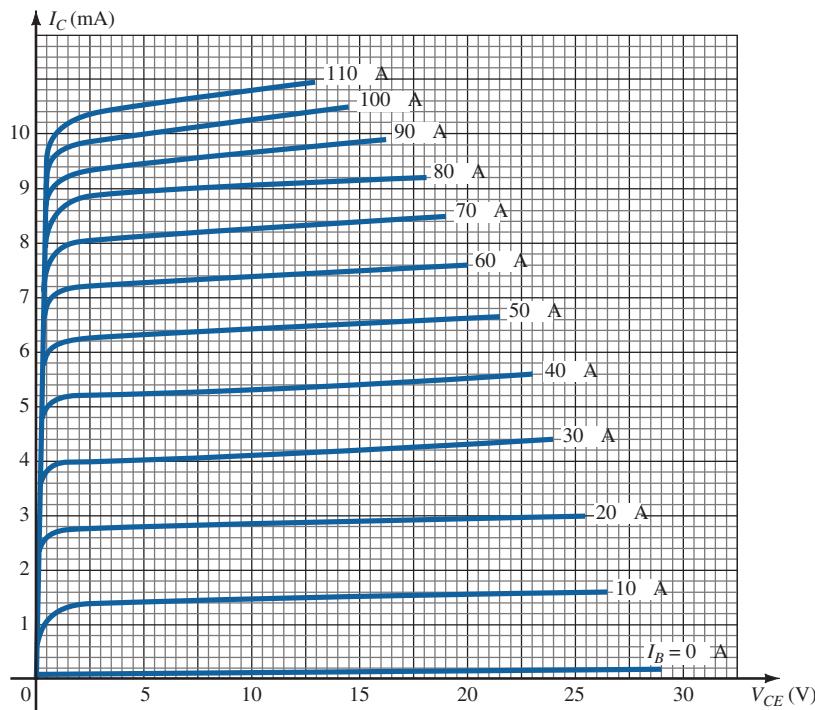


FIG. 121
Problems 5, 6, 9, 13, 24, 44, and 57.

6. a. Ignoring the provided value of $\beta_{(120)}$ draw the load line for the network of Fig. 118 on the characteristics of Fig. 121.
 b. Find the Q -point and the resulting I_{C_Q} and V_{CE_Q} .
 c. What is the beta value at this Q -point?
 7. If the base resistor of Fig. 118 is increased to $910\text{ k}\Omega$, find the new Q -point and resulting values of I_{C_Q} and V_{CE_Q} .

4 Emitter-Bias Configuration

8. For the emitter-stabilized bias circuit of Fig. 122, determine:
- I_{B_Q} .
 - I_{C_Q} .
 - V_{CE_Q} .
 - V_C .
 - V_B .
 - V_E .

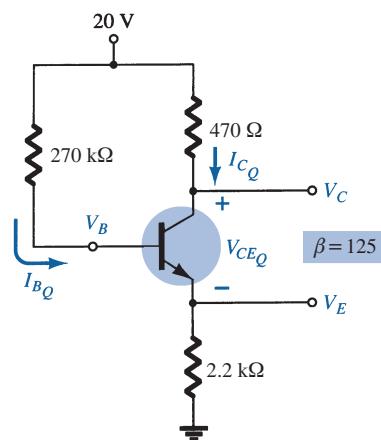


FIG. 122

Problems 8, 9, 12, 14, 66, 69, 72, and 76.

9. a. Draw the load line for the network of Fig. 122 on the characteristics of Fig. 121 using β from problem 8 to find I_{BQ} .
b. Find the Q -point and resulting values I_{CQ} and V_{CEQ} .
c. Find the value of β at the Q -point.
d. How does the value of part (c) compare with $\beta = 125$ in problem 8?
e. Why are the results for problem 9 different from those of problem 8?
10. Given the information provided in Fig. 123, determine:
 - a. R_C .
 - b. R_E .
 - c. R_B .
 - d. V_{CE} .
 - e. V_B .
11. Given the information provided in Fig. 124, determine:
 - a. β .
 - b. V_{CC} .
 - c. R_B .

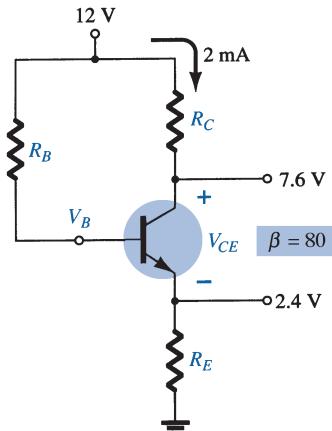


FIG. 123

Problem 10.

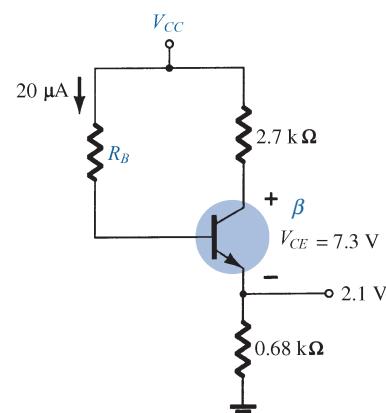


FIG. 124

Problem 11.

12. Determine the saturation current ($I_{C_{sat}}$) for the network of Fig. 122.
- *13. Using the characteristics of Fig. 121, determine the following for an emitter-bias configuration if a Q -point is defined at $I_{CQ} = 4 \text{ mA}$ and $V_{CEQ} = 10 \text{ V}$.
 - a. R_C if $V_{CC} = 24 \text{ V}$ and $R_E = 1.2 \text{ k}\Omega$.
 - b. β at the operating point.
 - c. R_B .
 - d. Power dissipated by the transistor.
 - e. Power dissipated by the resistor R_C .

- *14. a. Determine I_C and V_{CE} for the network of Fig. 118.
 b. Change β to 180 and determine the new value of I_C and V_{CE} for the network of Fig. 118.
 c. Determine the magnitude of the percentage change in I_C and V_{CE} using the following equations:

$$\% \Delta I_C = \left| \frac{I_{C(\text{part b})} - I_{C(\text{part a})}}{I_{C(\text{part a})}} \right| \times 100\%, \quad \% \Delta V_{CE} = \left| \frac{V_{CE(\text{part b})} - V_{CE(\text{part a})}}{V_{CE(\text{part a})}} \right| \times 100\%$$

- d. Determine I_C and V_{CE} for the network of Fig. 122.
 e. Change β to 187.5 and determine the new value of I_C and V_{CE} for the network of Fig. 122.
 f. Determine the magnitude of the percentage change in I_C and V_{CE} using the following equations:

$$\% \Delta I_C = \left| \frac{I_{C(\text{part c})} - I_{C(\text{part d})}}{I_{C(\text{part d})}} \right| \times 100\%, \quad \% \Delta V_{CE} = \left| \frac{V_{CE(\text{part c})} - V_{CE(\text{part d})}}{V_{CE(\text{part d})}} \right| \times 100\%$$

- g. In each of the above, the magnitude of β was increased 50%. Compare the percentage change in I_C and V_{CE} for each configuration, and comment on which seems to be less sensitive to changes in β .

5 Voltage-Divider Bias Configuration

15. For the voltage-divider bias configuration of Fig. 125, determine:
 a. I_{BQ} .
 b. I_{CQ} .
 c. V_{CEQ} .
 d. V_C .
 e. V_E .
 f. V_B .
16. a. Repeat problem 15 for $\beta = 140$ using the general approach (not the approximate).
 b. What levels are affected the most? Why?
17. Given the information provided in Fig. 126, determine:
 a. I_C .
 b. V_E .
 c. V_B .
 d. R_1 .

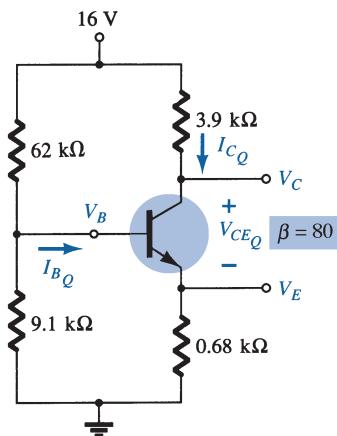


FIG. 125

Problems 15, 16, 20, 23, 25, 67,
 69, 70, 73, and 77.

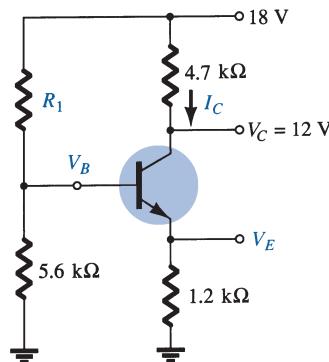


FIG. 126

Problems 17 and 19.

18. Given the information appearing in Fig. 127, determine:
 a. I_C .
 b. V_E .
 c. V_{CC} .
 d. V_{CE} .
 e. V_B .
 f. R_1 .

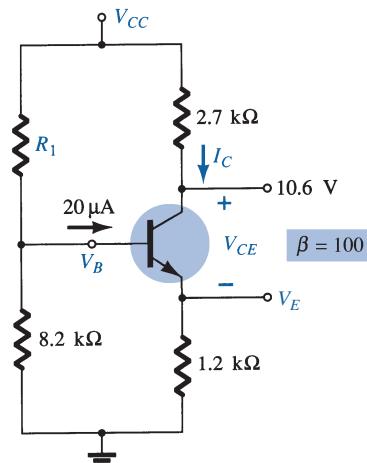


FIG. 127

Problem 18.

19. Determine the saturation current ($I_{C_{\text{sat}}}$) for the network of Fig. 126.
20. a. Repeat problem 16 with $\beta = 140$ using the approximate approach and compare results.
b. Is the approximate approach valid?
- *21. Determine the following for the voltage-divider configuration of Fig. 128 using the approximate approach if the condition established by Eq. (33) is satisfied.
 - a. I_C .
 - b. V_{CE} .
 - c. I_B .
 - d. V_E .
 - e. V_B .

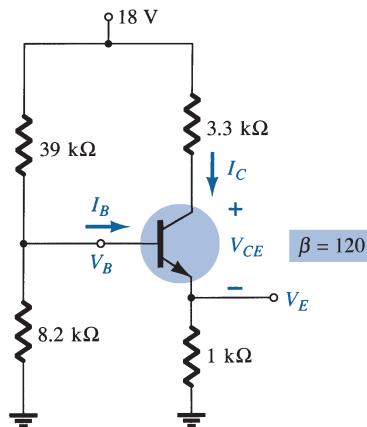


FIG. 128

Problems 21, 22, and 26.

- *22. Repeat Problem 21 using the exact (Thévenin) approach and compare solutions. Based on the results, is the approximate approach a valid analysis technique if Eq. (33) is satisfied?
23. a. Determine I_{C_Q} , V_{CE_Q} , and I_{B_Q} for the network of Problem 15 (Fig. 125) using the approximate approach even though the condition established by Eq. (33) is not satisfied.
b. Determine I_{C_Q} , V_{CE_Q} , and I_{B_Q} using the exact approach.
c. Compare solutions and comment on whether the difference is sufficiently large to require standing by Eq. (33) when determining which approach to employ.
- *24. a. Using the characteristics of Fig. 121, determine R_C and R_E for a voltage-divider network having a Q -point of $I_{C_Q} = 5 \text{ mA}$ and $V_{CE_Q} = 8 \text{ V}$. Use $V_{CC} = 24 \text{ V}$ and $R_C = 3R_E$.
b. Find V_E .
c. Determine V_B .
d. Find R_2 if $R_1 = 24 \text{ k}\Omega$ assuming that $\beta R_E > 10R_2$.
e. Calculate β at the Q -point.
f. Test Eq. (33), and note whether the assumption of part (d) is correct.

- *25. a. Determine I_C and V_{CE} for the network of Fig. 125.
 b. Change β to 120 (50% increase), and determine the new values of I_C and V_{CE} for the network of Fig. 125.
 c. Determine the magnitude of the percentage change in I_C and V_{CE} using the following equations:

$$\% \Delta I_C = \left| \frac{I_{C(\text{part b})} - I_{C(\text{part a})}}{I_{C(\text{part a})}} \right| \times 100\%, \quad \% \Delta V_{CE} = \left| \frac{V_{CE(\text{part b})} - V_{CE(\text{part a})}}{V_{CE(\text{part a})}} \right| \times 100\%$$

- d. Compare the solution to part (c) with the solutions obtained for parts (c) and (f) of Problem 14.
 e. Based on the results of part (d), which configuration is least sensitive to variations in β ?
 *26. a. Repeat parts (a) through (e) of Problem 25 for the network of Fig. 128. Change β to 180 in part (b).
 b. What general conclusions can be made about networks in which the condition $\beta R_E > 10R_2$ is satisfied and the quantities I_C and V_{CE} are to be determined in response to a change in β ?

6 Collector-Feedback Configuration

27. For the collector-feedback configuration of Fig. 129, determine:

- I_B .
- I_C .
- V_C .

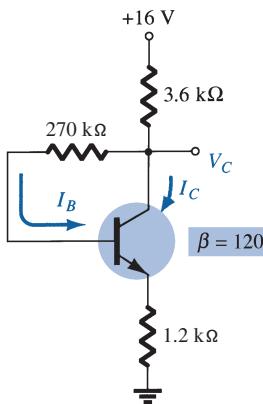


FIG. 129

Problems 27, 28, 74, and 78.

28. For the network of problem 27

- Determine I_{C_Q} using the equation $I_{C_Q} \cong \frac{V'}{R'} = \frac{V_{CC} - V_{BE}}{R_C + R_E}$
- Compare with the results of problem 27 for I_{C_Q} .
- Compare R' to $R_{F/\beta}$.
- Is the statement valid that the larger R' is compared with $R_{F/\beta}$, the more accurate the equation $I_{C_Q} \cong \frac{V'}{R'}$? Prove using a short derivation for the exact current I_{C_Q} .
- Repeat parts (a) and (b) for $\beta = 240$ and comment on the new level of I_{C_Q} .

29. For the voltage feedback network of Fig. 130, determine:

- I_C .
- V_C .
- V_E .
- V_{CE} .

30. a. Compare levels of $R' = R_C + R_E$ to $R_{F/\beta}$ for the network of Fig. 131.
 b. Is the approximation $I_{C_Q} \cong V'/R'$ valid?

- *31. a. Determine the levels of I_C and V_{CE} for the network of Fig. 131.
 b. Change β to 135 (50% increase), and calculate the new levels of I_C and V_{CE} .
 c. Determine the magnitude of the percentage change in I_C and V_{CE} using the following equations:

$$\% \Delta I_C = \left| \frac{I_{C(\text{part b})} - I_{C(\text{part a})}}{I_{C(\text{part a})}} \right| \times 100\%, \quad \% \Delta V_{CE} = \left| \frac{V_{CE(\text{part b})} - V_{CE(\text{part a})}}{V_{CE(\text{part a})}} \right| \times 100\%$$

- d. Compare the results of part (c) with those of Problems 14(c), 14(f), and 25(c). How does the collector-feedback network stack up against the other configurations in sensitivity to changes in β ?

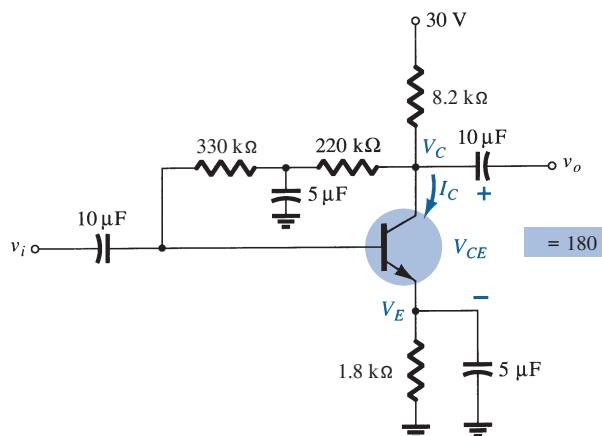


FIG. 130
Problems 29 and 30.

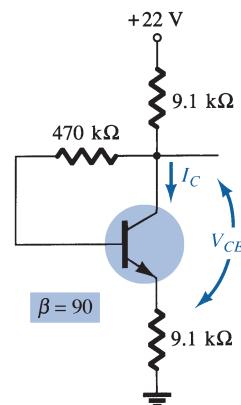


FIG. 131
Problems 30 and 31.

32. Determine the range of possible values for V_C for the network of Fig. 132 using the $1\text{-M}\Omega$ potentiometer.

*33. Given $V_B = 4\text{ V}$ for the network of Fig. 133, determine:

- V_E .
- I_C .
- V_C .
- V_{CE} .
- I_B .
- β .

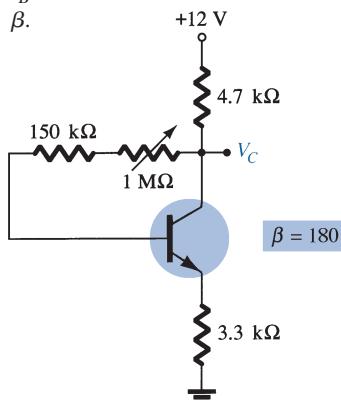


FIG. 132
Problem 32.

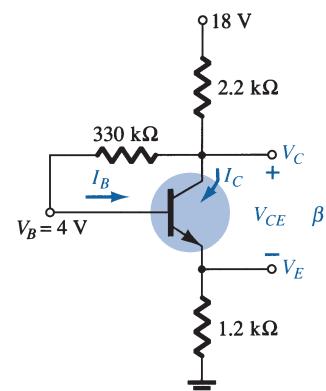


FIG. 133
Problem 33.

7 Emitter-Follower Configuration

*34. Determine the level of V_E and I_E for the network of Fig. 134.

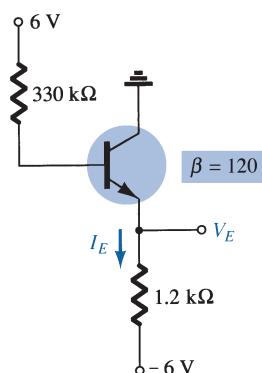


FIG. 134
Problem 34.

35. For the emitter follower network of Fig. 135

- Find I_B , I_C , and I_E .
- Determine V_B , V_C , and V_E .
- Calculate V_{BC} and V_{CE} .

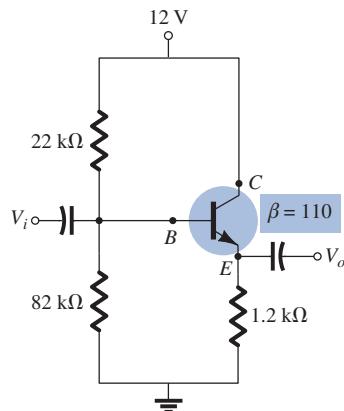


FIG. 135
Problem 35.

8 Common-Base Configuration

*36. For the network of Fig. 136, determine:

- I_B .
- I_C .
- V_{CE} .
- V_C .

*37. For the network of Fig. 137, determine:

- I_E .
- V_C .
- V_{CE} .

38. For the common-base network of Fig. 138

- Using the information provided determine the value of R_C .
- Find the currents I_B and I_E .
- Determine the voltages V_{BC} and V_{CE} .

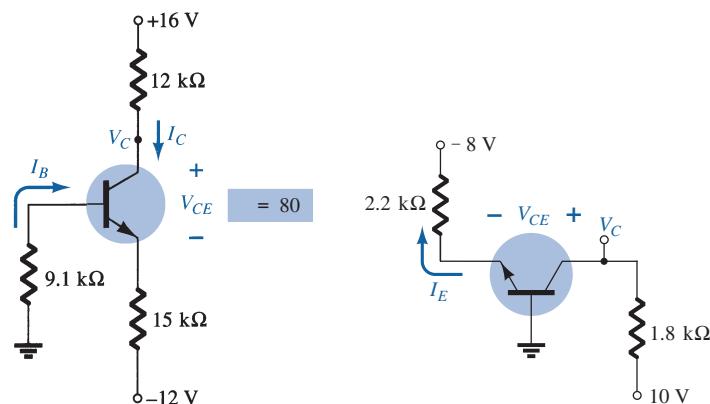


FIG. 136
Problem 36.

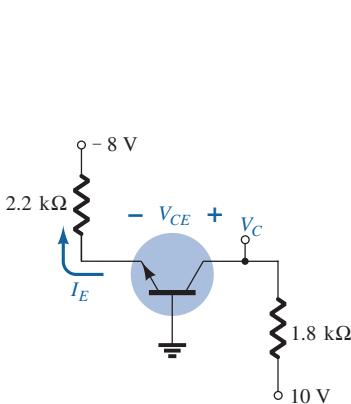


FIG. 137
Problem 37.

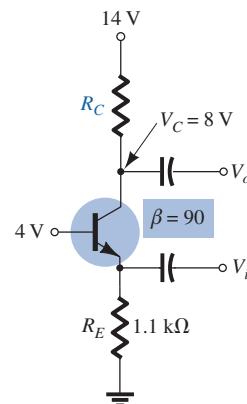


FIG. 138
Problem 38.

9 Miscellaneous Bias Configurations

*39. For the network of Fig. 139, determine:

- I_B .
- I_C .
- V_E .
- V_{CE} .

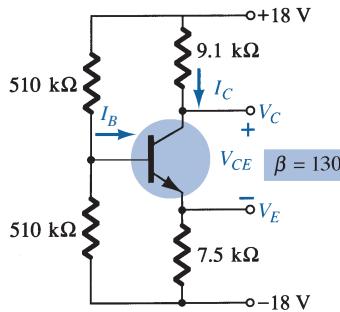


FIG. 139
Problem 39.

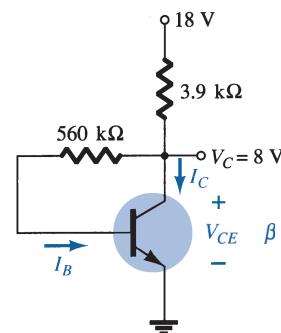


FIG. 140
Problems 40 and 68.

40. Given $V_C = 8\text{ V}$ for the network of Fig. 140, determine:

- I_B .
- I_C .
- β .
- V_{CE} .

11 Design Operations

- Determine R_C and R_B for a fixed-bias configuration if $V_{CC} = 12\text{ V}$, $\beta = 80$, and $I_{CQ} = 2.5\text{ mA}$ with $V_{CEQ} = 6\text{ V}$. Use standard values.
- Design an emitter-stabilized network at $I_{CQ} = \frac{1}{2}I_{C\text{sat}}$ and $V_{CEQ} = \frac{1}{2}V_{CC}$. Use $V_{CC} = 20\text{ V}$, $I_{C\text{sat}} = 10\text{ mA}$, $\beta = 120$, and $R_C = 4R_E$. Use standard values.
- Design a voltage-divider bias network using a supply of 24 V , a transistor with a beta of 110 , and an operating point of $I_{CQ} = 4\text{ mA}$ and $V_{CEQ} = 8\text{ V}$. Choose $V_E = \frac{1}{8}V_{CC}$. Use standard values.
- *44. Using the characteristics of Fig. 121, design a voltage-divider configuration to have a saturation level of 10 mA and a Q -point one-half the distance between cutoff and saturation. The available supply is 28 V , and V_E is to be one-fifth of V_{CC} . The condition established by Eq. (33) should also be met to provide a high stability factor. Use standard values.

12 Multiple BJT Networks

45. For the $R-C$ -coupled amplifier of Fig. 141 determine
- the voltages V_B , V_C , and V_E for each transistor.
 - the currents I_B , I_C , and I_E for each transistor

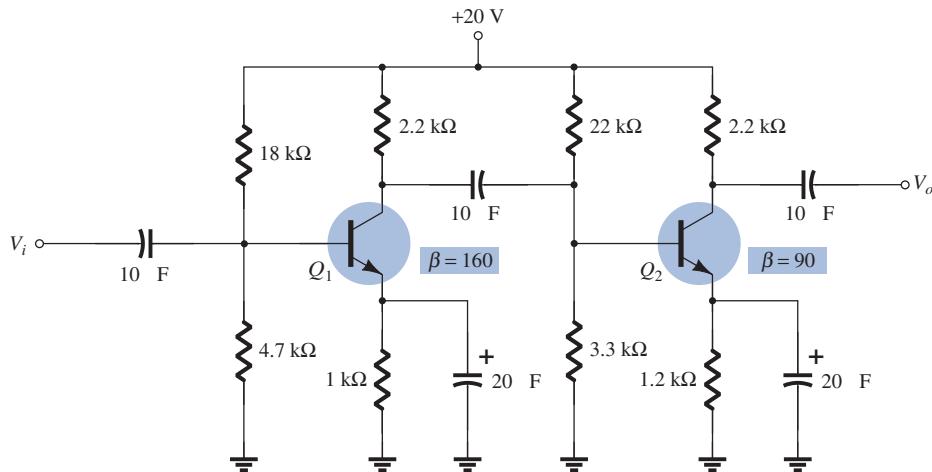


FIG. 141
Problem 45.

46. For the Darlington amplifier of Fig. 142 determine
- the level of β_D .
 - the base current of each transistor.
 - the collector current of each transistor.
 - the voltages V_{C_1} , V_{C_2} , V_{E_1} , and V_{E_2} .