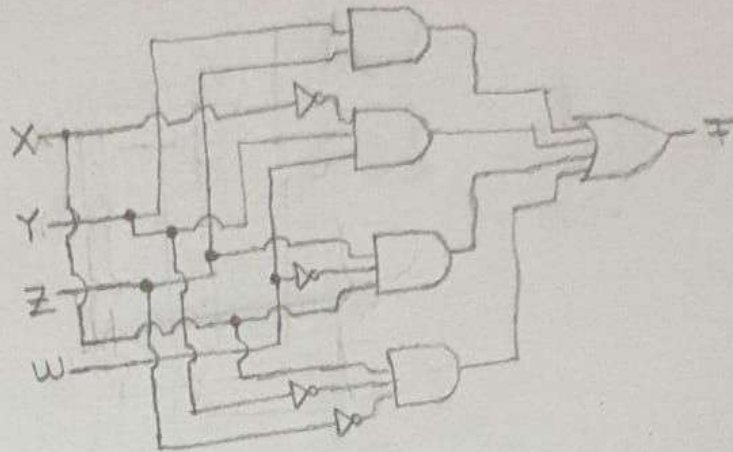


1) A)

X\YZW	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	0	0	1	1
10	1	1	0	1

K-map for F function



$$F = YZ + \bar{X}YW + XZ\bar{W} + X\bar{Y}\bar{Z}$$



1) B)

X	Y	Z	W	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


Truth Table for F function

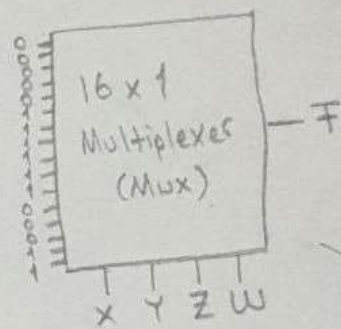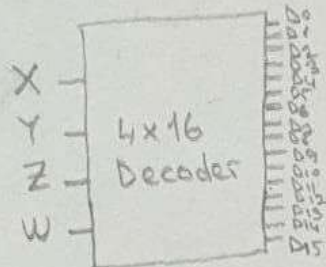

This belongs to question 1) C)


It is continuing on the other page ...

1) B)

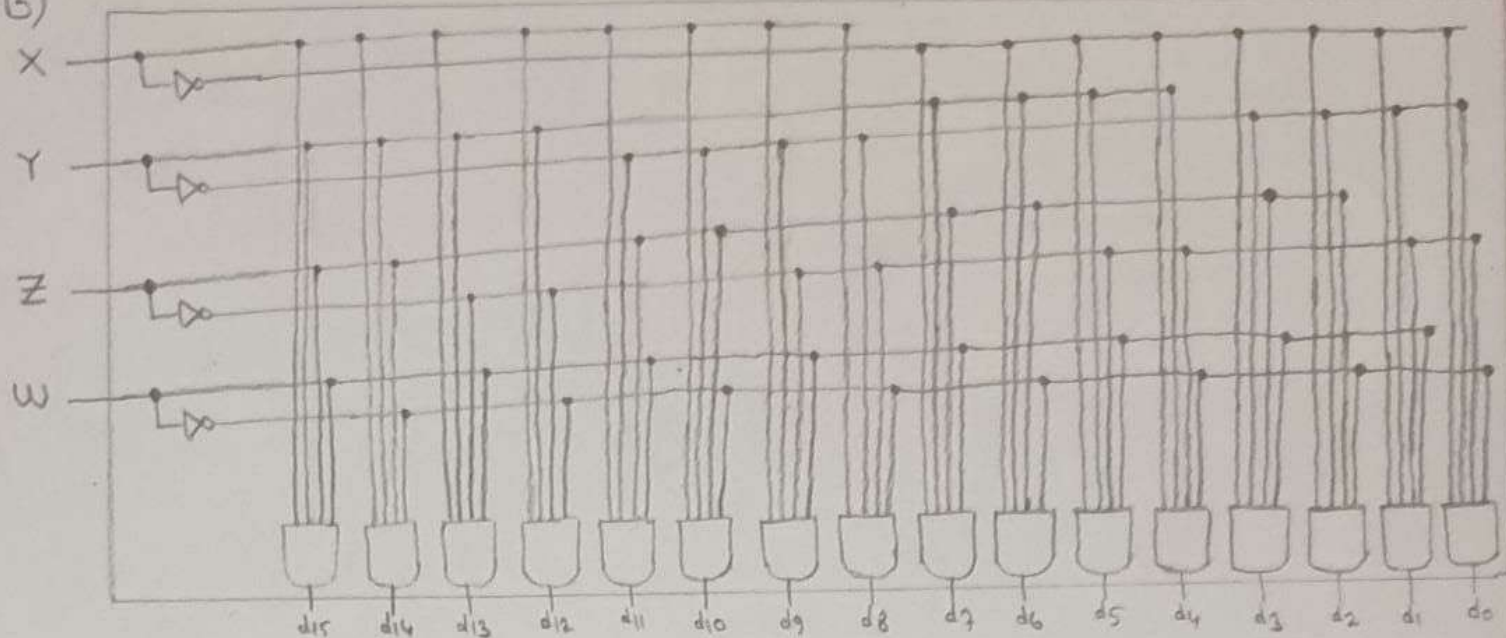

Decoder

1) C

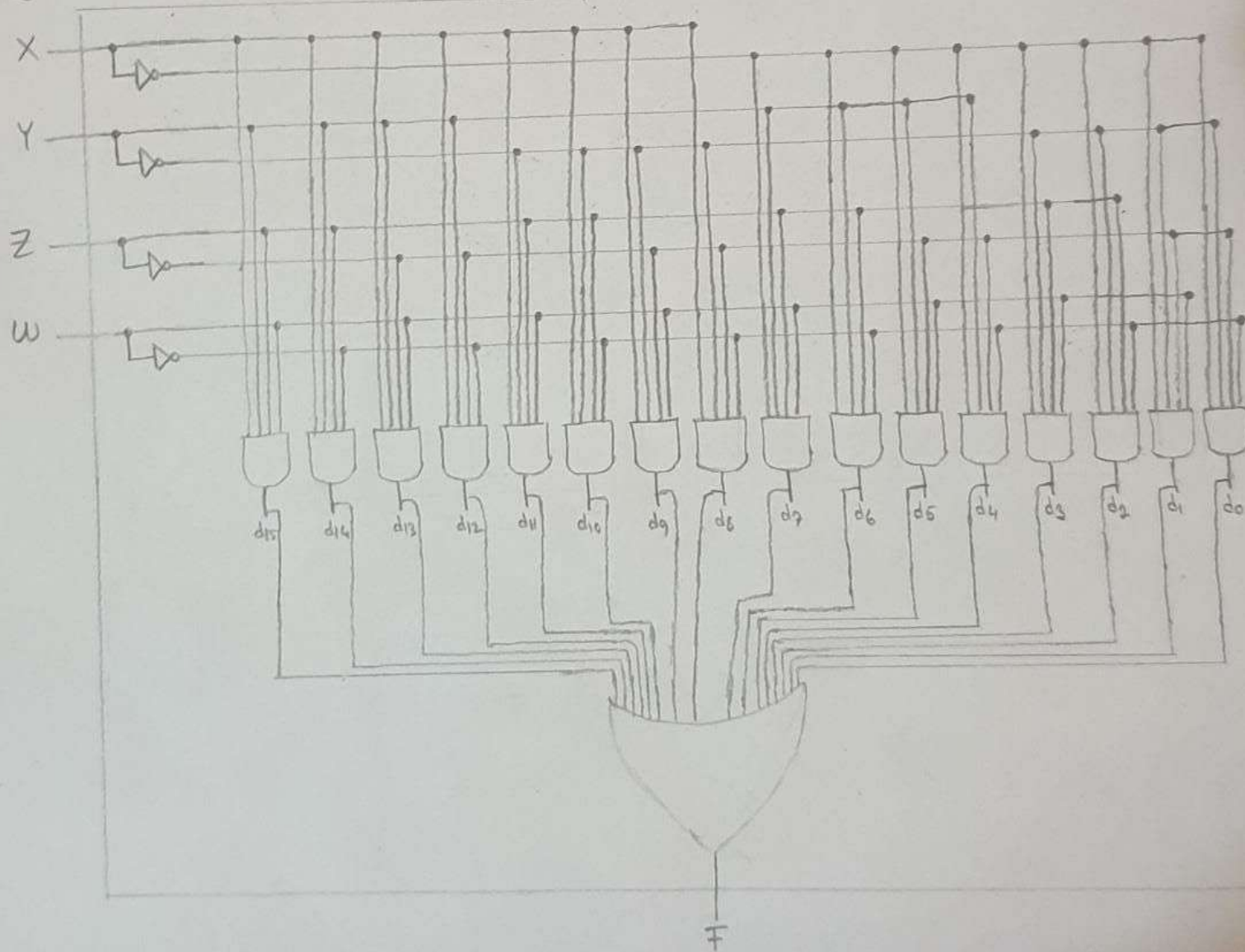

Multiplexer

2) A)

X	Y	Z	L
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Truth table

X \ YZ	00	01	11	10
0	1 ₂	1 ₁	0 ₃	1 ₂
1	0 ₄	0 ₃	0 ₃	0 ₆


$$L = \bar{X}\bar{Y} + \bar{X}\bar{Z}$$

$$L = \bar{X}\bar{Y}(Z + \bar{Z}) + \bar{X}\bar{Z}(Y + \bar{Y})$$

$$L = \bar{X}\bar{Y}Z + \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Z}Y + \bar{X}\bar{Z}\bar{Y}$$

$$\text{Canonical form} = \bar{X}\bar{Y}Z + \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Z}Y + \bar{X}\bar{Z}\bar{Y}$$

↓ circuit

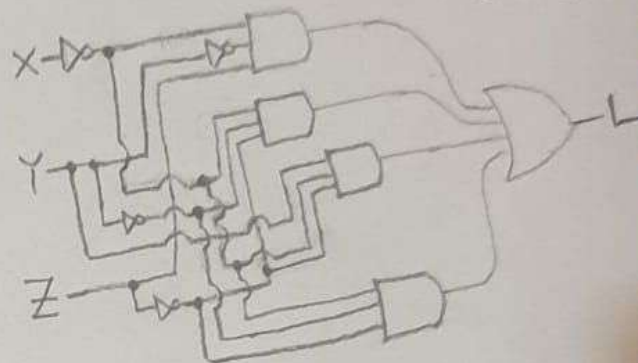


2) B)

$$L = \bar{X}\bar{Y} + \bar{X}\bar{Z}$$


$$\bar{L} = \overline{\bar{X}\bar{Y} + \bar{X}\bar{Z}}$$
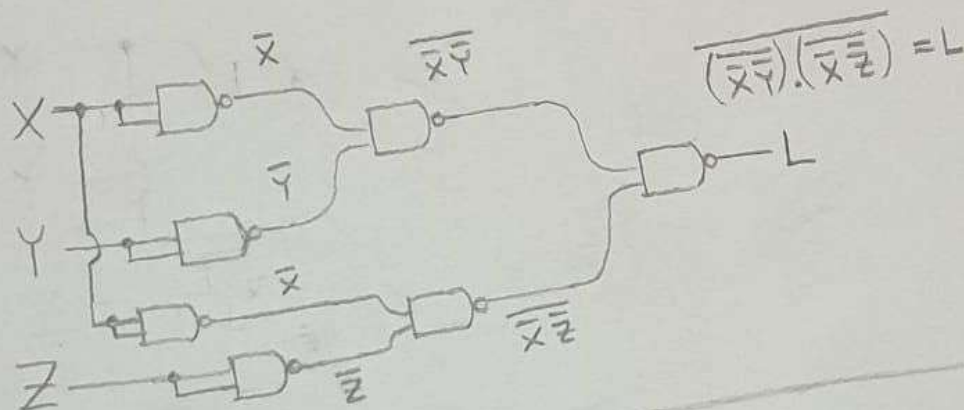
$$\bar{L} = (\overline{\bar{X}\bar{Y}}) \cdot (\overline{\bar{X}\bar{Z}}) = L$$




2) C) $L = \bar{X}\bar{Y} + \bar{X}\bar{Z}$

AND gate

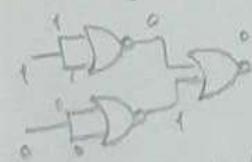

OR gate


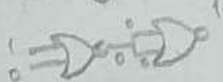


Truth table is valid. It is tested.


NOR truth table

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Inverter

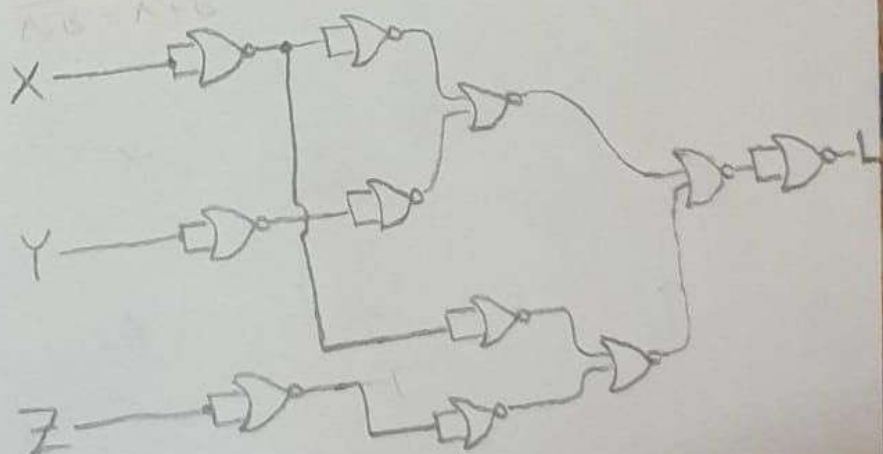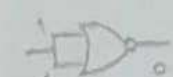

3)

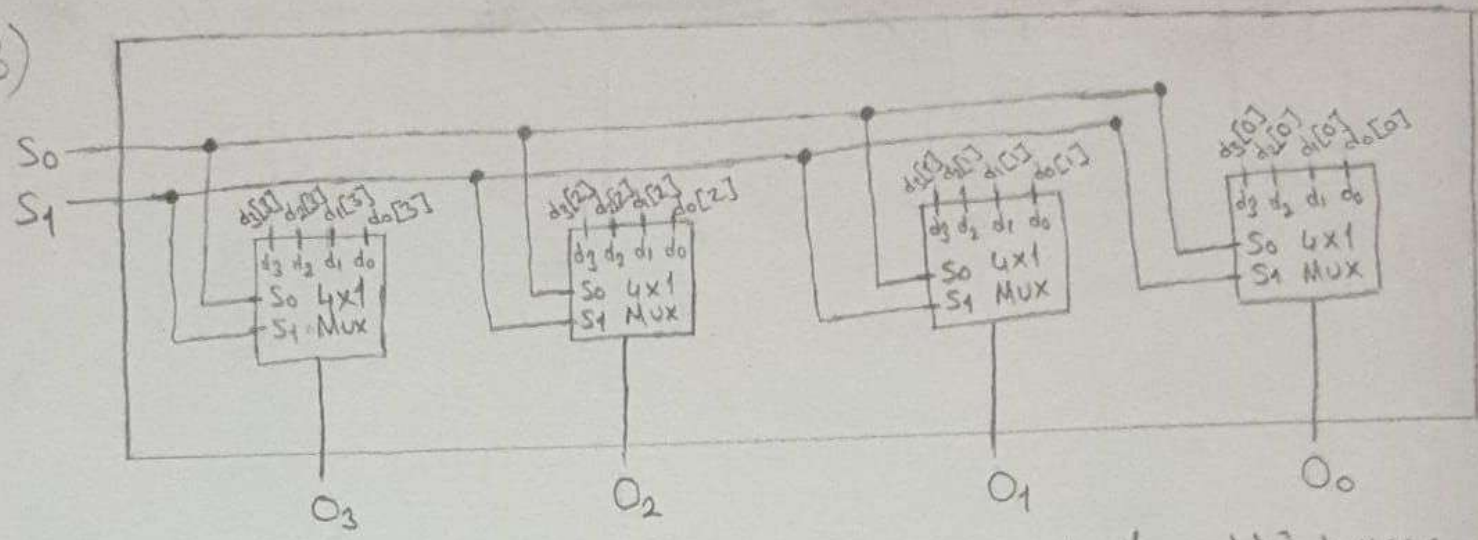

It is a 4-bit 4x1 multiplexer that uses four 4x1 multiplexers.