


Sinusoidal Steady-State

Week 8-9

Brief Summary

- **AC Instead of DC.**
- **Sinusoidal Inputs Instead of Constant Inputs.**
- **Can Still Use Techniques we have previously learned.**
- **Need to Use Complex Numbers**
- **Everything Else is Almost the Same**

Sinusoidal Sources

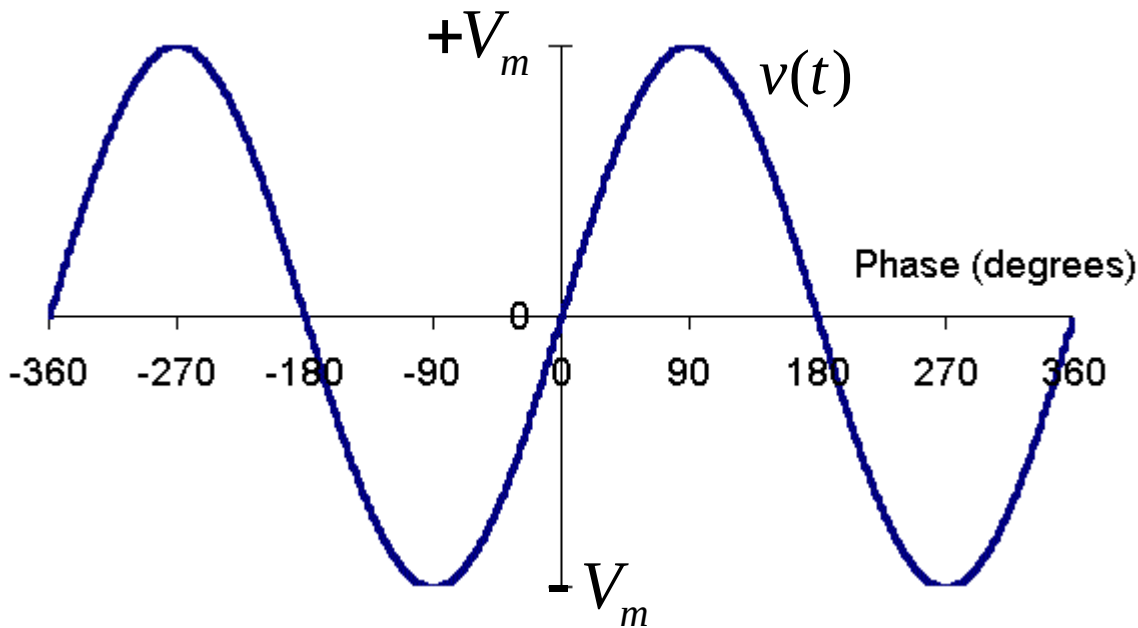

$V_m \equiv$ Magnitude {sine varies between -1 and 1}

t = time (in seconds)

ω = Angular Frequency (in rad / s)

T = Period (in seconds)

f = frequency (in $cycles / sec \equiv Hertz$)

**Sine Wave
Periodic Function**

**Repeats every 360° or
 2π rads or T sec**

For a 60Hz sine wave,

$$T = \frac{1}{60} \text{ sec}$$

$$v(t) = V_m \sin(\omega t)$$

$$\omega = 2\pi f = \frac{2\pi}{T} \text{ (rad/s)}$$

$$f = \frac{1}{T} \text{ (cycles/s)}$$

ωt is in radians

Degree/Radian Conversions

$$\left. \frac{Deg}{360^\circ} = \frac{rad}{2\pi} \right\} \text{Fundamental}$$

$$\text{OR} \quad rad = \left(\frac{Deg}{360} \right) 2\pi$$

$$\text{OR} \quad rad = \frac{Deg}{180} \cdot \pi \quad \left. \right\} \text{Standard Equation}$$

Examples

$$2\pi \text{ radians} = 360^\circ$$

$$\pi \text{ radians} = 180^\circ$$


General Form of Sine Wave

$$v(t) = V_m \sin(\omega t + \phi)$$

ϕ often given in Degrees, but must be converted to Radians.

$\phi \equiv$ Phase Angle

e.g. $v(t) = V_m \sin(5t + 30^\circ)$

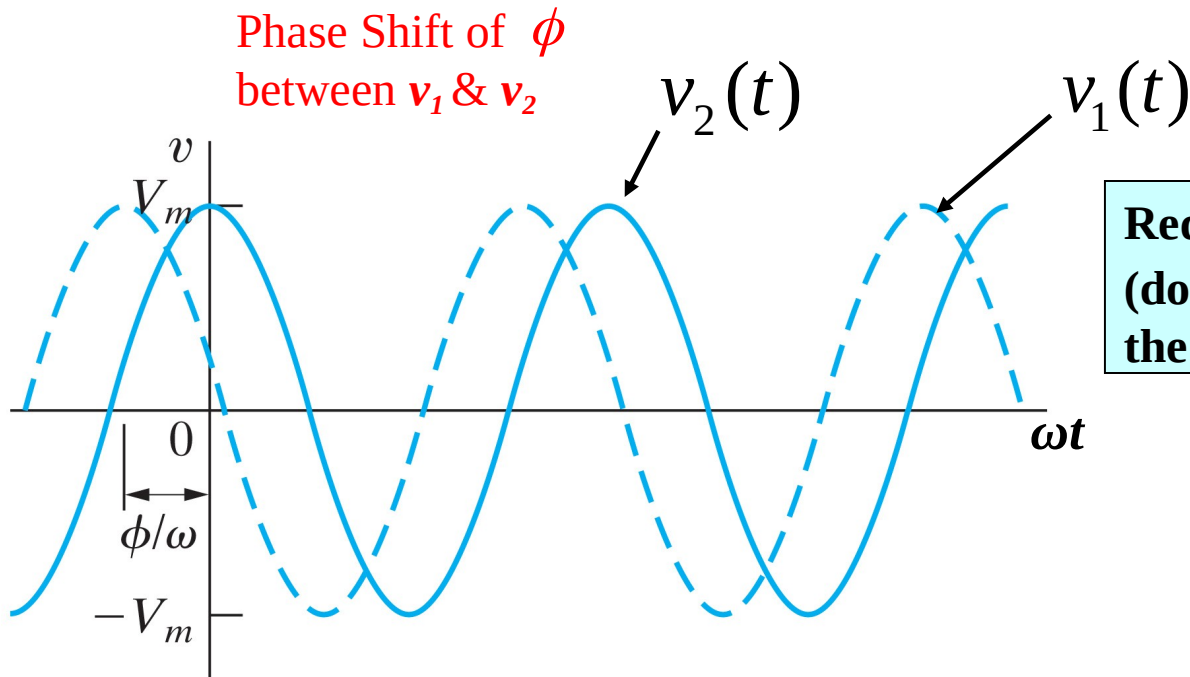

Reducing ϕ to zero shifts $v_1(t)$ (dotted line) ϕ / ω time units to the right

$$v_1(t) = V_m \cos(\omega t + \phi)$$

$$v_2(t) = V_m \cos(\omega t)$$

Figure: 09-02

Copyright © 2008 Pearson Prentice Hall, Inc.

Root-Mean-Square (RMS)

$$f_{rms} = \sqrt{\frac{1}{T} \int_T f^2(t) dt}$$

RMS definition

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \sin^2(\omega t + \phi) dt}$$

RMS Calculation of an AC signal

(Square **R**oot of the **M**ean value of the **S**quared Function)

Using $\sin^2(\theta) = \frac{1}{2} - \frac{1}{2}\cos(2\theta)$, we can show


$$V_{rms} = \frac{V_m}{\sqrt{2}} \text{ for a sine wave}$$

After integrated over a period and simplifying

At Power Outlet:

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{311.12}{\sqrt{2}} = 220V$$

Sinusoidal Response: Find $i(t)$

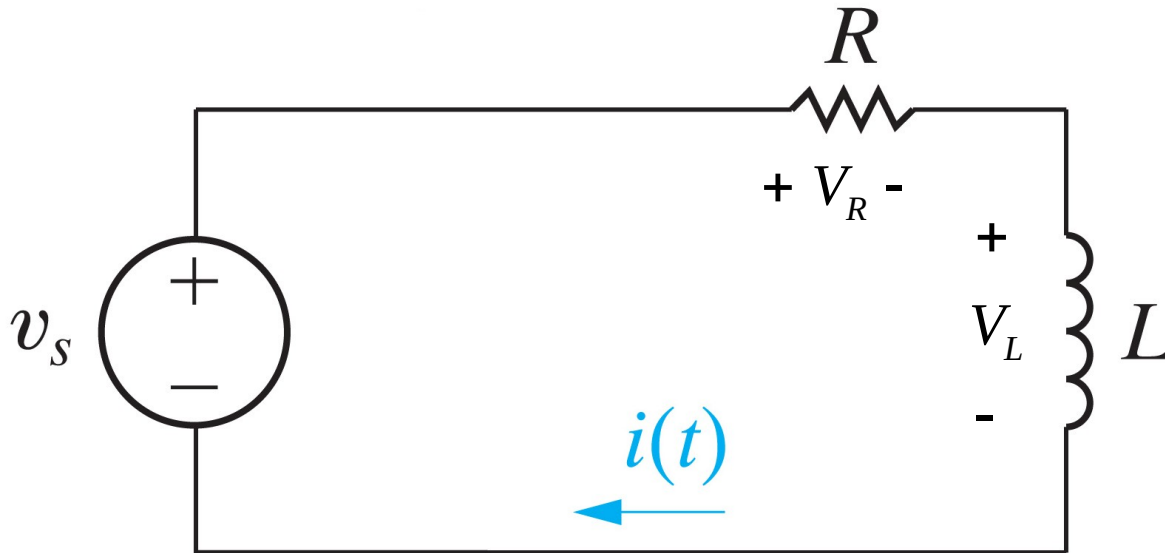

$$v_s = V_m \cos(\omega t + \phi)$$

$$V_s = V_R + V_L \quad \left. \vphantom{V_s = V_R + V_L} \right\} \text{KVL}$$

$$V_m \cos(\omega t + \phi) = Ri + L \frac{di}{dt} \quad \left. \vphantom{V_m \cos(\omega t + \phi) = Ri + L \frac{di}{dt}} \right\} \text{Use Ohm's Law and Inductor Law}$$

Solution of Differential Equation requires Advanced Tools

Sinusoidal Response (Contd.)

$$v_s = V_m \cos(\omega t + \phi) \left\} \begin{array}{l} \text{Voltage Input to RL Circuit} \end{array} \right.$$

Neglects
Transients

$$\left\{ i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos \left(\omega t + \phi - \tan^{-1} \left[\frac{\omega L}{R} \right] \right) \right\} \begin{array}{l} \text{Steady} \\ \text{State} \\ \text{Solution} \end{array}$$

Notes:

1. $i(t)$ has the same form as $V_s(t)$ in steady state
2. $i(t)$ has a different amplitude and different phase when compared to $V_s(t)$
3. Use Phasors to find the Steady State Solution

Phasors Definition

Phasor

A Complex Number Which Contains Amplitude and Phase Information of a Sinusoidal Function.

Does Not Contain Information on frequency (i.e. ω)
Frequency Does Not Change in a Linear Circuit

Phasor exploits Euler's Identity

$$e^{\pm j\theta} = \cos \theta \pm j \sin \theta \quad (j = \sqrt{-1})$$

$$\cos \theta = \frac{1}{2} (e^{j\theta} + e^{-j\theta})$$

$$\sin \theta = -j \frac{1}{2} (e^{j\theta} - e^{-j\theta})$$

Useful identities

Review of Complex Numbers

We can express a complex number in two ways

Rectangular

$$\overline{A} = a + j \cdot b \quad \left. \vphantom{\overline{A} = a + j \cdot b} \right\} j = \sqrt{-1}$$

Complex Number Real Part Imaginary Part


$$\operatorname{Re}[\overline{A}] = a; \quad \operatorname{Im}[\overline{A}] = b$$

a and b are “Real” Numbers
 jb is an “Imaginary” Number
 A is a “Complex” Number

Polar

$$\overline{A} = ce^{j\theta} = c \angle \theta \quad \left. \vphantom{\overline{A} = ce^{j\theta} = c \angle \theta} \right\} j = \sqrt{-1}$$

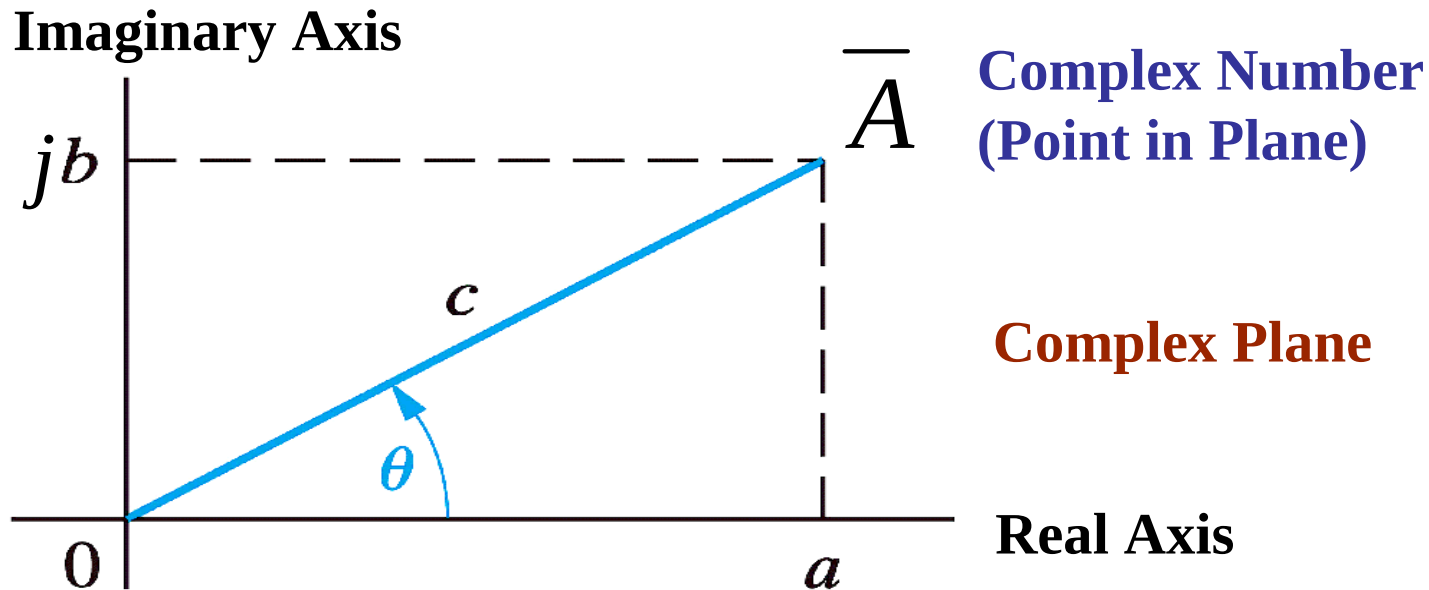Polar \longleftrightarrow Rectangular Conversion




$$\bar{A} = a + jb = c \angle \theta$$

$$c = \sqrt{a^2 + b^2} \quad \theta = \tan^{-1}\left(\frac{b}{a}\right) \quad \left. \vphantom{\begin{matrix} c \\ \theta \end{matrix}} \right\} \text{Rectangular} \rightarrow \text{Polar}$$

$$\left. \begin{matrix} a = c \cos(\theta) \\ b = c \sin(\theta) \end{matrix} \right\} \text{Polar} \rightarrow \text{Rectangular}$$

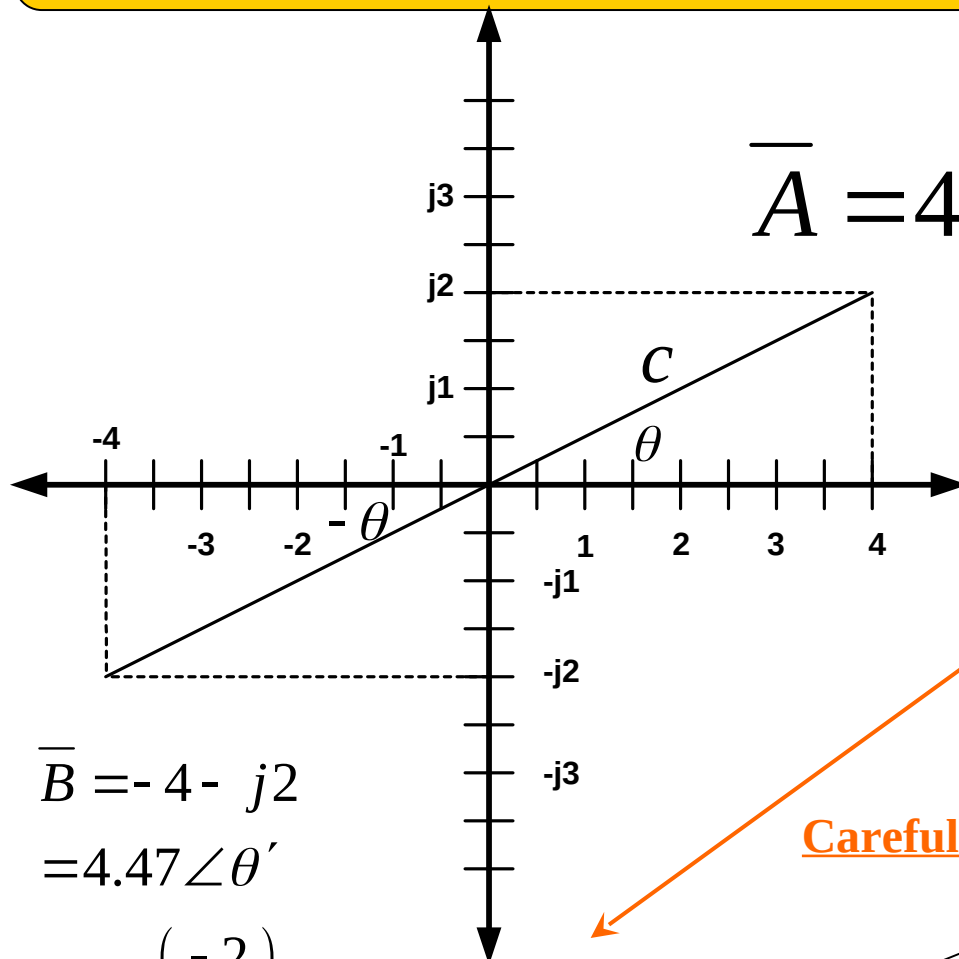Two Examples: Rectangular to Polar Conversion



$$\bar{A} = 4 + j2$$

$$C = \sqrt{4^2 + 2^2} = 4.47$$

$$\theta = \tan^{-1}\left(\frac{2}{4}\right) = 26.6^\circ$$

$$\bar{A} = 4.47 \angle 26.6^\circ \equiv 4.47 e^{j26.6}$$

$$\bar{B} = -4 - j2$$

$$= 4.47 \angle \theta'$$

$$\tan^{-1}\left(\frac{-2}{-4}\right) = 26.6^\circ \text{ (from x-axis)}$$

$$\theta' = 26.6^\circ + 180^\circ = 206.6^\circ$$

Careful !

$$\begin{aligned} \bar{B} &= 4.47 \angle 206.6^\circ \equiv \\ &\equiv 4.47 \angle 206.6^\circ - 360^\circ \\ &= 4.47 \angle -153.4^\circ \end{aligned}$$

Complex Conjugate

Reverse Signs of Imaginary Part

$$\overline{A} = a + jb = c \angle \theta$$

$$\overline{A}^* = a - jb = c \angle -\theta$$

Note: $\overline{A} \cdot \overline{A}^* = (a + jb)(a - jb) = c \angle \theta \cdot c \angle -\theta$ } Can we simplify further?

$$(a + jb)(a - jb) = a^2 + jba - jba - j^2b^2$$

} Multiply it out

$$= a^2 - j^2b^2 = a^2 + b^2$$

} $j^2 = -1$

$$\overline{A} \cdot \overline{A}^* = a^2 + b^2 = c^2$$

$$c \angle \theta \cdot c \angle -\theta = c^2 \angle (\theta + (-\theta)) = c^2 \angle 0 = c^2$$

add angles

Complex Arithmetic

$$\bar{A} = a + jb = c_1 \angle \theta_1$$

$$\bar{B} = y + jz = c_2 \angle \theta_2$$

Given two complex numbers

$$\bar{A} + \bar{B} = (a + y) + j(b + z) \quad \text{Add}$$

$$\bar{A} - \bar{B} = (a - y) + j(b - z) \quad \text{Subtract}$$

Must Convert to Rectangular

$$\bar{A} \cdot \bar{B} = (a + jb) \cdot (y + jz) = ay + jby + jza - bz$$

$$\bar{A} \cdot \bar{B} = c_1 \angle \theta_1 \cdot c_2 \angle \theta_2 = c_1 \cdot c_2 \angle (\theta_1 + \theta_2)$$

$$\frac{\bar{A}}{\bar{B}} = \frac{c_1 \angle \theta_1}{c_2 \angle \theta_2} = \frac{c_1}{c_2} \angle (\theta_1 - \theta_2)$$

$$\frac{\bar{A}}{\bar{B}} = \frac{a + jb}{y + jz} \cdot \frac{y - jz}{y - jz} = \frac{(a + jb) \cdot (y - jz)}{y^2 + z^2}$$

Integer Powers

$$\bar{A}^k = (a + jb)^k = [c_1 \angle \theta_1]^k$$

$$\bar{A}^k = c_1^k \angle (k \cdot \theta_1)$$

Follows from Polar Multiplication

Back to AC Circuits

$$e^{\pm j\theta} = \cos \theta \pm j \sin \theta \quad \left. \vphantom{e^{\pm j\theta}} \right\} \text{Euler Identity}$$

$$\operatorname{Re} \left[e^{j\theta} \right] = \cos \theta$$

$$\operatorname{Im} \left[e^{j\theta} \right] = \sin \theta$$

$$v = V_m \sin(\omega t + \phi)$$

$$v = V_m \operatorname{Im} \left[e^{j(\omega t + \phi)} \right]$$

$$v = \operatorname{Im} \left[V_m e^{j\phi} e^{j\omega t} \right]$$

For steady state

$\left[\begin{array}{l} \omega \text{ Does Not Change} \\ \phi \text{ and } V_m \text{ Do Change} \end{array} \right]$

Phasor Representation

$$\bar{V} = V_m e^{j\phi} \equiv V_m \angle \phi = P \{ V_m \sin(\omega t + \phi) \} \quad \left. \vphantom{\bar{V}} \right\} \text{P stands for Phasor}$$

$$\bar{V} = V_m \angle \phi \quad \text{Polar}$$

$$\bar{V} = V_m \cos \phi + j V_m \sin \phi \quad \text{Rectangular}$$

$$v(t) = V_m \sin(\omega t + \phi) \quad \left. \vphantom{v(t)} \right\} \text{Time Domain}$$

$$\bar{V} = V_m \angle \phi \quad \left. \vphantom{\bar{V}} \right\} \text{Frequency Domain}$$

$$\bar{V} = V_m e^{j\phi} \quad \text{Phasor}$$

Phasor is a
Complex Number

$$\text{Euler} \quad e^{j\phi} = \cos \phi + j \sin \phi$$

$$\bar{V} = V_m e^{j\phi} = V_m \cos \phi + j V_m \sin \phi = a + jb = \bar{V}$$



Phasor Representation (Contd.)

$$\overline{V} = V_m e^{j\phi} \equiv V_m \angle \phi$$

Frequency Domain

$$v(t) = V_m \sin(\omega t + \phi)$$

Time Domain

Example


$$\overline{V} = 215 \angle -112^\circ$$

Frequency Domain

$$v(t) = 215 \sin(\omega t - 112^\circ)$$

Time Domain

Apply Concepts to AC RL Circuit

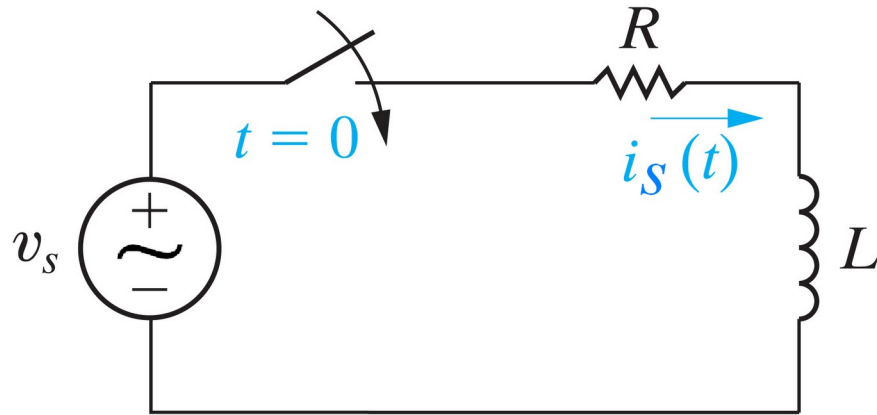

$$v_s(t) = V_m \sin(\omega t + \phi)$$

$$i_s(t) = I \sin(\omega t + \beta)$$

Find Steady-State Solution

Note v_s and i_s are Not Necessarily in Phase

$$\textcircled{1} \quad v_s = Ri_s + L \frac{di_s}{dt} \quad \left. \vphantom{\frac{di_s}{dt}} \right\} \text{KVL}$$

$$\textcircled{2} \quad v_s = \text{Im} \left\{ V_m e^{j\phi} e^{j\omega t} \right\} \quad i_s = \text{Im} \left\{ I e^{j\beta} e^{j\omega t} \right\} \quad \left. \vphantom{\text{Im}} \right\} \text{Euler Representation}$$

$$\textcircled{3} \quad \text{Im} \left\{ V_m e^{j\phi} e^{j\omega t} \right\} = R \text{Im} \left\{ I e^{j\beta} e^{j\omega t} \right\} + L \frac{d}{dt} \text{Im} \left\{ I e^{j\beta} e^{j\omega t} \right\} \quad \left. \vphantom{\frac{d}{dt}} \right\} \text{Substitute } \textcircled{2} \text{ into } \textcircled{1}$$

$$\textcircled{4} \quad \text{Im} \left\{ V_m e^{j\phi} e^{j\omega t} \right\} = R \text{Im} \left\{ I e^{j\beta} e^{j\omega t} \right\} + Lj\omega \text{Im} \left\{ I e^{j\beta} e^{j\omega t} \right\}$$

$$\textcircled{5} \quad \text{Im} \left\{ V_m e^{j\phi} e^{j\omega t} \right\} = (R + j\omega L) \text{Im} \left\{ I e^{j\beta} e^{j\omega t} \right\} \quad \left. \vphantom{\text{Im}} \right\} \text{Apply phasor notation to } \textcircled{5}$$

Ohm's Law-like Relationship

$$\textcircled{6} \quad V_m \angle \phi = (R + j\omega L) I \angle \beta$$

Time Domain Solution to the Circuit

$$\bar{I} = I \angle \beta = \frac{V_m \angle \phi}{R + j\omega L} \quad \left. \vphantom{\frac{V_m \angle \phi}{R + j\omega L}} \right\} \text{Impedance Law}$$

$$\bar{I} = \frac{V_m \angle \phi}{\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1} \left(\frac{\omega L}{R} \right)} \quad \left. \vphantom{\frac{V_m \angle \phi}{\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1} \left(\frac{\omega L}{R} \right)}} \right\} \text{Convert denominator to polar form}$$

$$\bar{I} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle \left(\phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right) \quad \left. \vphantom{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle \left(\phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right)}} \right\} \begin{array}{l} \text{Divide magnitudes} \\ \text{Subtract angles} \end{array}$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\omega t + \phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right) \quad \left. \vphantom{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\omega t + \phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right)}} \right\} \begin{array}{l} \text{Because } V_m \text{ was} \\ \text{defined to be a sine} \\ \text{function} \end{array}$$

Time Domain Solution to the Circuit

(Contd.)

Cosine Input $\left\{ V_m \cos(\omega t + \phi) = Ri + L \frac{di}{dt} \right\}$ **Differential Equation**

Cosine Output $\left\{ i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos \left(\omega t + \phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right) \right\}$ **Steady State Solution**

Sine Input $\left\{ V_m \sin(\omega t + \phi) = Ri + L \frac{di}{dt} \right\}$ **Differential Equation**

Sine Output $\left\{ i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\omega t + \phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right) \right\}$ **Steady State Solution**

Impedance Functions

$$\bar{V}_s = \bar{I}_s Z_{eq} \quad \left. \vphantom{\bar{V}_s = \bar{I}_s Z_{eq}} \right\} \text{Ohm's Law for Phasors}$$

$$Z_{eq} = R + j\omega L \quad \left. \vphantom{Z_{eq} = R + j\omega L} \right\} \text{Impedance Function}$$

$$Z_{eq} = Z_R + Z_L \quad \left. \vphantom{Z_{eq} = Z_R + Z_L} \right\} \text{Passive elements have a steady state impedance function}$$

$$Z_R = R$$

Resistor

$$Z_L = j\omega L$$

Inductor

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

Capacitor

Essentials of Phasors

$$\bar{A} = a + jb = c \angle \theta$$

$$c = \sqrt{a^2 + b^2} \quad \theta = \tan^{-1} \left(\frac{b}{a} \right)$$

$$a = c \cos(\theta) \quad b = c \sin(\theta)$$

$$\sin(\omega t) \equiv \cos(\omega t - 90^\circ)$$

**Important
Trig
Formulae**

$$v(t) = V_m \cos(\omega t + \phi)$$

$$\bar{V} = V_m \angle \phi$$


$$I(t) = I_m \cos(\omega t + \beta)$$

$$\bar{I} = I_m \angle \beta$$

**Phasors
Notation**

Impedance for 2nd – order circuit
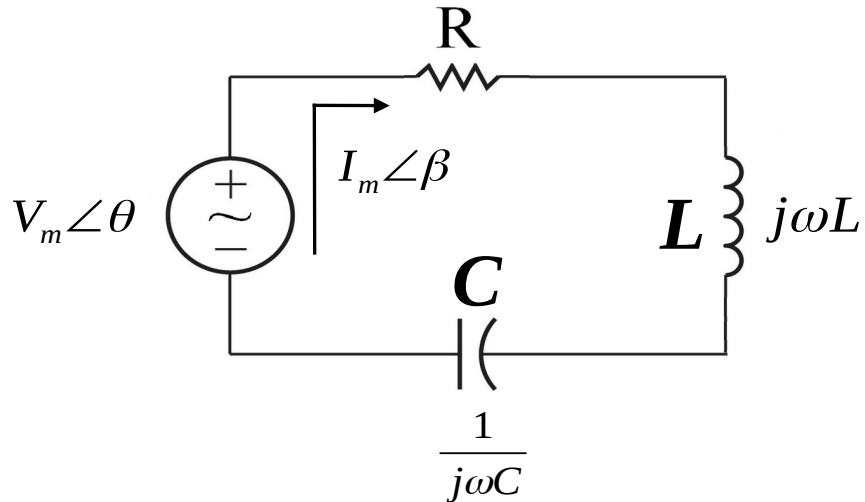
$$Z_R = R \quad Z_L = j\omega L \quad Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$



$$V_m \angle \theta = I_m \angle \beta [Z_R + Z_L + Z_C] \quad \left. \vphantom{V_m \angle \theta} \right\} \text{KVL}$$

$$V_m \angle \theta = I_m \angle \beta \cdot Z_{eq}$$

$$Z_{eq} = R + j\omega L + \frac{1}{j\omega C}$$

$$\bar{I} = I_m \angle \beta = \frac{V_m \angle \theta}{R + j\omega L + \frac{1}{j\omega C}}$$

Solve for \bar{I}

Assume Cosine function for consistency with the book

$$\begin{array}{ll} v(t) = V_m \cos(\omega t + \phi) & \left. \vphantom{v(t)} \right\} \text{Cosine Input} \\ \bar{V} = V_m \angle \phi & \left. \vphantom{\bar{V}} \right\} \text{Phasor Representation} \\ v(t) = V_m \sin(\omega t + \phi) \equiv V_m \cos(\omega t + \phi - 90) & \left. \vphantom{v(t)} \right\} \text{Sine Input} \\ \bar{V} = V_m \angle (\phi - 90) & \left. \vphantom{\bar{V}} \right\} \text{Phasor Representation} \end{array}$$

Note the Trig formula often used

$$\bar{A} = a + jb = c \angle \theta$$

$$c = \sqrt{a^2 + b^2} \qquad \theta = \tan^{-1} \left(\frac{b}{a} \right)$$

$$a = c \cos(\theta) \qquad b = c \sin(\theta)$$

$$\left[\sin(\omega t) = \cos(\omega t - 90) \right]$$

Drill Exercise

a) $v(t) = 170 \cos(377t - 40^\circ) \text{ (V)}$ } Time Function

$$\bar{V} = 170 \angle -40^\circ \text{ (V)}$$

Phasor Representation

b) $i(t) = 10 \sin(1000t + 20^\circ) \text{ (A)}$ } Time Function

$$\bar{I} = 10 \angle (20^\circ - 90^\circ) \text{ (A)}$$

$\sin(\omega t) = \cos(\omega t - 90^\circ)$

$$\bar{I} = 10 \angle -70^\circ \text{ (A)}$$

Phasor Representation

c) $v(t) = 300 \cos(20,000\pi t + 45^\circ) - 100 \sin(20,000\pi t + 30^\circ) \text{ (mV)}$ } Time Function

$$\bar{V} = 300 \angle 45^\circ - 100 \angle (30^\circ - 90^\circ)$$

Phasor Representation

$$\bar{V} = 300 \angle 45^\circ - 100 \angle -60^\circ$$

Need to simplify

$$300 \angle 45^\circ$$

\Downarrow

$$a_1 + b_1 j$$

$$a_1 = 300 \cos(45^\circ) = 212.13$$

$$b_1 = 300 \sin(45^\circ) = 212.13$$

$$a_2 = 100 \cos(-60^\circ) = 50$$

$$b_2 = 100 \sin(-60^\circ) = -86.60$$

$$100 \angle -60^\circ$$

\Downarrow

$$a_2 + b_2 j$$

Drill Exercise (Contd.)

$$\bar{V} = (212.13 + j212.13) - (50 - j86.60) \quad \left. \vphantom{\bar{V}} \right\} \text{Substitute and add}$$

$$\bar{V} = 162.13 + j298.73 \quad \left. \vphantom{\bar{V}} \right\} \text{Rectangular form}$$

$$c = \sqrt{(162.13)^2 + (298.73)^2} = 339.89$$

$$\theta = \tan^{-1}(298.73/162.13) = 61.51^\circ$$

Convert to polar

$$\bar{V} = 339.89 \angle 61.51^\circ \quad (mV)$$

Phasor Representation

$$v(t) = 339.89 \cos(20,000\pi t + 61.51^\circ) \quad (mV)$$

Time Function

Drill Exercise (Contd.)

$$d) \quad \bar{V} = (60 + j30 + 100\angle -28^\circ) \text{ (V)} \quad \left. \vphantom{\bar{V}} \right\} \text{Find Phasor}$$

$$100\angle -28^\circ = 88.295 - j46.947 \quad \left. \vphantom{100\angle -28^\circ} \right\} \text{Convert to Rectangular form}$$

$$\bar{V} = (60 + j30 + 88.295 - j46.947) \text{ (V)} \quad \left. \vphantom{\bar{V}} \right\} \text{After combining}$$

$$\bar{V} = (148.295 - j16.947) \quad \left. \vphantom{\bar{V}} \right\} \text{Simplify}$$

$$\bar{V} = 149.26\angle -6.52^\circ \quad \left. \vphantom{\bar{V}} \right\} \text{Convert to Polar}$$

$$v(t) = 149.26 \cos(\omega t - 6.52^\circ) \text{ (V)} \quad \left. \vphantom{v(t)} \right\} \text{Time Function}$$


$$\cos(\omega t) = \sin(\omega t + 90^\circ) \quad \left. \vphantom{\cos(\omega t)} \right\} \text{Trig Identity}$$

$$v(t) = 149.26 \sin(\omega t + 90^\circ - 6.52^\circ) \text{ (V)}$$

$$v(t) = 149.26 \sin(\omega t + 83.48^\circ) \text{ (V)} \quad \left. \vphantom{v(t)} \right\} \text{In terms of a sine function}$$

Impedance and Reactance (R , L , and C)

Resistor:

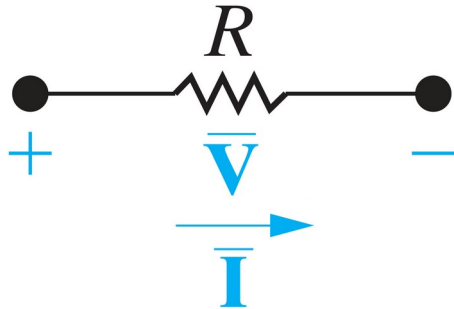

Ohm's Law:

$$v = i \cdot R \quad \text{Time Domain}$$

$$\bar{V} = \bar{I} \cdot R \quad \text{Frequency Domain}$$

No Phase Shift

v and i are in “In – Phase”

Inductor:


For $i(t) = I_m \cos(\omega t + \theta) \Rightarrow \bar{I} = I_m \angle \theta$ } I_m is Amplitude

$$v = L \frac{di}{dt} = -L \cdot I_m \cdot \omega \cdot \sin(\omega t + \theta) = -\omega \cdot L \cdot I_m \cdot \sin(\omega t + \theta)$$

$$v = -\omega \cdot L \cdot I_m \cdot \cos(\omega t + \theta - 90^\circ)$$

$$\therefore \bar{V} = -\omega \cdot L \cdot I_m \cdot \angle(\theta - 90^\circ) \} \text{Phasor Representation}$$
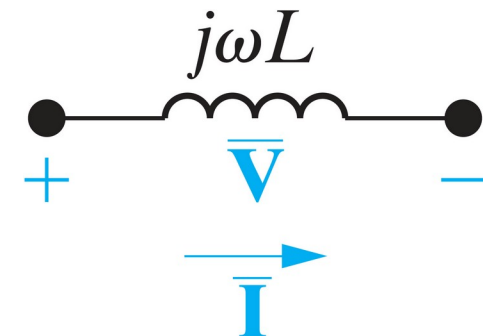
$$\bar{V} = -\omega \cdot L \cdot I_m \cdot e^{j(\theta - 90^\circ)} = -\omega \cdot L \cdot I_m \cdot e^{j\theta} e^{-j90^\circ}$$



Inductor Impedance

$$\bar{V} = -\omega \cdot L \cdot I_m \cdot e^{j\theta} e^{-j90^\circ} \quad \left\{ \begin{array}{l} \text{From previous slide} \end{array} \right.$$

$$\bar{V} = -\omega \cdot L \cdot I_m \cdot e^{j\theta} [-j] \quad \left\{ \begin{array}{l} e^{-j90^\circ} = \cos(90^\circ) - j \sin(90^\circ) = -j \end{array} \right.$$

$$\bar{V} = (j\omega L) I_m e^{j\theta} = (j\omega L) I_m \angle \theta \quad \left\{ \begin{array}{l} \text{Simplify} \end{array} \right.$$

$$\textcircled{1} \quad \bar{V} = (j\omega L) \bar{I} \quad \left\{ \begin{array}{l} \text{Like Ohm's Law} \end{array} \right.$$

Voltage Leads
Current for
Inductors


Current Leads
Voltage for
Capacitors

$$\textcircled{2} \quad \bar{V} = (\omega L \angle 90^\circ) (I_m \angle \theta) \quad \left\{ \begin{array}{l} \text{Substitute } j = \angle 90^\circ \text{ and } \bar{I} = I_m \angle \theta \text{ into } \textcircled{1} \end{array} \right.$$

$$\underbrace{\bar{V} = \omega \cdot L \cdot I_m \cdot \angle(\theta + 90^\circ)}_{\text{Phasor}} \Rightarrow \underbrace{v(t) = \omega \cdot L \cdot I_m \cdot \cos(\omega t + \theta + 90^\circ)}_{\text{Time Domain}} \quad \left\{ \begin{array}{l} \text{Voltage Leads Current} \end{array} \right.$$

$$i(t) = I_m \cos(\omega t + \theta) \quad \left\{ \begin{array}{l} \text{Original definition of } i(t) \end{array} \right.$$

Capacitor

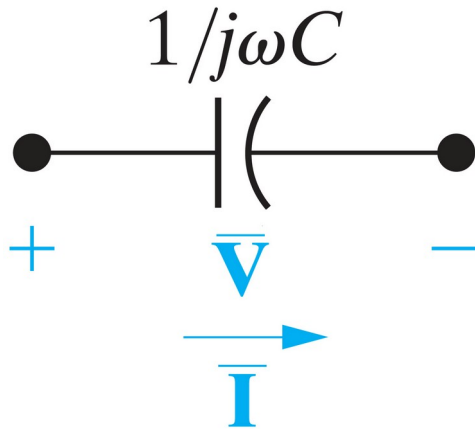

Use Similar Arguments

$$\bar{V} = \left(\frac{1}{j\omega C} \right) \bar{I} \quad \left. \vphantom{\bar{V}} \right\} \text{Like Ohm's Law}$$

$$\bar{V} = \left(\frac{-j}{\omega C} \right) \bar{I} \quad \left. \vphantom{\bar{V}} \right\} \text{Use } \frac{1}{j} = -j$$

Current Leads Voltage

Impedance Summary

$$\bar{V}_R = \bar{I} (R)$$

$$\bar{V}_L = \bar{I} (j\omega L)$$

$$\bar{V}_C = \bar{I} \left(\frac{1}{j\omega C} \right)$$

All Look Like A
Form Of
“Ohm’s” Law

$$\bar{V} = \bar{I}Z \text{ where}$$

$$Z_R = R$$

$$Z_L = j\omega L$$

$$Z_C = \left(\frac{1}{j\omega C} \right)$$

Note:

1. Z is a Complex Number
2. Z is NOT a Phasor

Reactance: Imaginary Part of Impedance

$$\omega L \quad \text{for Inductors} \quad \left. \vphantom{\omega L} \right\} \boxed{Z_L = j\omega L}$$

$$-\frac{1}{\omega C} \quad \text{for Capacitors} \quad \left. \vphantom{-\frac{1}{\omega C}} \right\} \boxed{Z_C = -\frac{j}{\omega C}}$$

$$0 \quad \text{for Resistors} \quad \left. \vphantom{0} \right\} \boxed{Z_R = R}$$


$$Z_{Total} = \text{Resistance} + j \text{ Reactance}$$

Notes:

So we can think of these “Impedances” as “Analogous to Resistance”.

Ohm’s Law, KVL, KCL, all behave Mathematically as if **Z**’s were **R**’s .

Example: Find $v(t)$

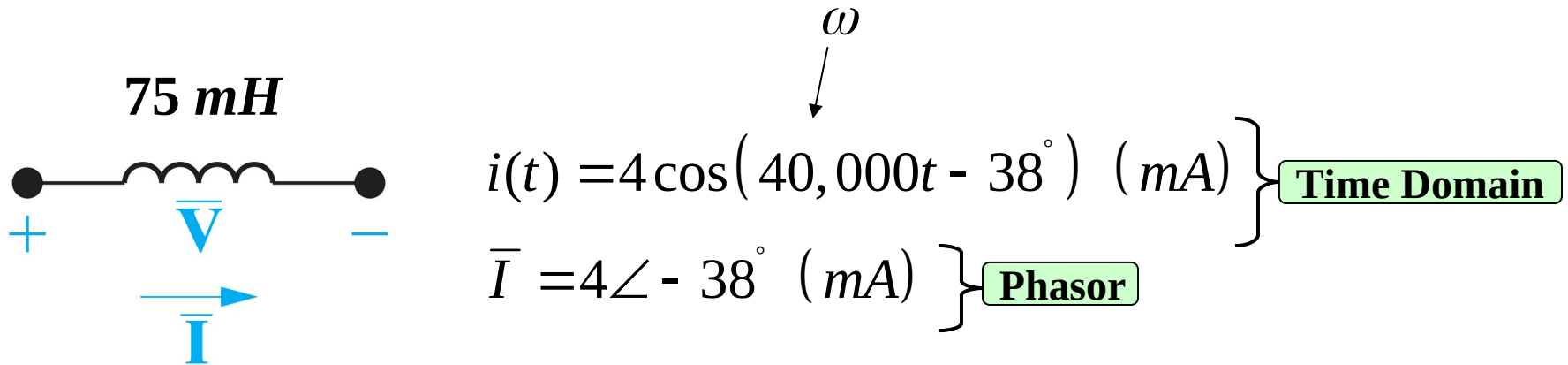

a) Reactance $= \omega L = 40,000(75 \times 10^{-3})$

$$\omega L = 3000 \text{ (}\Omega\text{)} \quad \text{Positive Number}$$

b) Impedance $= Z_L = j\omega L = j3000 \text{ (}\Omega\text{)} \quad \text{Complex Number}$

Example (Contd.)

$$\begin{aligned} c) \quad \bar{V} &= \bar{I} \cdot j\omega L = (4 \times 10^{-3} \angle -38^\circ) \cdot j40,000 \cdot 0.075 \quad \left. \vphantom{\bar{V}} \right\} \text{Use Ohm's Law} \\ &= (4 \times 10^{-3} \angle -38^\circ) \cdot j3000 \\ &= (12 \angle -38^\circ) \cdot j \\ &= (12 \angle -38^\circ) \cdot (\angle 90^\circ) \quad \left. \vphantom{\bar{V}} \right\} j = 90^\circ \\ \bar{V} &= 12 \angle 52^\circ \text{ (V)} \quad \left. \vphantom{\bar{V}} \right\} \text{Phasor} \end{aligned}$$

$$\begin{aligned} d) \quad v(t) &= 12 \cos(\omega t + 52^\circ) \text{ (V)} \quad \left. \vphantom{v(t)} \right\} \text{Time Domain} \\ v(t) &= 12 \cos(40,000t + 52^\circ) \text{ (V)} \quad \left. \vphantom{v(t)} \right\} \text{Plug in } \omega \end{aligned}$$

Kirchhoff's Laws in the Frequency Domain

$$v_1(t) + v_2(t) + \dots + v_n(t) = 0 \quad \left. \vphantom{v_1(t) + v_2(t) + \dots + v_n(t) = 0} \right\} \text{KVL}$$

$$\bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_n = 0 \quad \text{Phasor Version}$$

$$i_1(t) + i_2(t) + \dots + i_n(t) = 0 \quad \left. \vphantom{i_1(t) + i_2(t) + \dots + i_n(t) = 0} \right\} \text{KCL}$$

$$\bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_n = 0 \quad \text{Phasor Version}$$


KVL and KCL along with $\bar{V} = \bar{I} \bar{Z}$

Forms the Basis of Frequency Domain (AC) Analysis

We can use same techniques as in Chap. 1 - 4

but we must manipulate complex numbers.

Example: Find $i_4(t)$

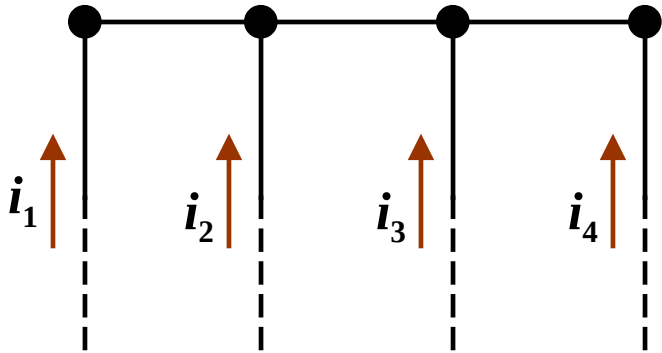

$$i_1(t) = 100 \cos(\omega t + 25^\circ) \text{ A}$$

$$i_2(t) = 100 \cos(\omega t + 145^\circ) \text{ A}$$

$$i_3(t) = 100 \cos(\omega t - 95^\circ) \text{ A}$$

$$\text{KCL:} \quad i_4 = -(i_1 + i_2 + i_3) \quad \bar{I}_4 = -(\bar{I}_1 + \bar{I}_2 + \bar{I}_3)$$

$$\bar{I}_1 = 100 \angle 25^\circ = 90.63 + j42.26$$

Convert

$$\bar{I}_2 = 100 \angle 145^\circ = -81.92 + j57.36$$

Convert

$$\bar{I}_3 = 100 \angle -95^\circ = -8.71 - j99.62$$

Convert

$$\bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 0 - j0$$

Add together

$$\bar{I}_4 = 0 + j0 \text{ A} = 0$$

$$i_4(t) = 0 \text{ (A)}$$

Series and Parallel Combinations

Series: $Z_{tot} = Z_1 + Z_2 + \dots + Z_n$ } **Add**

Parallel: $\frac{1}{Z_{tot}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$ } **Add reciprocals**

$n = 2 \Rightarrow Z_{tot} = \frac{Z_1 Z_2}{Z_1 + Z_2}$

Admittance Makes Parallel Combinations Easier


$$Y = \left(\frac{1}{Z} \right) = G + jB$$

$G \equiv$ Conductance

$B \equiv$ Susceptance

Series and Parallel Combinations


(Contd.)

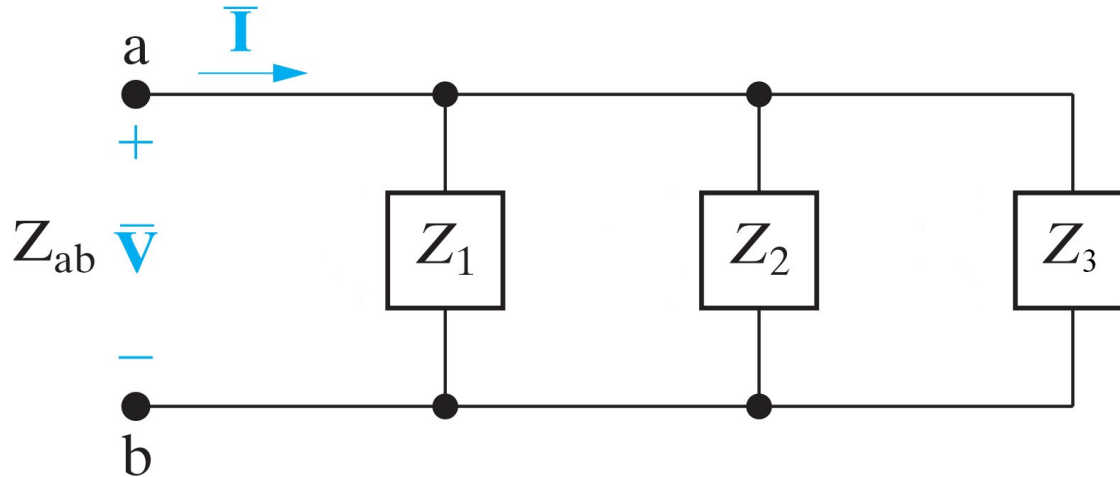

$$Y_{ab} = Y_1 + Y_2 + Y_3 = Y_m \angle \theta \quad \left. \vphantom{Y_{ab} = Y_1 + Y_2 + Y_3} \right\} \text{Add admittance}$$

$$Z_{ab} = \frac{1}{Y_{ab}} = \frac{1}{Y_m \angle \theta} = \frac{1}{Y_m} \angle -\theta \quad \left. \vphantom{Z_{ab} = \frac{1}{Y_{ab}}} \right\} \text{Reciprocate to obtain impedance}$$

Example: RLC Circuit

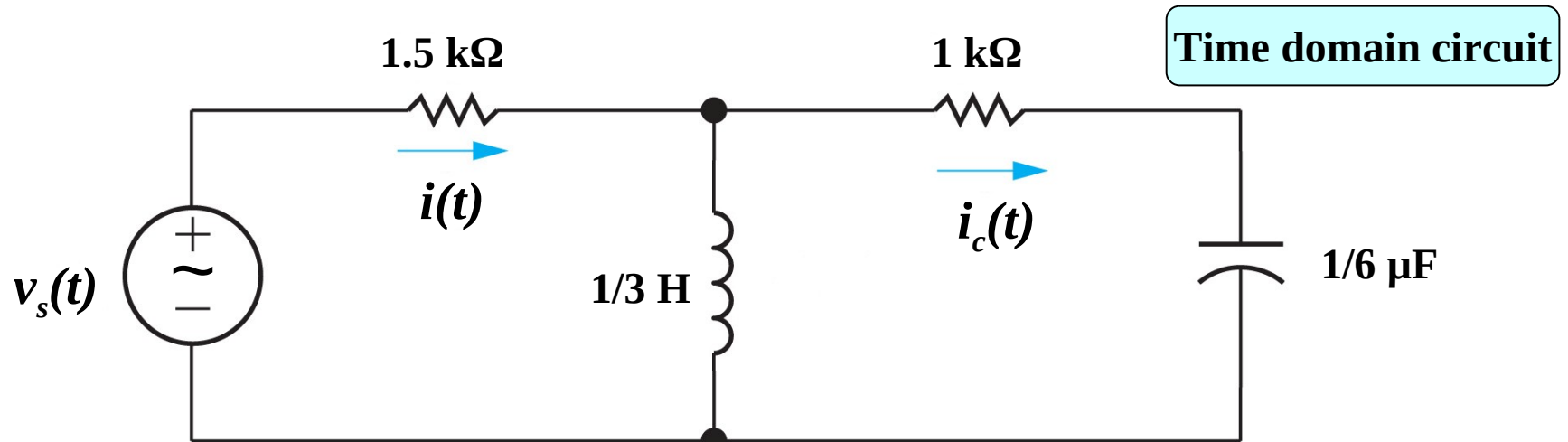

$$\left. \begin{aligned} v_s &= 40 \sin(3000t) \\ \omega &= 3000 \text{ rad/s} \end{aligned} \right\}$$

Given

Find the steady currents $i(t)$ and $i_c(t)$

$$j\omega L = j(3000) \left(\frac{1}{3} \right) = j1 \text{ (k}\Omega\text{)}$$

Inductor impedance


$$\frac{1}{j\omega C} = \frac{-j}{\omega C} = -j \left(\frac{1}{3000} \right) \left(\frac{1}{1/6 \times 10^{-6}} \right) = -j2 \text{ (k}\Omega\text{)}$$

Capacitor impedance

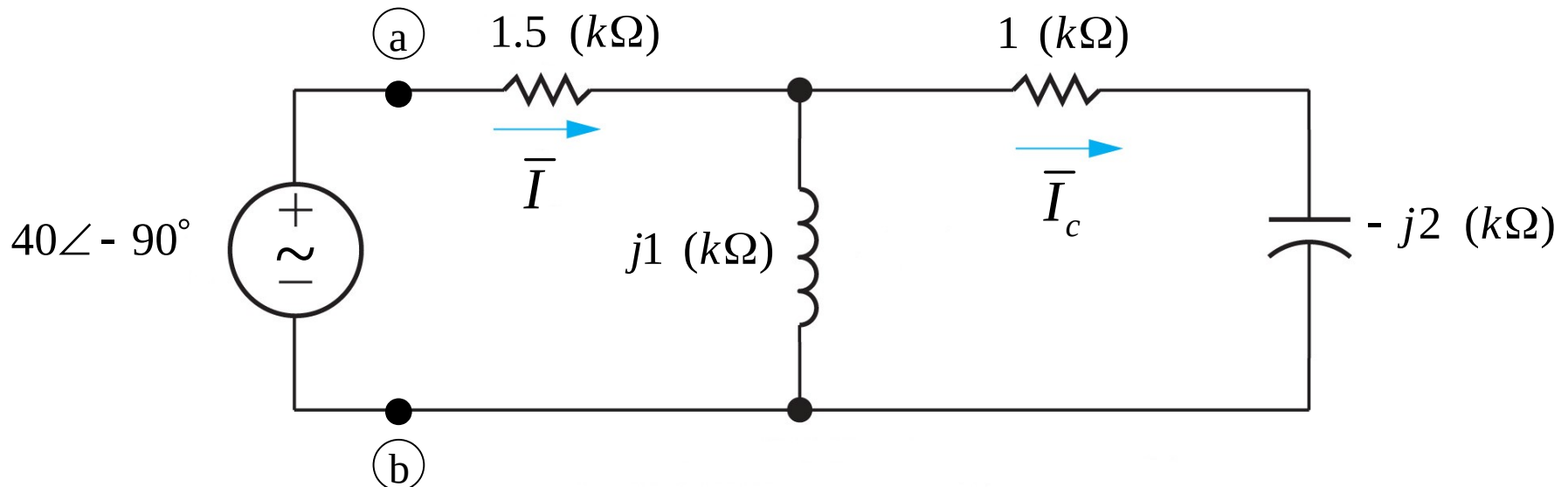Example (Contd.)


Find the Frequency Domain Circuit

$$\bar{V}_s = 40 \angle -90^\circ \quad \left. \vphantom{\bar{V}_s} \right\} \text{ since } V_s = 40 \underline{\underline{\sin 3000t}}$$



Find Impedance at (a) and (b) then find $i(t)$ and $i_c(t)$

Example (Contd.)

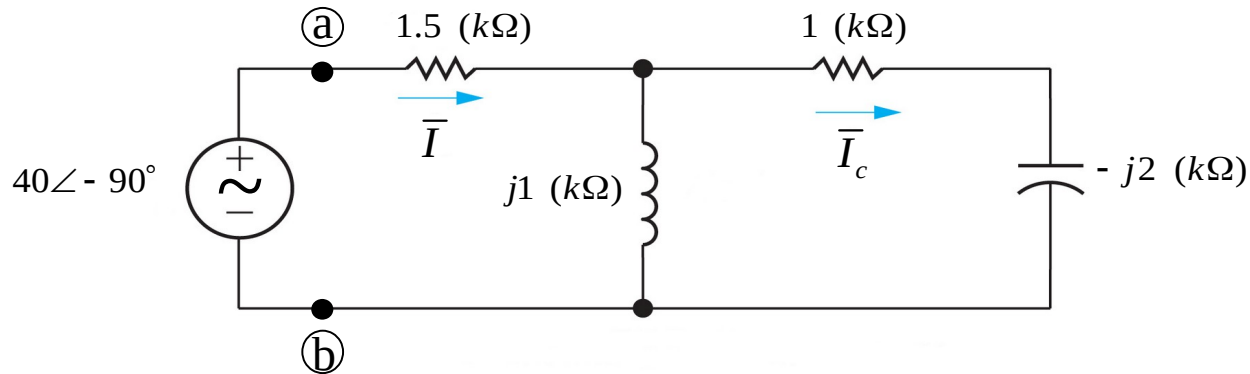

Find Equivalent Impedance "Seen" by the Source:

$$Z_{eq} = [1.5 + j \parallel (1 - j2)] \text{ (k}\Omega\text{)} \quad \left. \vphantom{Z_{eq}} \right\} \text{Impedance at (a) and (b)}$$

$$= 1.5 + \frac{j(1 - j2)}{j + (1 - j2)} = 1.5 + \frac{j + 2}{-j + 1}$$

$$= 1.5 + \frac{2 + j}{1 - j} \left(\frac{1 + j}{1 + j} \right) = 1.5 + \frac{2 + 2j + j - 1}{1 - j + j + 1}$$

$$= 1.5 + \frac{1 + j3}{2} = 2 + j1.5 \quad \leftarrow \text{Complex Conjugate}$$

$$Z_{eq} = 2.5\angle 36.9^\circ \text{ (k}\Omega\text{)}$$

Convert to Polar

Example: RLC Circuit

Find \bar{I}

$$\bar{V}_s = \bar{I} \cdot Z_{eq} \quad \left\{ \begin{array}{l} \text{Ohm's Law} \end{array} \right.$$

$$\bar{I} = \frac{\bar{V}_s}{Z_{eq}} = \frac{40 \angle -90^\circ}{2.5 \angle 36.9^\circ} \left(\frac{V}{k\Omega} \right)$$

$$\bar{I} = 16 \angle -126.9^\circ (mA) \quad \left\{ \begin{array}{l} \text{Phasor} \end{array} \right.$$

Plug in numbers

$$i(t) = 16 \cos(3000t - 126.9^\circ) (mA)$$

$$\left\{ \begin{array}{l} \bar{V}_s = 40 \angle -90^\circ (V) \\ Z_{eq} = 2.5 \angle 36.9^\circ (k\Omega) \end{array} \right. \quad \left\{ \begin{array}{l} \text{Found this} \\ \text{so far} \end{array} \right.$$

Note: Phase shift between \bar{I} and \bar{V}


$$\bar{I} = 16 \angle -126.90$$

$$\bar{V}_s = 40 \angle -90^\circ$$

- V and I Out of Phase 36.9°
- Due to Impedance of Circuit

Time domain

Example: Find \bar{I}_c (Contd.)

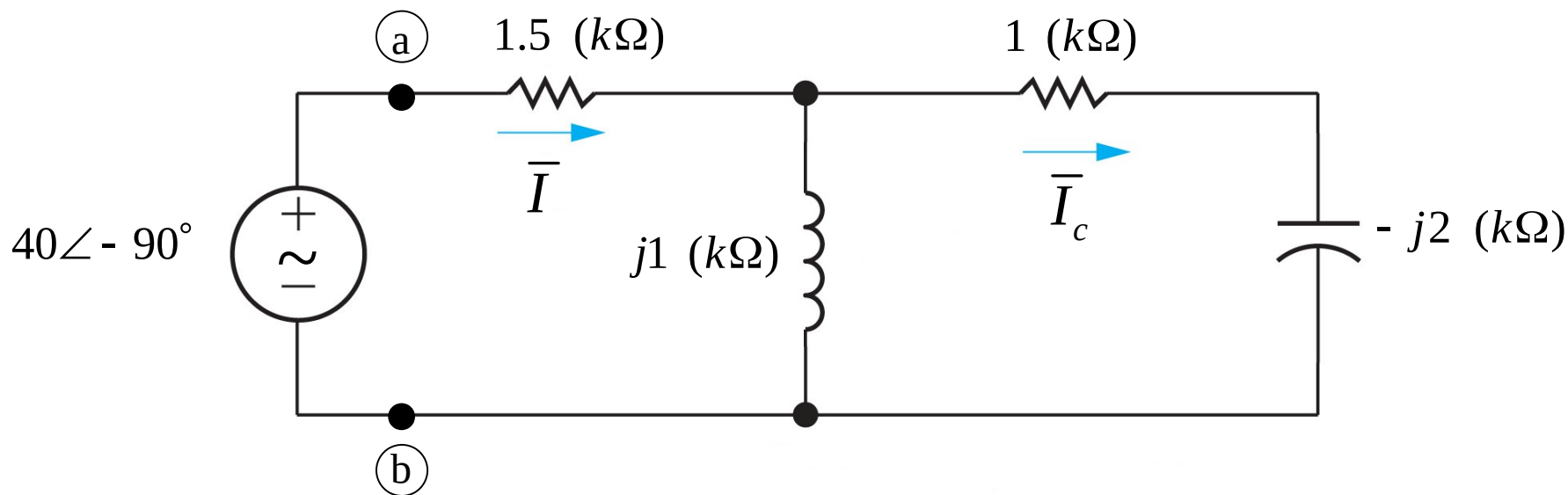

$$\bar{I} = 16\angle -126.9^\circ$$

From Previous slide

$$\bar{I}_c = \frac{j1}{j1 + 1 - j2} \bar{I}$$

Current Division

Example (Contd.)

$$\bar{I}_c = \frac{j1}{1-j} \cdot \bar{I} = \frac{-1+j}{2} \cdot \bar{I} \quad \left\{ \begin{array}{l} \text{From Previous Slide} \end{array} \right.$$


$$\bar{I}_c = 16 \angle -126.9^\circ (-1+j) (1/2) = 8 \angle -126.9^\circ [-1+j] \quad \left\{ \begin{array}{l} \text{Plug in numbers} \end{array} \right.$$

$$\bar{I}_c = 8 \angle -126.9^\circ \sqrt{2} \angle 135^\circ \quad \left\{ \begin{array}{l} \text{Caution} \end{array} \right.$$


$$\bar{I}_c = 8\sqrt{2} \angle (-126.9 + 135)^\circ (mA) \quad \left\{ \begin{array}{l} \text{Simplify} \end{array} \right.$$

$$\bar{I}_c = 11.31 \angle 8.1^\circ \quad \left\{ \begin{array}{l} \text{Phasor} \end{array} \right.$$
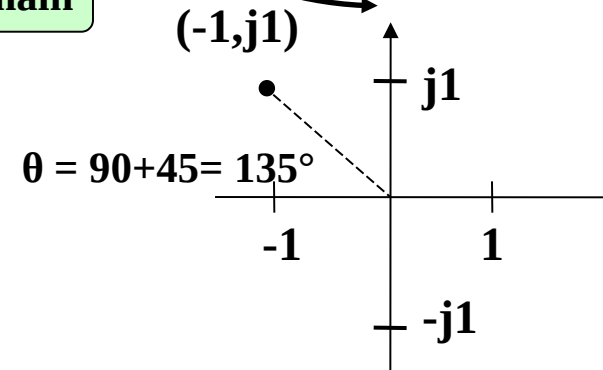
$$i_c(t) = 11.31 \cos(3000t + 8.1^\circ) (mA) \quad \left\{ \begin{array}{l} \text{Time Domain} \end{array} \right.$$



Example: Find $v_o(t)$

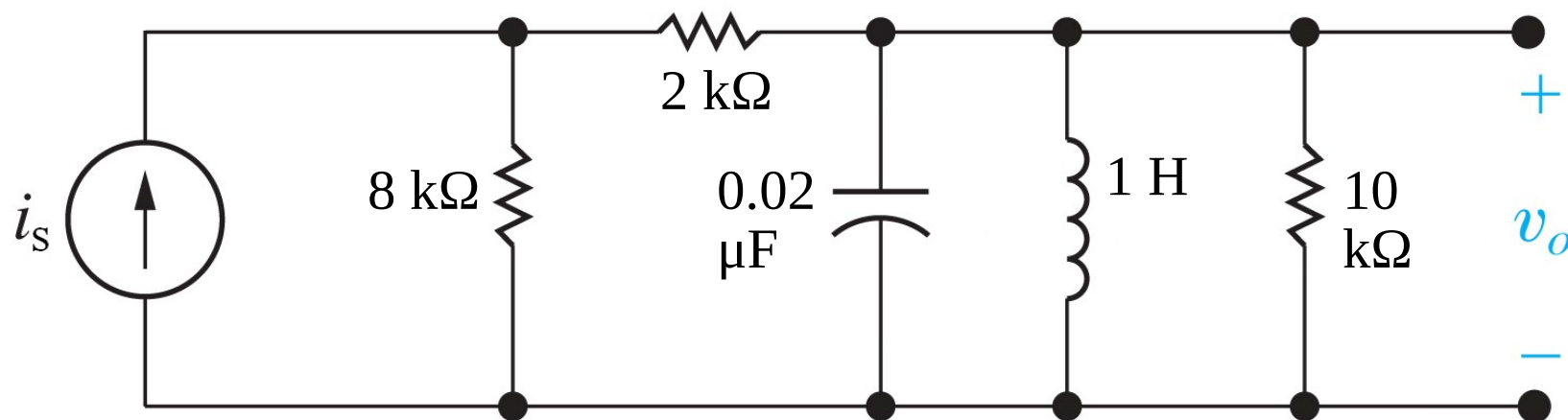

$$i_s = 12.5 \cos(5000t) \text{ (mA)}$$

$$\omega = 5000 \text{ rad/sec}$$

Given

$$Z_L = j\omega L = j(5000)(1) = j5000 \text{ (}\Omega\text{)}$$

Impedance


$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{5000} \cdot \frac{1}{0.02 \times 10^{-6}} = -j10^4 \text{ (}\Omega\text{)}$$

Impedance

$$\bar{I}_s = 12.5 \angle 0^\circ \text{ (mA)}$$

Phasor

Example (Contd.)

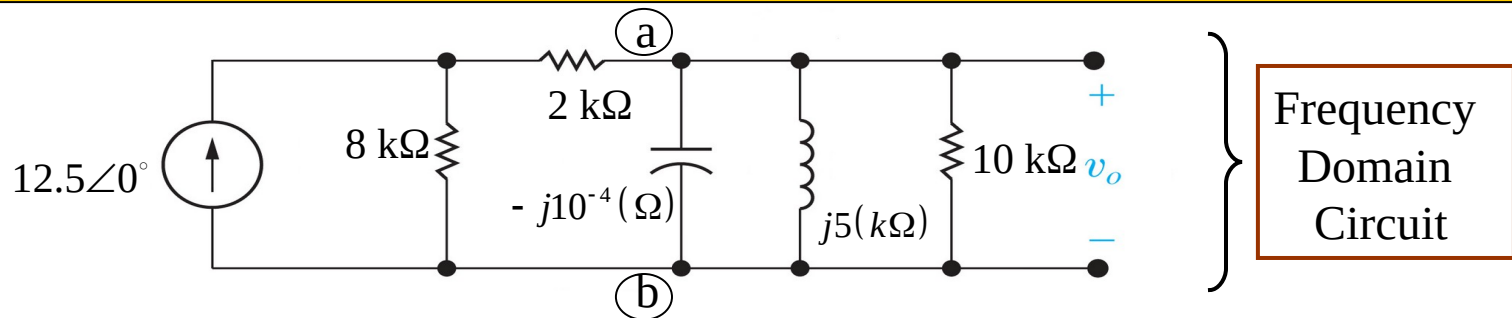

$$\bar{V}_s' = \bar{I}_s \cdot 8\text{ k}\Omega = (12.5\angle 0^\circ \text{ mA})(8 \times 10^3 \Omega)$$

$$\bar{V}_s' = 100\angle 0^\circ \text{ (V)}$$

Source transformation
at (a) and (b)

$$R_{eq} = 8\text{ k}\Omega + 2\text{ k}\Omega = 10(\text{ k}\Omega)$$


Series resistors

$$\bar{I}_s' = \frac{\bar{V}_s'}{R_{eq}} = \frac{100\angle 0^\circ}{10\text{ k}\Omega}$$

Convert back to current source


$$\bar{I}_s' = 10\angle 0^\circ \text{ (mA)}$$

$$10\angle 0^\circ \text{ (mA)}$$

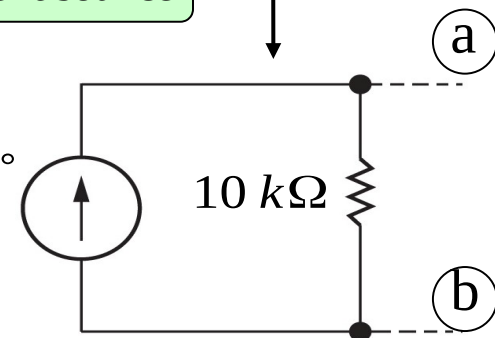

Example (Contd.)

Frequency Domain Equivalent Circuit

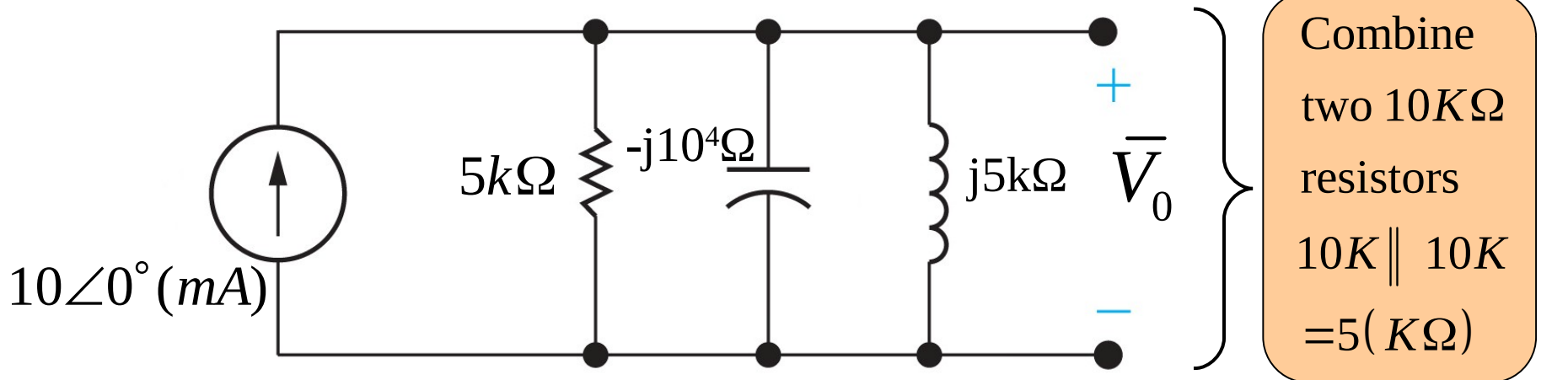

$$\bar{V}_0 = \bar{I} \cdot Z_{eq} = \frac{\bar{I}}{Y_{eq}}$$

Use admittance
for
parallel circuit

$$Y = \frac{1}{Z}$$

$$Y_{eq} = \frac{1}{5K} + \frac{1}{-j10^4} + \frac{1}{j5 \times 10^3} = \frac{1}{5K} + j10^{-4} - j0.2 \times 10^{-3} \quad \left\{ \text{Find } Y_{eq} \right.$$

$$Y_{eq} = 2 \times 10^{-4} - j10^{-4} = 0.224 \angle -26.57^\circ (m\Omega^{-1}) \quad \left\{ \text{Simplify} \right.$$

Example (Contd.)

$$Y_{eq} = 2 \times 10^{-4} - j10^{-4} = 0.224 \angle -26.57^\circ (m\Omega^{-1}) \quad \left. \vphantom{Y_{eq}} \right\} \text{From previous slide}$$

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{0.224 \times 10^{-3}} \angle 26.57^\circ (\Omega) \quad \left. \vphantom{Z_{eq}} \right\} \text{Find } Z_{eq}$$


$$\bar{V}_0 = \bar{I} \cdot Z_{eq} \quad \left. \vphantom{\bar{V}_0} \right\} \text{Ohm's Law}$$

$$\bar{V}_0 = 10 \angle 0^\circ (mA) \cdot \left[\frac{1}{0.224 \times 10^{-3}} \angle 26.57^\circ \right] (\Omega) \quad \left. \vphantom{\bar{V}_0} \right\} \text{Plug in numbers}$$

$$\bar{V}_0 = 44.64 \angle 26.57^\circ \quad \left. \vphantom{\bar{V}_0} \right\} \text{Phasor}$$

$$v_0(t) = 44.64 \cos(5000t + 26.57^\circ) (V) \quad \left. \vphantom{v_0(t)} \right\} \text{Time Domain}$$

Example: Frequency Dependent Impedance

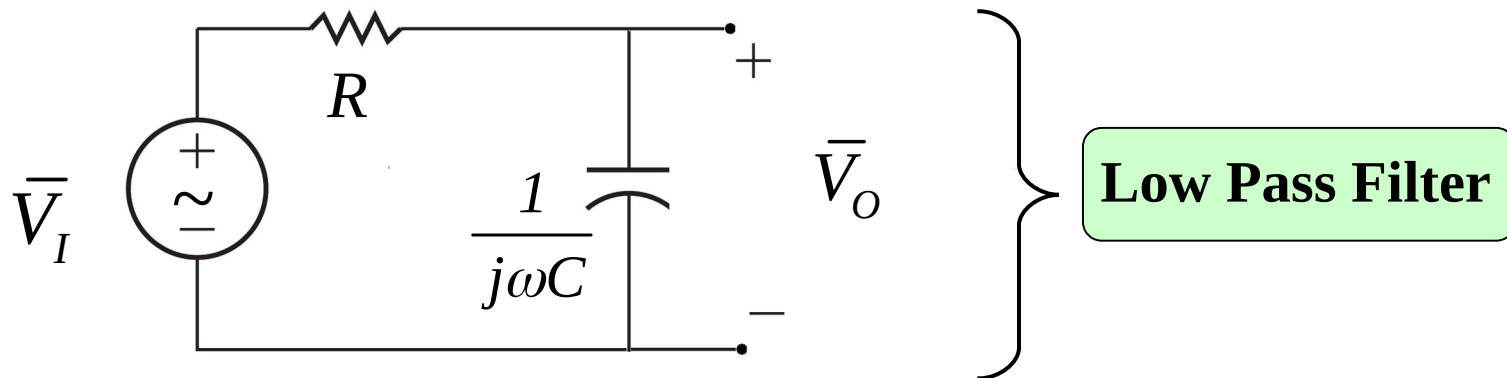

Find the Gain \equiv Transfer Function $\equiv \frac{\bar{V}_O}{\bar{V}_I} = \bar{A}_v$

$\bar{A}_v \equiv 1$ is the best we can hope for in a Passive Circuit.

Example: Frequency Dependent Impedance (Contd.)


Voltage Division:

$$\bar{V}_0 = \frac{1/j\omega C}{1/j\omega C + R} \cdot \bar{V}_I = \frac{1/j\omega C}{(1 + j\omega CR)/j\omega C} \cdot \bar{V}_I \quad \left. \vphantom{\bar{V}_0} \right\} \text{Simplify}$$

$$A_v = \frac{\bar{V}_0}{\bar{V}_I} = \frac{1}{1 + j\omega RC} \quad \left. \vphantom{A_v} \right\} \text{Transfer function}$$

$$\omega = 0 \Rightarrow A_v = 1$$
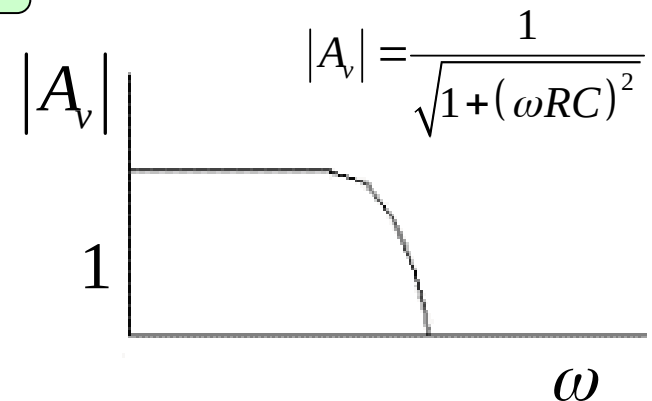
$$\omega \rightarrow \infty \Rightarrow A_v \rightarrow 0$$




Taking Output Across "R" \Rightarrow High Pass Filter

$$A_v = \frac{\bar{V}_R}{\bar{V}_I} = \frac{R}{R + 1/j\omega C}$$

High Pass Filter if we take V_0 across the Resistor

Node Voltage Analysis: Find $v_1(t)$

Frequency Domain

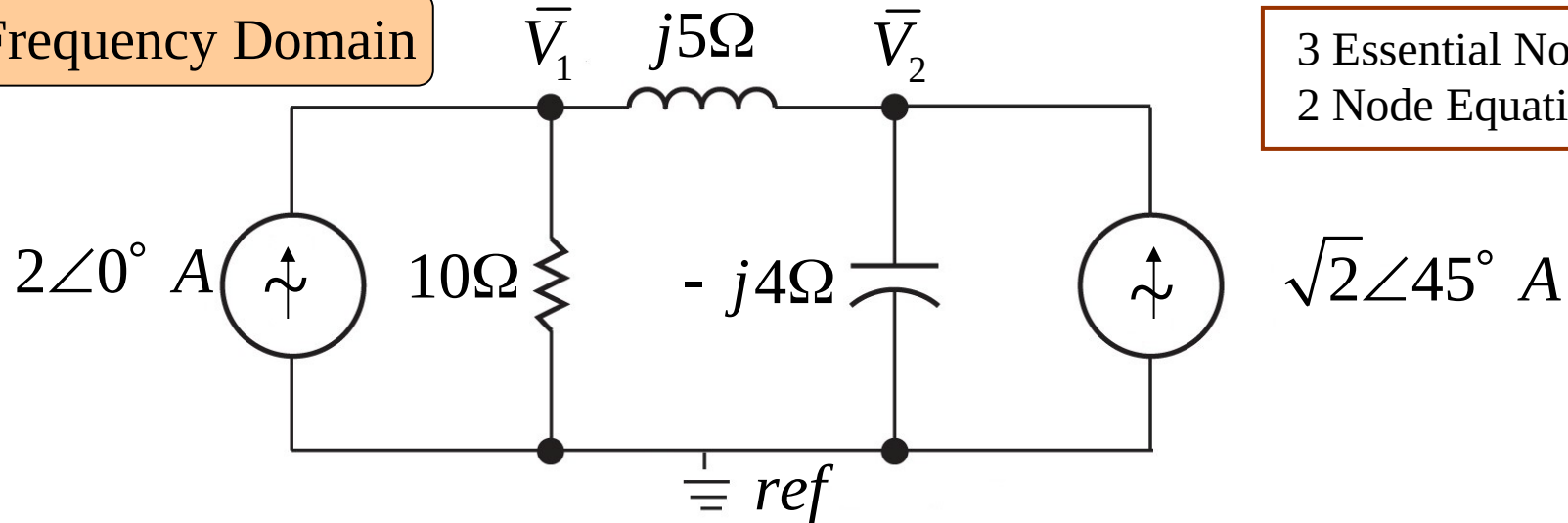


3 Essential Nodes
2 Node Equations

$$(1) \quad -2\angle 0^\circ + \frac{\bar{V}_1}{10} + \frac{\bar{V}_1 - \bar{V}_2}{j5} = 0 \quad \left. \vphantom{\frac{\bar{V}_1 - \bar{V}_2}{j5}} \right\} \text{Node equation for } \bar{V}_1$$

$$(1) \quad \bar{V}_1 \frac{j5}{10} + \bar{V}_1 - \bar{V}_2 = +2\angle 0^\circ (j5) = 2j5 = j10 \quad \left. \vphantom{\bar{V}_1 - \bar{V}_2} \right\} \text{Simplify}$$

$$(1) \quad \bar{V}_1(1 + j0.5) - \bar{V}_2 = j10$$

Node Voltage Analysis (Contd.)

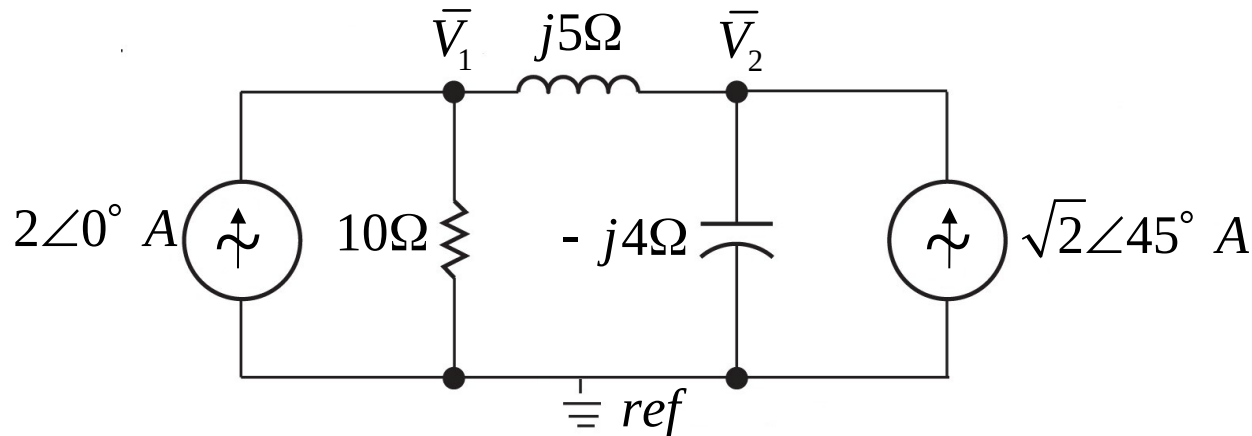

$$(2) \quad \frac{\bar{V}_2 - \bar{V}_1}{j5} + \frac{\bar{V}_2}{-j4} = \sqrt{2}\angle 45^\circ = 1 + j \quad \left. \vphantom{\frac{\bar{V}_2 - \bar{V}_1}{j5}} \right\} \text{Node equation for } \bar{V}_2$$

$$\begin{aligned} -j4(\bar{V}_2 - \bar{V}_1) + j5\bar{V}_2 &= 20 + j20 \\ j4(\bar{V}_1) + \bar{V}_2(j5 - j4) &= 20 + j20 \end{aligned} \quad \left. \vphantom{j4(\bar{V}_1) + \bar{V}_2(j5 - j4)} \right\} \text{Simplify}$$

$$(2) \quad \bar{V}_1(j4) + \bar{V}_2(j) = 20 + j20$$

$$(2) \quad j\bar{V}_2 = 20 + j20 - \bar{V}_1(j4) \quad \left. \vphantom{j\bar{V}_2} \right\} \text{Solve for } \bar{V}_2$$

$$\bar{V}_2 = \frac{20}{j} + 20 - \bar{V}_1 4 \quad \left. \vphantom{\bar{V}_2} \right\} \text{Simplify}$$

$$(2) \quad \bar{V}_2 = 20 - 4\bar{V}_1 - j20 \quad \xrightarrow{\text{Plug (2) into (1)}} \bar{V}_1(1 + j0.5) - 20 + 4\bar{V}_1 + j20 = j10$$

Node Voltage Analysis (Contd.)

$$\bar{V}_1(1 + j0.5 + 4) = j10 - j20 + 20 \quad \left. \vphantom{\bar{V}_1(1 + j0.5 + 4)} \right\} \text{From previous slide}$$


$$\bar{V}_1(5 + j0.5) = 20 - j10 \quad \left. \vphantom{\bar{V}_1(5 + j0.5)} \right\} \text{Simplify}$$

$$\bar{V}_1 = \frac{20 - j10}{5 + j0.5} = \frac{22.36 \angle -26.57^\circ}{5.02 \angle 5.71^\circ} \quad \left. \vphantom{\bar{V}_1 = \frac{20 - j10}{5 + j0.5}} \right\} \text{Solve for } \bar{V}_1$$

$$\bar{V}_1 = 4.45 \angle -32.28^\circ \quad \left. \vphantom{\bar{V}_1 = 4.45 \angle -32.28^\circ} \right\} \text{Phasor}$$

$$v_1(t) = 4.45 \cos(\omega t - 32.28^\circ) \text{ (V)} \quad \left. \vphantom{v_1(t) = 4.45 \cos(\omega t - 32.28^\circ)} \right\} \text{Time domain}$$

Mesh Analysis: Find \bar{I}

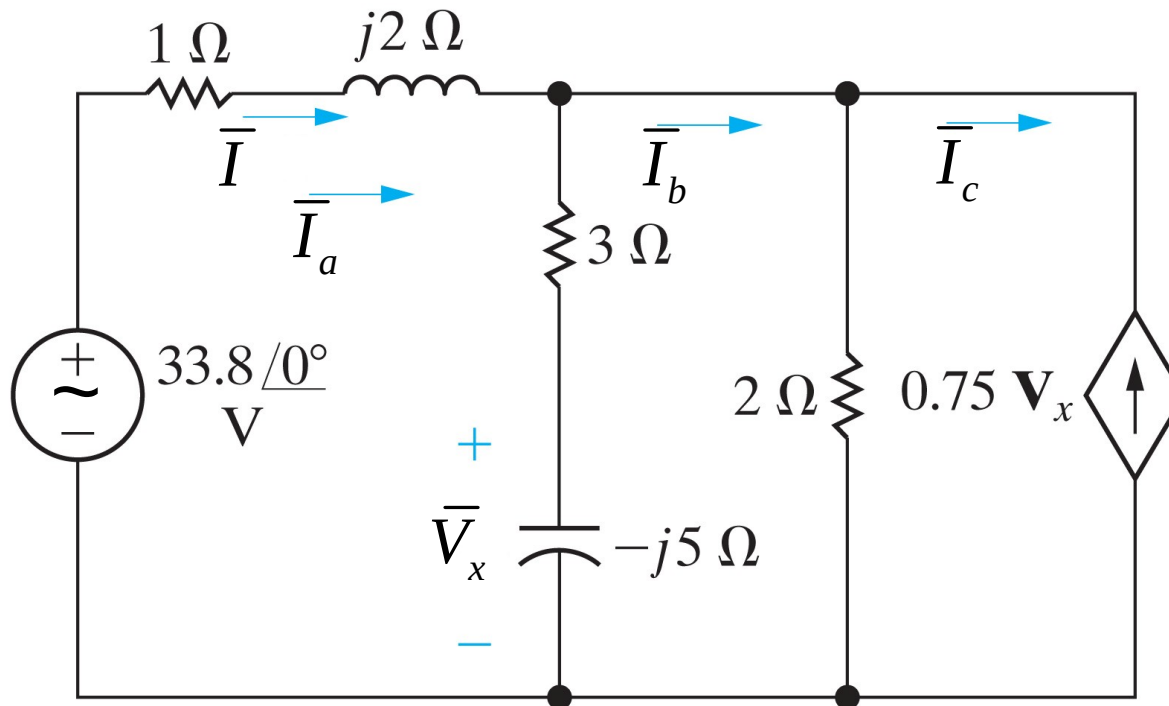


Note $\bar{I} \equiv \bar{I}_a$

$$(a) \quad 33.8\angle 0^\circ = (1 + j2)\bar{I}_a + (3 - j5)(\bar{I}_a - \bar{I}_b) \quad \left. \vphantom{33.8\angle 0^\circ} \right\} \text{Mesh a}$$

$$(1 + j2 + 3 - j5)\bar{I}_a - (3 - j5)\bar{I}_b = 33.8 \quad \left. \vphantom{(1 + j2 + 3 - j5)\bar{I}_a} \right\} \text{Simplify}$$

$$(a) \quad (4 - j3)\bar{I}_a - (3 - j5)\bar{I}_b = 33.8$$

Mesh Analysis (Contd.)

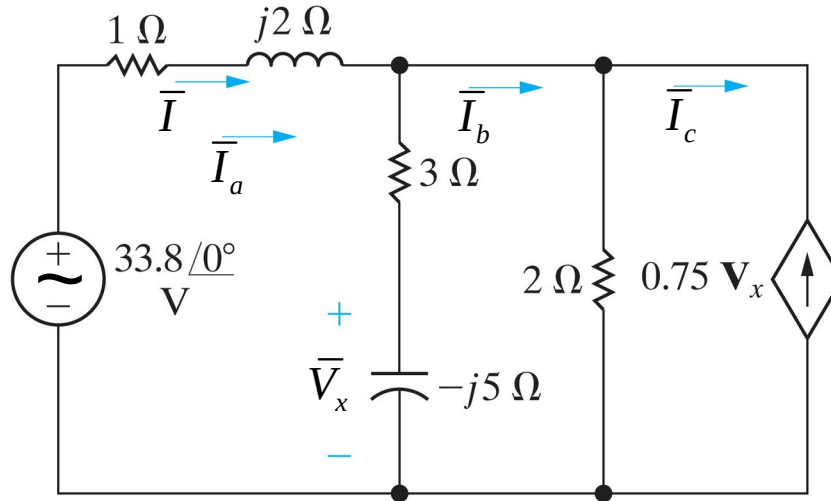

$$\begin{aligned}
 (b) \quad & (3 - j5)(\bar{I}_b - \bar{I}_a) + 2(\bar{I}_b - \bar{I}_c) = 0 & \left. \begin{array}{l} \text{Mesh b} \\ \text{Simplify} \end{array} \right\} \\
 & - (3 - j5)\bar{I}_a + (3 - j5 + 2)\bar{I}_b - 2\bar{I}_c = 0
 \end{aligned}$$

$$(b) \quad - (3 - j5)\bar{I}_a + (5 - j5)\bar{I}_b - 2\bar{I}_c = 0$$

$$(c) \quad \bar{I}_c = -0.75\bar{V}_x = -0.75[-j5(\bar{I}_a - \bar{I}_b)] \quad \left. \begin{array}{l} \text{Constraint} \end{array} \right\}$$

$$(c) \quad \bar{I}_c = j3.75(\bar{I}_a - \bar{I}_b)$$

$$\bar{V}_x = -j5(\bar{I}_a - \bar{I}_b)$$

Mesh Analysis (Contd.)

$$-(3 - j5)\bar{I}_a + (5 - j5)\bar{I}_b - j7.5(\bar{I}_a - \bar{I}_b) = 0 \quad \left. \vphantom{-(3 - j5)\bar{I}_a} \right\} \begin{array}{l} \text{Substitute (c)} \\ \text{into (b)} \end{array}$$

$$(b) \quad -(3 + j2.5)\bar{I}_a + (5 + j2.5)\bar{I}_b = 0 \quad \left. \vphantom{-(3 + j2.5)\bar{I}_a} \right\} \begin{array}{l} \text{Simplify} \end{array}$$


$$(a) \quad (4 - j3)\bar{I}_a - (3 - j5)\bar{I}_b = 33.8$$

Solve two Equations for two unknowns

Result:

$$\bar{I} = \bar{I}_a = 29.07 \angle 3.95^\circ \text{ (A)}$$

Example Using Mesh Current

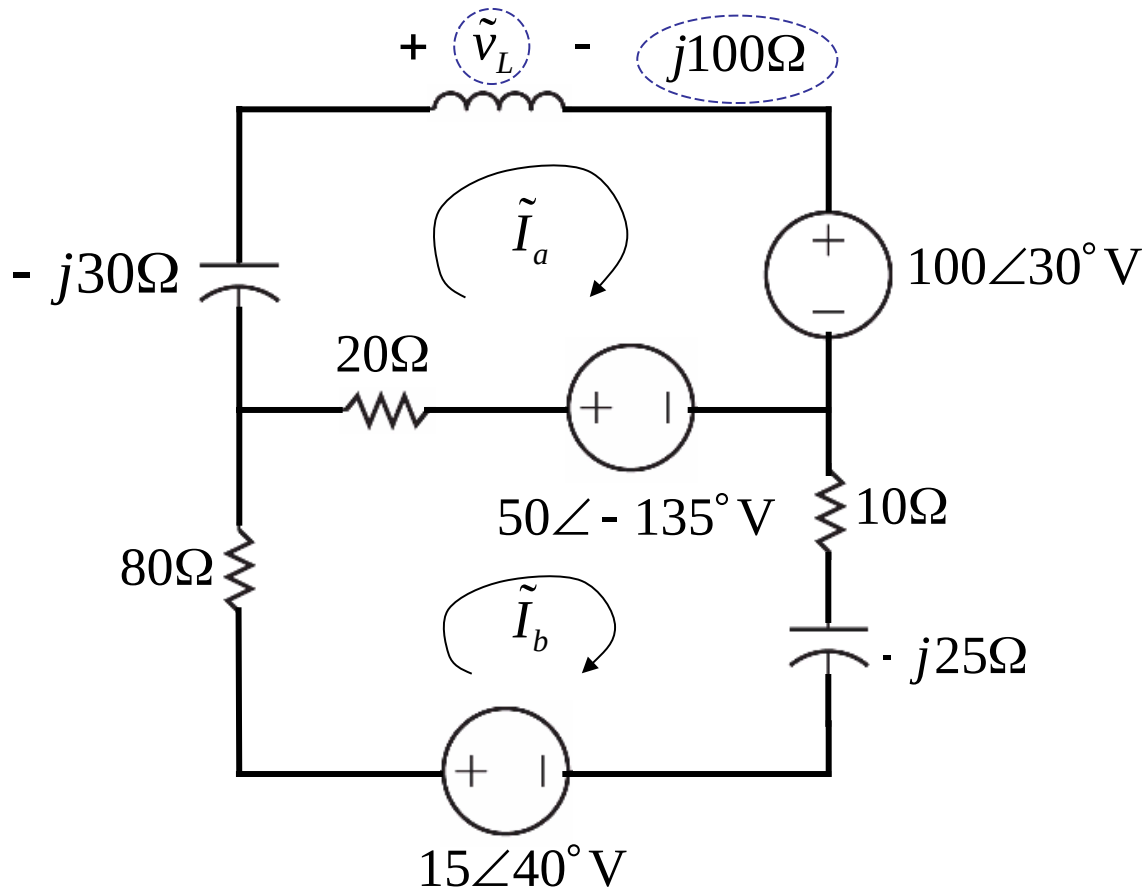

Find Mesh Currents

\tilde{I}_a , \tilde{I}_b , and \tilde{v}_L .

Can You Find L ?

No

$$Z_L = j\omega L = j100$$

$$L = \frac{j100}{j\omega}$$

Side
Note


Note: $Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$

$$Z_L = j\omega L$$

Need

$$L = \frac{100}{\omega} \quad f = \frac{\omega}{2\pi}$$

Example Using Mesh Current (Contd.)

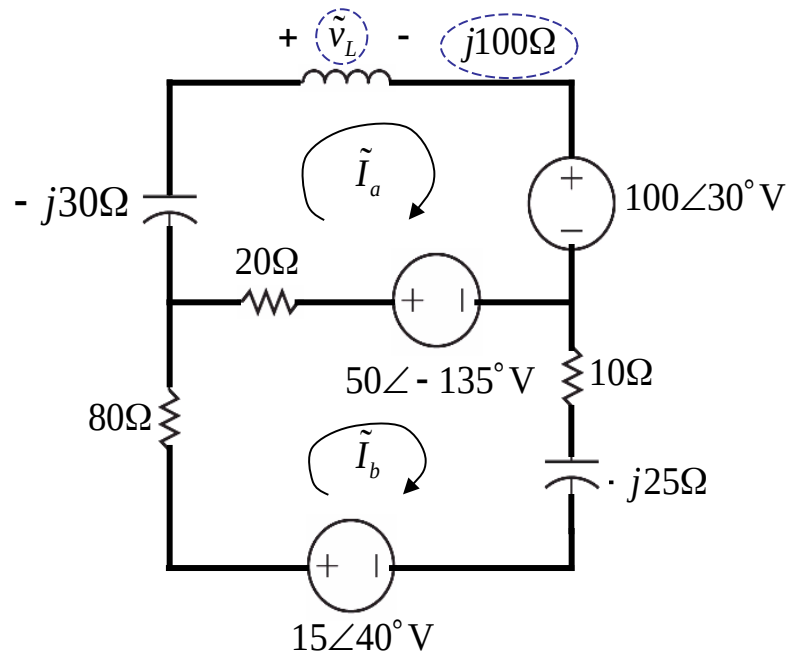

Mesh (a)

$$\begin{aligned} \text{(a)} \quad & \tilde{I}_a(-j30) + \tilde{I}_a(j100) + 100\angle 30^\circ - 50\angle -135^\circ + (\tilde{I}_a - \tilde{I}_b)(20) = 0 \\ \text{(b)} \quad & \tilde{I}_b(80) + (\tilde{I}_b - \tilde{I}_a)(20) + 50\angle -135^\circ + \tilde{I}_b(10 - j25) - 15\angle 40^\circ = 0 \end{aligned}$$

Mesh (b)

Example Using Mesh Current (Contd.)

$$\textcircled{a} \quad \tilde{I}_a(-j30 + j100 + 20) + \tilde{I}_b(-20) = (50\angle -135^\circ - 100\angle 30^\circ)$$

$$(20 + j70)\tilde{I}_a - 20\tilde{I}_b = 148.9\angle -145^\circ \quad \left. \vphantom{(20 + j70)\tilde{I}_a - 20\tilde{I}_b = 148.9\angle -145^\circ} \right\} \text{Convert to Rectangular to Add}$$

$$\textcircled{b} \quad -20\tilde{I}_a + (80 + 20 + 10 - j25)\tilde{I}_b = (15\angle 40^\circ - 50\angle -135^\circ)$$

$$-20\tilde{I}_a + (110 - j25)\tilde{I}_b = 64.96\angle 43.85^\circ \quad \left. \vphantom{-20\tilde{I}_a + (110 - j25)\tilde{I}_b = 64.96\angle 43.85^\circ} \right\} \text{Convert to Rectangular to Add}$$


**Matrix
Form**

$$\begin{bmatrix} (20 + j70) & -20 \\ -20 & (110 - j25) \end{bmatrix} \begin{bmatrix} \tilde{I}_a \\ \tilde{I}_b \end{bmatrix} = \begin{bmatrix} 148.9\angle -145^\circ \\ 64.96\angle 43.85^\circ \end{bmatrix} \quad \left. \vphantom{\begin{bmatrix} (20 + j70) & -20 \\ -20 & (110 - j25) \end{bmatrix} \begin{bmatrix} \tilde{I}_a \\ \tilde{I}_b \end{bmatrix} = \begin{bmatrix} 148.9\angle -145^\circ \\ 64.96\angle 43.85^\circ \end{bmatrix}} \right\} \begin{array}{l} \text{Two equations} \\ \text{Two unknowns} \end{array}$$


$$\rightarrow \tilde{I}_a = 1.943\angle -136.7^\circ \text{ (A)} \quad \tilde{I}_b = 0.6535\angle 88.2^\circ \text{ (A)} \quad \left. \vphantom{\tilde{I}_a = 1.943\angle -136.7^\circ \text{ (A)} \quad \tilde{I}_b = 0.6535\angle 88.2^\circ \text{ (A)}} \right\} \text{Solution}$$

$$\tilde{V}_L = \tilde{I}_a Z_L = \underbrace{(1.943\angle 136.7^\circ)}_{\tilde{I}_a} \underbrace{(j100)}_{Z_L} = 194.3\angle -133^\circ \text{ (V)} \quad \left. \vphantom{\tilde{V}_L = \tilde{I}_a Z_L = 194.3\angle -133^\circ \text{ (V)}} \right\} \text{Ohm's Law}$$

Thevenin and Norton Equivalent Circuits

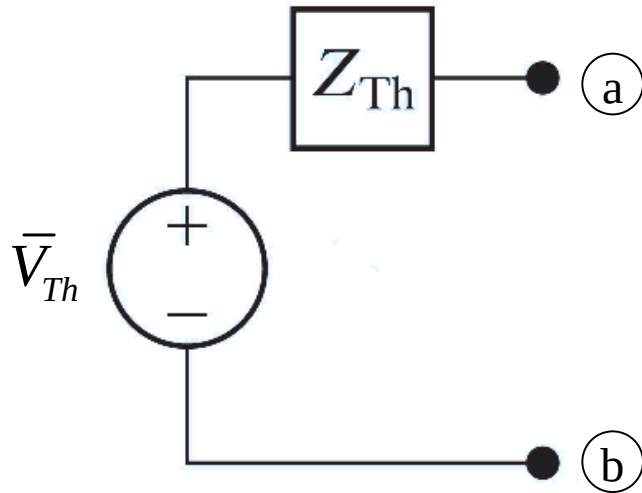


Thevenin
Equivalent

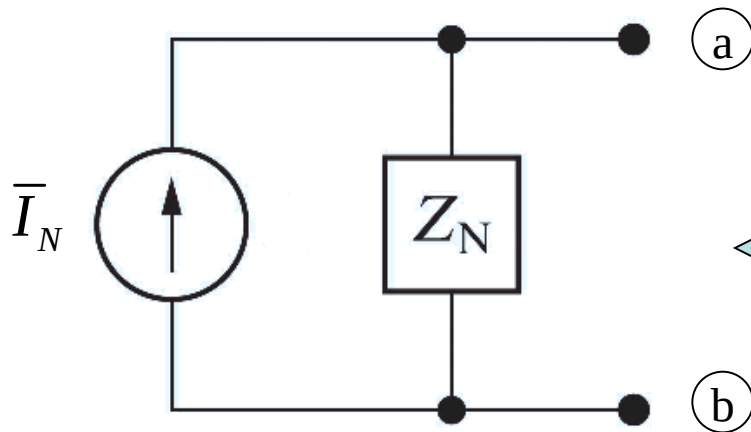

Norton
Equivalent

Example: Find Thevenin Equivalent

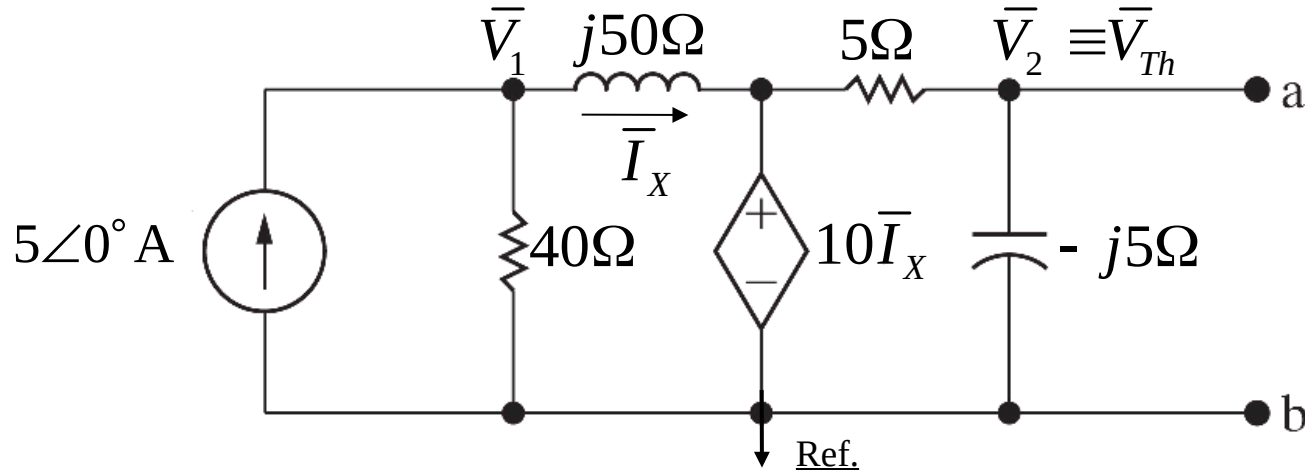

$$\bar{V}_{Th} = \bar{V}_{oc} = \bar{V}_{ab}$$

Use Node Voltages ; only 2 Unknown: \bar{V}_1 , and \bar{V}_{Th}

Write equation for \bar{I}_x in terms of \bar{V}_1 and \bar{V}_{Th}


Example (Contd.)

Node \bar{V}_1 $-5\angle 0^\circ + \frac{\bar{V}_1}{40} + \frac{\bar{V}_1 - 10\bar{I}_x}{j50} = 0$

① $\bar{V}_1 [0.025 - j0.02] + 0.2j\bar{I}_x = 5$

Node \bar{V}_{Th} $\frac{\bar{V}_{Th} - 10\bar{I}_x}{5} + \frac{\bar{V}_{Th}}{-j5} = 0$ $5\angle 0^\circ \text{ A}$

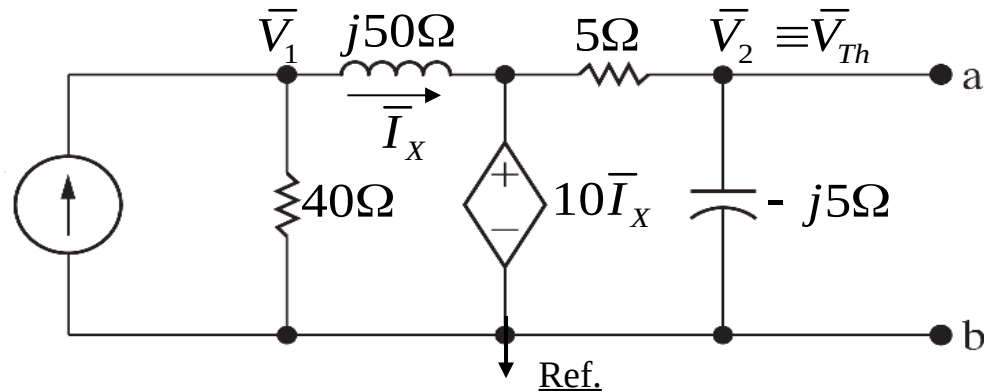② $\bar{V}_{Th} [0.2 + j0.2] - 2\bar{I}_x = 0$



$j50\bar{I}_x = \bar{V}_1 - 10\bar{I}_x$ } Find another equation for \bar{I}_x

$\bar{I}_x [j50 + 10] = \bar{V}_1$ } Solve for \bar{I}_x


$\bar{I}_x = \frac{\bar{V}_1}{10 + j50}$ } Substitute into ① and ②
Solve for $\bar{V}_{Th} = 20\angle -90^\circ \text{ (V)}$

Example (Contd.)

Find Z_{Th}

- Open Independent Current Source

- Apply Test Voltage at a – b.

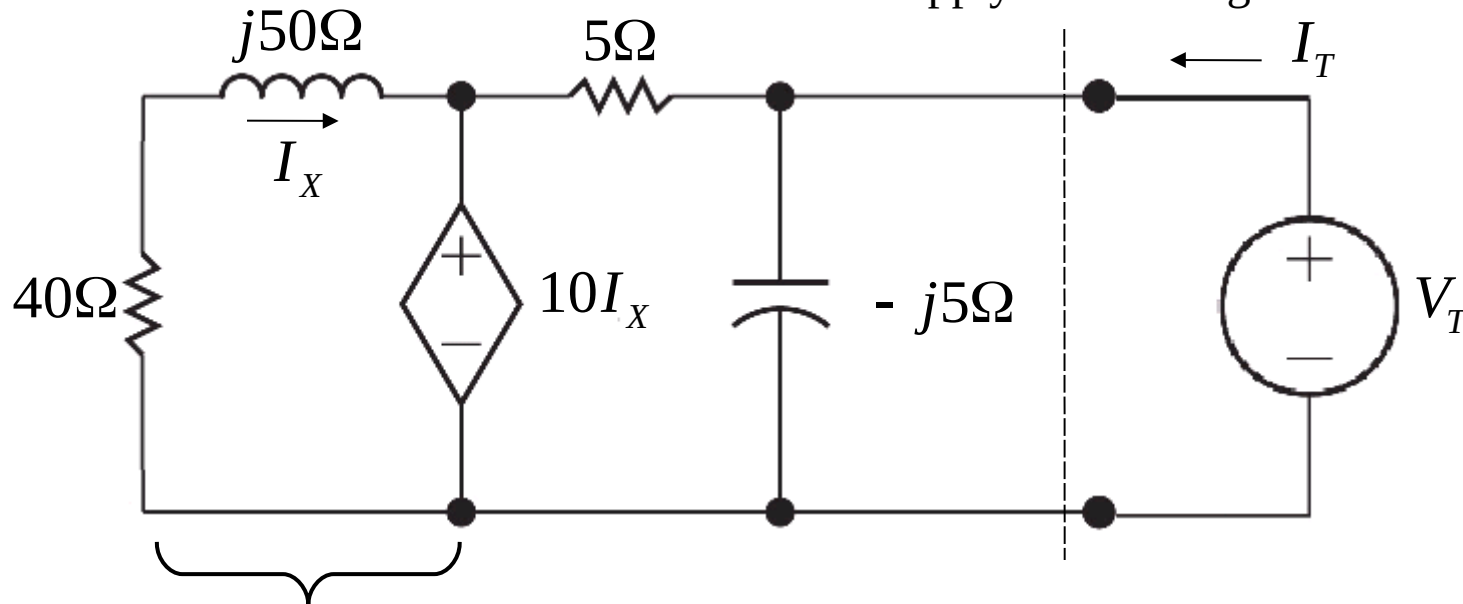


Redraw
circuit with
5 amp
source
open

Write
an equation
for I_X

$$\left\{ \begin{aligned} 10\bar{I}_X &= -\bar{I}_X [40 + j50] \end{aligned} \right\} \text{KVL}$$

$$I_X = 0 \Rightarrow 10I_X = 0$$


Example (Contd.)

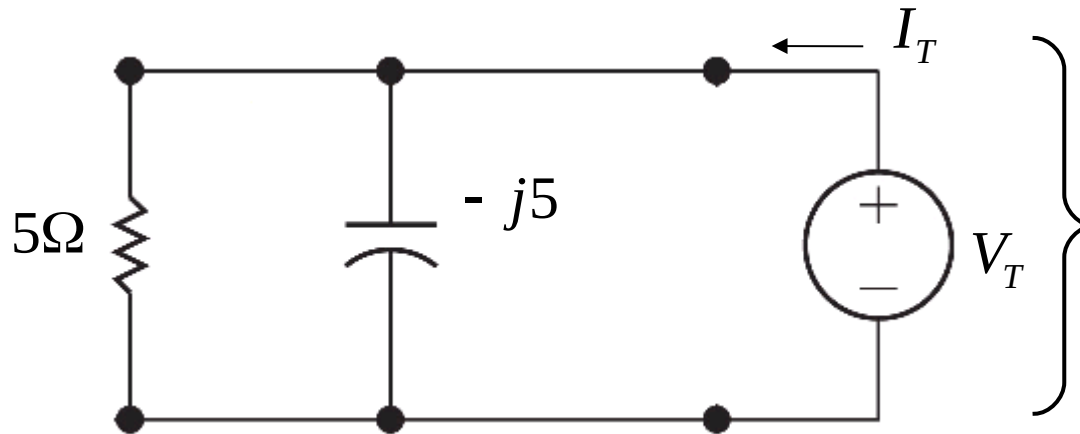

Redraw circuit with dependent source shorted

$$\begin{array}{l}
 \text{KCL} \left\{ I_T = \frac{V_T}{5} + \frac{V_T}{-j5} \right. \\
 \text{Solve for } I_T \left\{ \begin{array}{l} I_T = V_T \left[\frac{1}{5} + \frac{1}{-j5} \right] \\ I_T = V_T \left[\frac{-j5 + 5}{-j25} \right] \end{array} \right.
 \end{array}
 \quad \nearrow \quad
 \begin{array}{l}
 Z_{Th} = \frac{V_T}{I_T} = \frac{-j25}{5 - j5} = \frac{-j5}{1 - j} \quad \left\{ \text{Solve for } Z_{Th} \right. \\
 Z_{Th} = \frac{5}{+j(1 - j)} = \frac{5}{j + 1} \cdot \left(\frac{j - 1}{j - 1} \right) \quad \left\{ \text{Simplify} \right. \\
 Z_{Th} = \frac{5(j - 1)}{-2} = 2.5 - j2.5(\Omega)
 \end{array}$$

Example (Contd.)

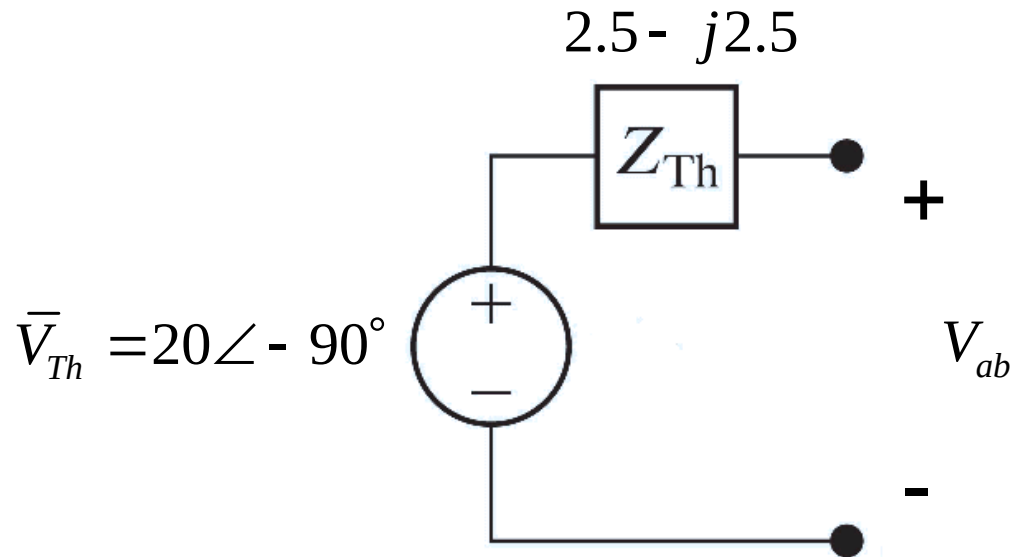


**Thevenin
Equivalent**

Phasor Diagrams

“For Visualization”

Magnitude \angle Phase Angle



“Graphs”

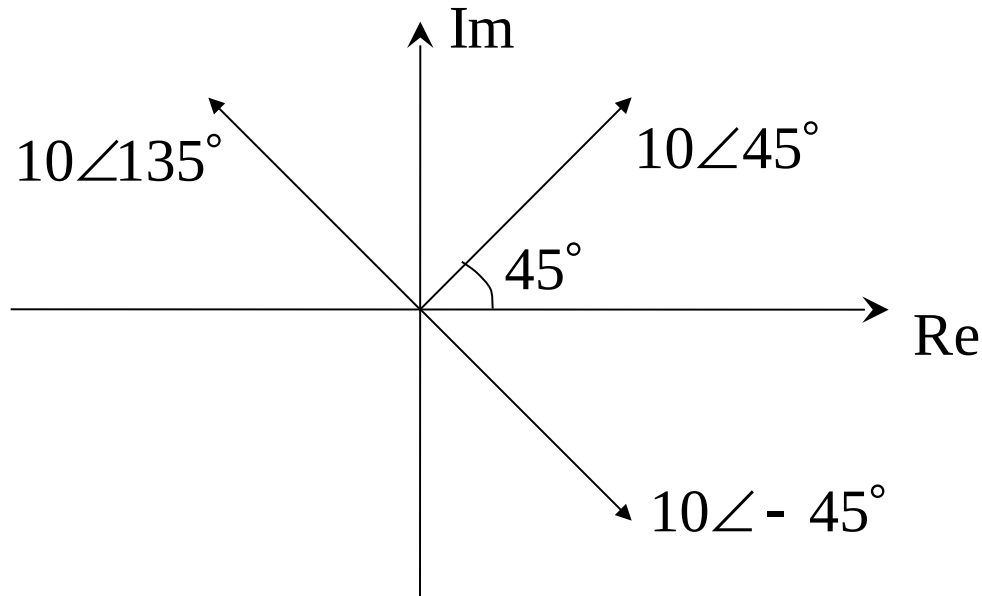

Can then plot \bar{I} and \bar{V} on Complex Planes

Phasor Diagrams

(Contd.)

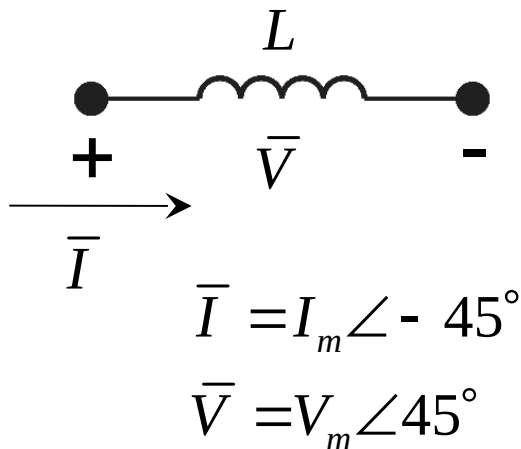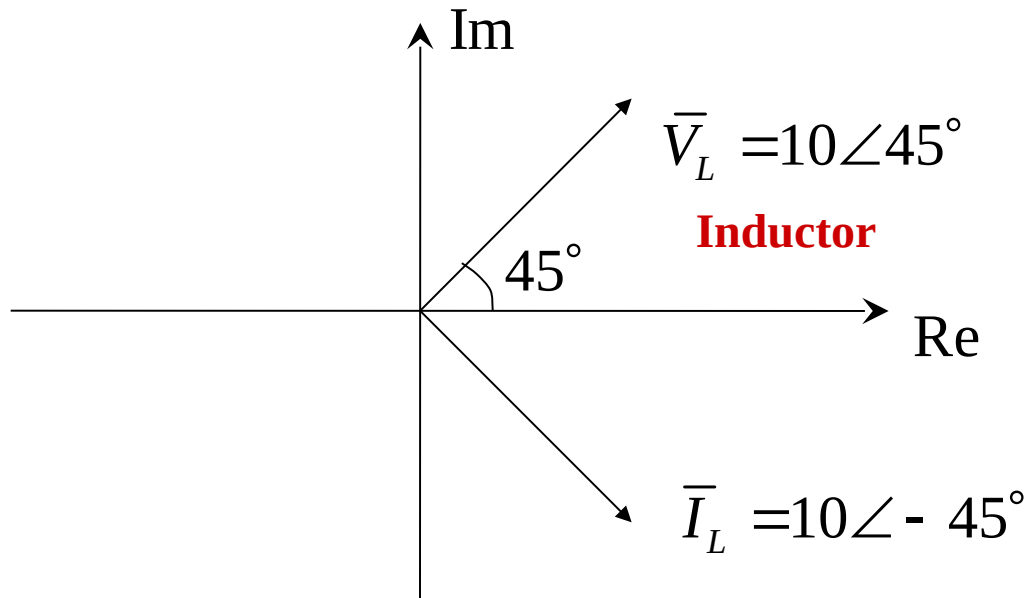


If $\bar{V} = V_m \angle 45^\circ$

$$\bar{I} = \frac{\bar{V}}{j\omega L} = \frac{V_m}{\omega L} \angle 45^\circ (-j) = \frac{V_m}{\omega L} \angle -45^\circ$$

I_m

Voltage "Leads" Current.

Example

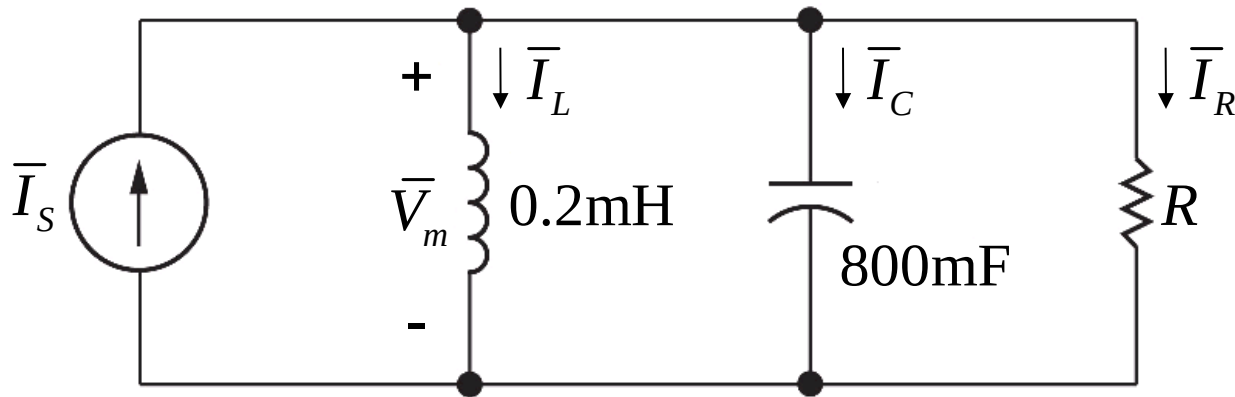

- ① Assume $\omega = 5000 \text{ rad/s}$
- ② Assume $\bar{V}_m = V_m \angle 0^\circ$

Choose R such that \bar{I}_R lags \bar{I}_S by $\angle 45^\circ$

$$\bar{I}_S = \bar{I}_L + \bar{I}_C + \bar{I}_R \quad \left. \vphantom{\bar{I}_S = \bar{I}_L + \bar{I}_C + \bar{I}_R} \right\} \text{KCL}$$

Construct Phasor Diagram of \bar{I}_S by plotting \bar{I}_L , \bar{I}_C , and \bar{I}_R

$$\textcircled{1} \quad \bar{I}_L = \frac{\bar{V}_m}{Z_L} = \frac{V_m \angle 0^\circ}{j\omega L} = \frac{V_m \angle 0^\circ}{j(5000)(0.2 \times 10^{-3})} \quad \left. \vphantom{\bar{I}_L = \frac{\bar{V}_m}{Z_L}} \right\} \text{Ohm's Law}$$


$$\bar{I}_L = V_m \angle -90^\circ \equiv -jV_m$$

Example (Contd.)

$$\textcircled{2} \quad \bar{I}_C = \frac{\bar{V}_m}{Z_L} = \frac{V_m \angle 0^\circ}{\frac{1}{j\omega C}} = j(5000)(800 \times 10^{-6})V_m \angle 0^\circ \quad \left. \vphantom{\bar{I}_C} \right\} \text{Ohm's Law}$$

$$= j4V_m \angle 0^\circ \quad \bar{I}_C = 4V_m \angle 90^\circ = j4V_m$$
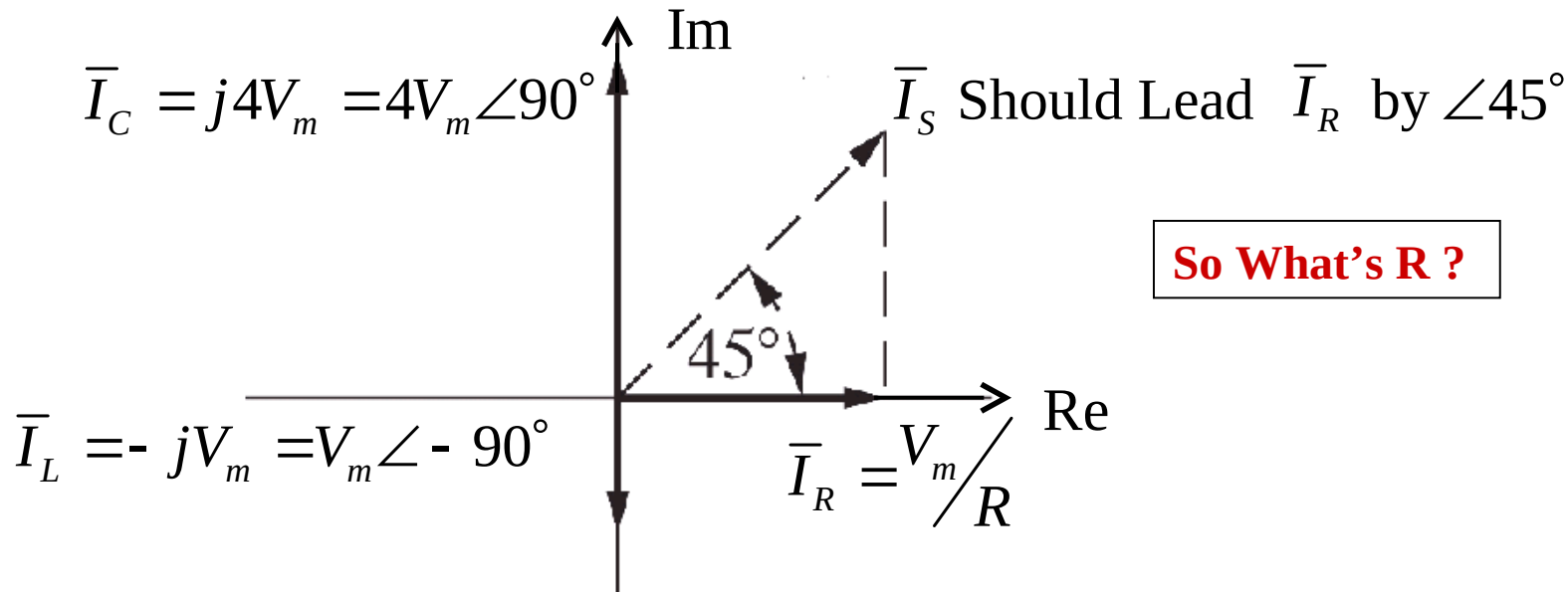
$$\textcircled{3} \quad \bar{I}_R = \frac{V_m \angle 0^\circ}{R} = \frac{V_m}{R} \angle 0^\circ \quad \left. \vphantom{\bar{I}_R} \right\} \text{Ohm's Law}$$




Example (Contd.)

$$\bar{I}_s = \bar{I}_L + \bar{I}_C + \bar{I}_R \quad \left. \vphantom{\bar{I}_s} \right\} \text{KCL}$$

$$\bar{I}_s = \frac{V_m}{R} + j3V_m \quad \left. \vphantom{\bar{I}_s} \right\} \text{Plug in values}$$

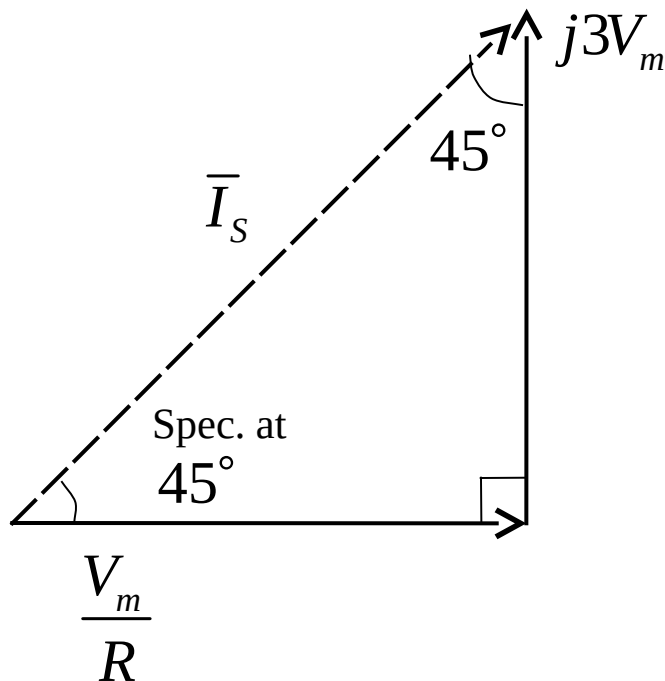Construct \bar{I}_s by “Vector” or Phasor Sum



Isosceles Triangle \Rightarrow 2 Sides Are Equal

$$\boxed{\boxed{|\text{Re}| = |\text{Im}|} \Rightarrow \left| \frac{V_m}{R} \right| = |j3V_m|}$$

$$\frac{V_m}{R} = 3V_m \Rightarrow R = \frac{1}{3}(\Omega)$$