

## EXAMPLE 9-17

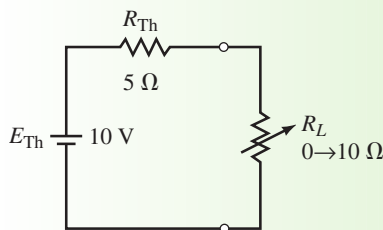


FIGURE 9-72



Use PSpice to input the circuit of Figure 9-72 and use the Probe postprocessor to display output voltage, current, and power as a function of load resistance.

**Solution** The circuit is constructed as shown in Figure 9-73.

- Double-click on each resistor in the circuit and change the Reference cells to RTH and RL. Click on Apply to accept the changes.
- Double-click on the value for RL and enter **{Rx}**. Place the PARAM part adjacent to RL. Use the *Property Editor* to assign a default value of **10 Ω** to Rx. Click on Apply. Have the display show the name and value and then exit the *Property Editor*. If necessary, refer to Example 7-15 for the complete procedure on how to assign parameters to a circuit component.

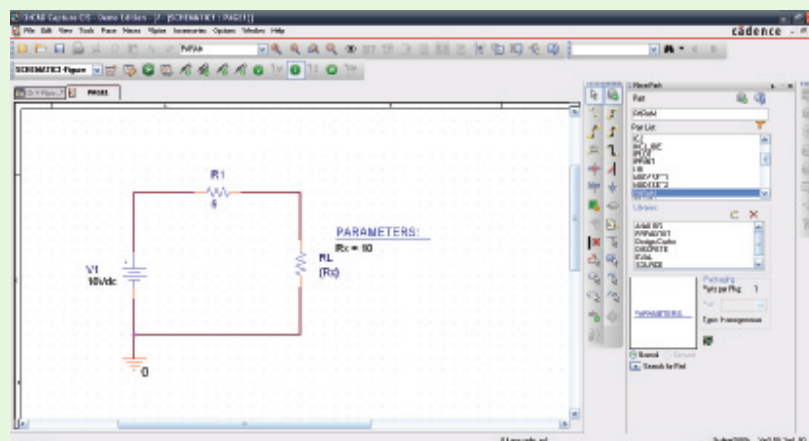


FIGURE 9-73

- Adjust the *Simulation Settings* to result in a dc sweep of the load resistor from **0.1 Ω** to **10 Ω** in **0.1 Ω** increments.
- Click on the *Run* icon once the circuit is complete.
- Once the design is simulated, you will see a blank screen with the abscissa (horizontal axis) showing RX scaled from 0 to 10 Ω.
- Since we would like to have a simultaneous display of voltage, current, and power, it is necessary to do the following:

**To display  $V_L$ :** Click *Trace* and then *Add Trace*. Select **V(RL:1)**. Click *OK* and the load voltage will appear as a function of load resistance.

**To display  $I_L$ :** First add another axis by clicking on *Plot* and *Add Y Axis*. Next, click *Trace* and then *Add Trace*. Select **I(RL)**. Click *OK* and the load current will appear as a function of load resistance.

**To display  $P_L$ :** Add another Y axis. Click *Trace* and *Add Trace*. One method of showing power is to enter **W(RL)** and then click *OK*. The display will appear as shown in Figure 9-74. The color and line thickness of a trace can be changed by right-clicking anywhere on the desired trace and selecting *Trace Property*.

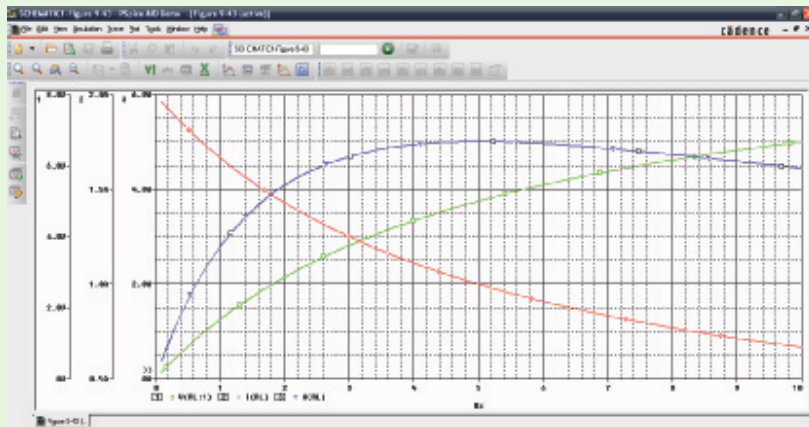


FIGURE 9-74

© Cengage Learning 2013

## PRACTICE PROBLEMS 8


Use PSpice to input the circuit of Figure 9-66. Use the Probe postprocessor to obtain voltage, current, and power for the load resistor as it is varied from 0 to 5 k $\Omega$ .

## Putting It into Practice

A simple battery cell (such as a D cell) can be represented as a Thévenin equivalent circuit as shown in the accompanying figure.

The Thévenin voltage represents the open-circuit (or unloaded) voltage of the battery cell, while the Thévenin resistance is the internal resistance of the battery. When a load resistance is connected across the terminals of the battery, the voltage  $V_{ab}$  will decrease due to the voltage drop across the internal resistor. By taking two measurements, it is possible to find the Thévenin equivalent circuit of the battery.

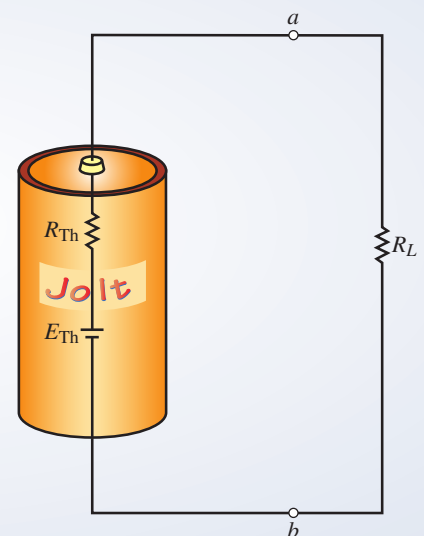When no load is connected between the terminals of the battery, the terminal voltage is found to be  $V_{ab} = 1.493$  V. When a resistance of  $R_L = 10.6$   $\Omega$  is connected across the terminals, the voltage is measured to be  $V_{ab} = 1.430$  V. Determine the Thévenin equivalent circuit of the battery. Use the measurements to determine the efficiency of the battery for the given load.



© Cengage Learning 2013

## Problems

## 9.1 Superposition Theorem

1. Given the circuit of Figure 9–75, use superposition to calculate the current through each of the resistors.
2. Use superposition to determine the voltage drop across each of the resistors of the circuit in Figure 9–76.
3. Use superposition to solve for the voltage  $V_a$  and the current  $I$  in the circuit of Figure 9–77.

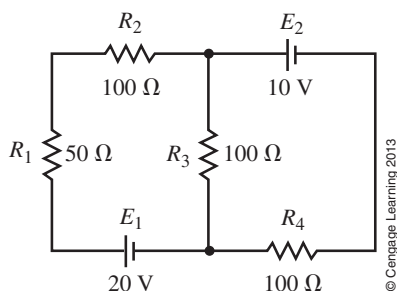


FIGURE 9–75

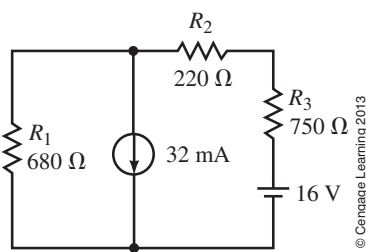


FIGURE 9–76

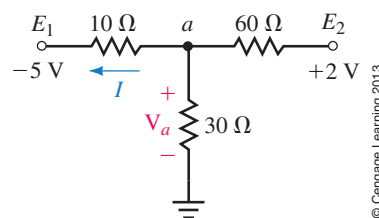


FIGURE 9–77

4. Using superposition, find the current through the 480-Ω resistor in the circuit of Figure 9–78.
5. Given the circuit of Figure 9–79, what must be the value of the unknown voltage source to ensure that the current through the load is  $I_L = 5$  mA as shown? Verify the results using superposition.
6. If the load resistor in the circuit of Figure 9–80 is to dissipate 120 W, determine the value of the unknown voltage source. Verify the results using superposition.

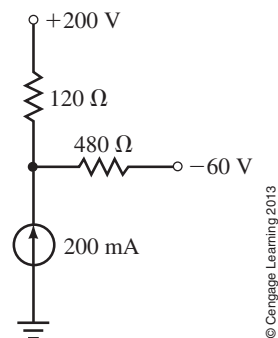


FIGURE 9–78

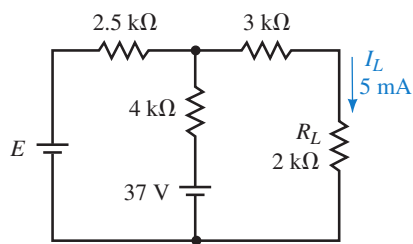


FIGURE 9–79

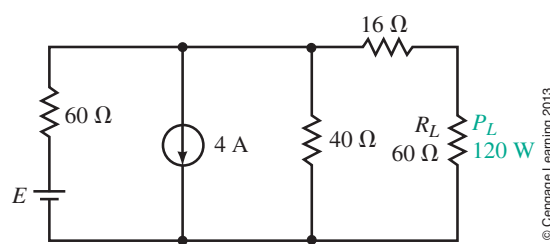


FIGURE 9–80

## 9.2 Thévenin's Theorem

7. Find the Thévenin equivalent external to  $R_L$  in the circuit of Figure 9–81. Use the equivalent circuit to find  $V_{ab}$ .
8. Repeat Problem 7 for the circuit of Figure 9–82.
9. Repeat Problem 7 for the circuit of Figure 9–83.
10. Repeat Problem 7 for the circuit of Figure 9–84.
11. Refer to the circuit of Figure 9–85:
  - a. Find the Thévenin equivalent circuit external to  $R_L$ .
  - b. Use the equivalent circuit to determine  $V_{ab}$  when  $R_L = 20 \Omega$  and when  $R_L = 50 \Omega$ .

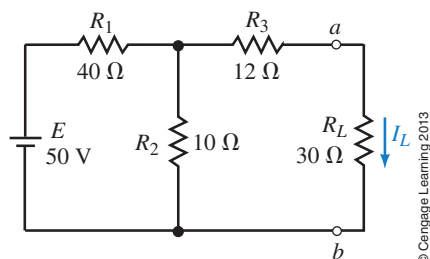


FIGURE 9-81

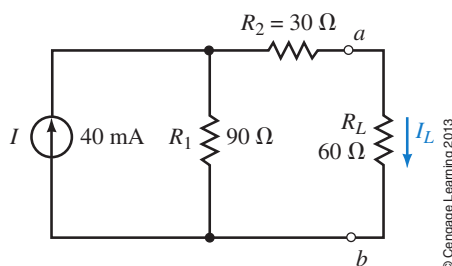


FIGURE 9-82

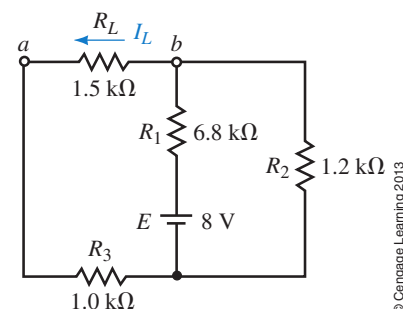


FIGURE 9-83

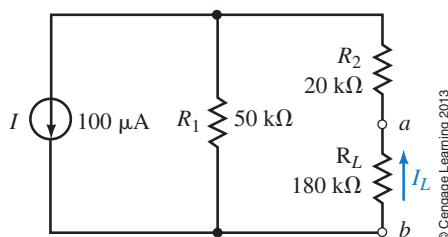


FIGURE 9-84

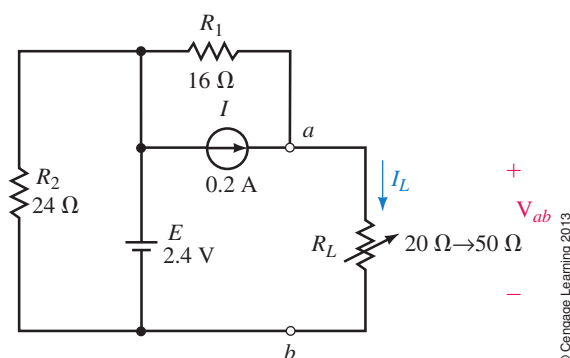


FIGURE 9-85

12. Refer to the circuit of Figure 9-86:

- Find the Thévenin equivalent circuit external to  $R_L$ .
- Use the equivalent circuit to determine  $V_{ab}$  when  $R_L = 10 \text{ k}\Omega$  and when  $R_L = 20 \text{ k}\Omega$ .

13. Refer to the circuit of Figure 9-87:

- Find the Thévenin equivalent circuit external to the indicated terminals.
- Use the Thévenin equivalent circuit to determine the current through the indicated branch.

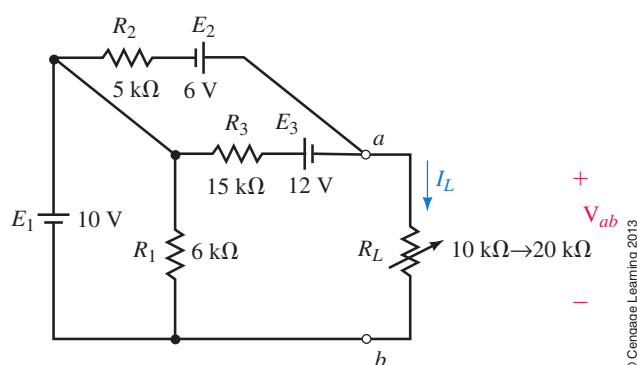


FIGURE 9-86

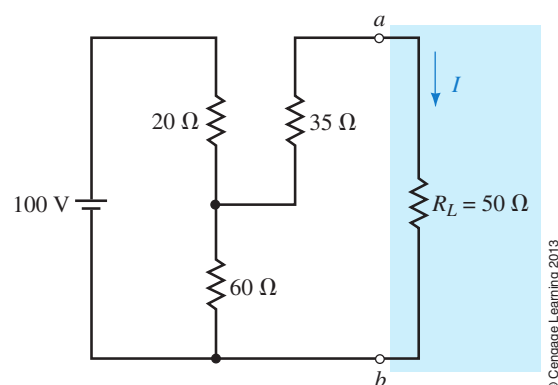


FIGURE 9-87

14. Refer to the circuit of Figure 9-88:

- Find the Thévenin equivalent circuit external to  $R_L$ .
- Use the Thévenin equivalent circuit to find  $V_L$ .

15. Refer to the circuit of Figure 9-89:

- Find the Thévenin equivalent circuit external to the indicated terminals.
- Use the Thévenin equivalent circuit to determine the current through the indicated branch.

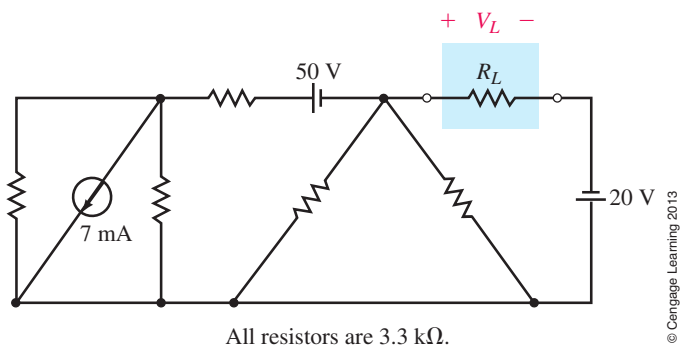


FIGURE 9-88

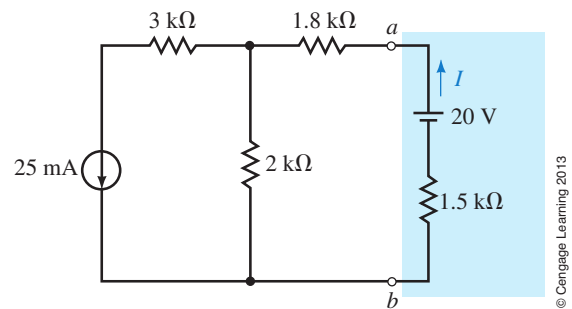


FIGURE 9-89

16. Refer to the circuit of Figure 9-90:
- Find the Thévenin equivalent circuit external to the indicated terminals.
  - If  $R_5 = 1 \text{ k}\Omega$ , use the Thévenin equivalent circuit to determine the voltage  $V_{ab}$  and the current through this resistor.

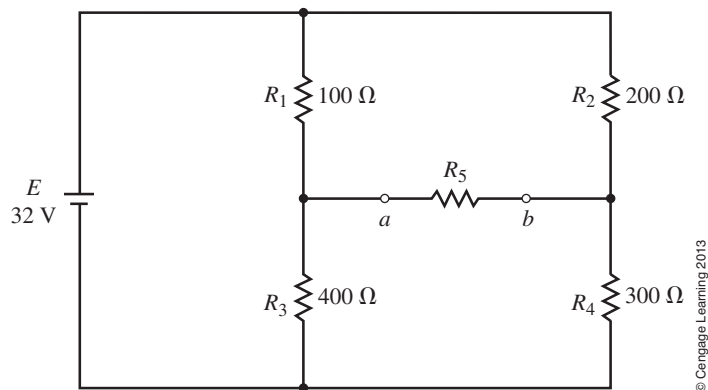


FIGURE 9-90

17. Refer to the circuit of Figure 9-91:
- Find the Thévenin equivalent circuit external to  $R_L$ .
  - Use the Thévenin equivalent circuit to find the current  $I$  when  $R_L = 0$ ,  $10 \text{ k}\Omega$ , and  $50 \text{ k}\Omega$ .
18. Refer to the circuit of Figure 9-92:
- Find the Thévenin equivalent circuit external to  $R_L$ .
  - Use the Thévenin equivalent circuit to find the power dissipated by  $R_L$ .

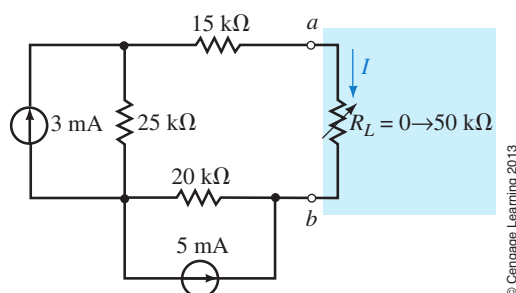


FIGURE 9-91

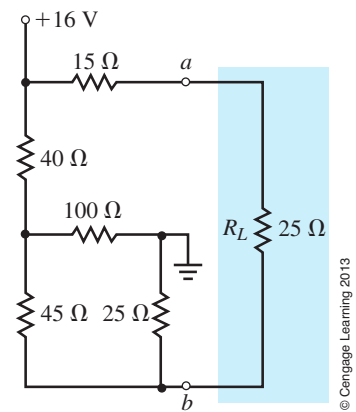


FIGURE 9-92

19. Repeat Problem 17 for the circuit of Figure 9–93.  
 20. Repeat Problem 17 for the circuit of Figure 9–94.

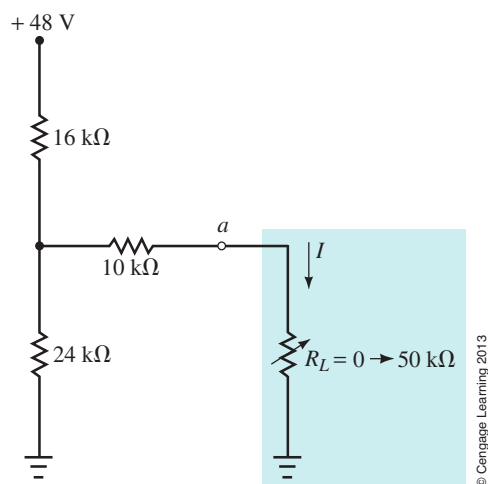


FIGURE 9–93

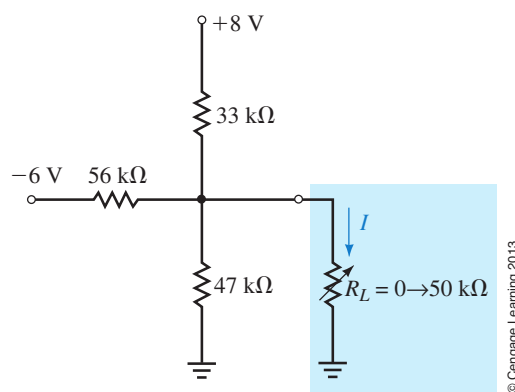


FIGURE 9–94

21. Find the Thévenin equivalent circuit of the network external to the indicated branch as shown in Figure 9–95.  
 22. Refer to the circuit of Figure 9–96.  
 a. Find the Thévenin equivalent circuit external to the indicated terminals.  
 b. Use the Thévenin equivalent circuit to determine the current through the indicated branch.  
 23. Repeat Problem 22 for the circuit of Figure 9–97.

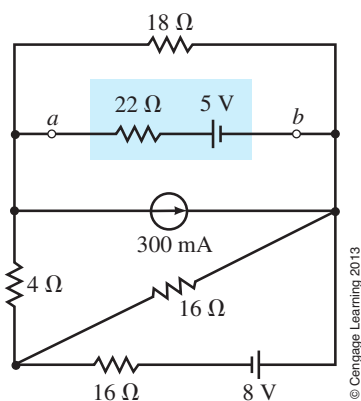


FIGURE 9–95

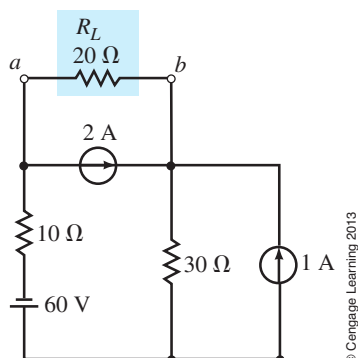


FIGURE 9–96

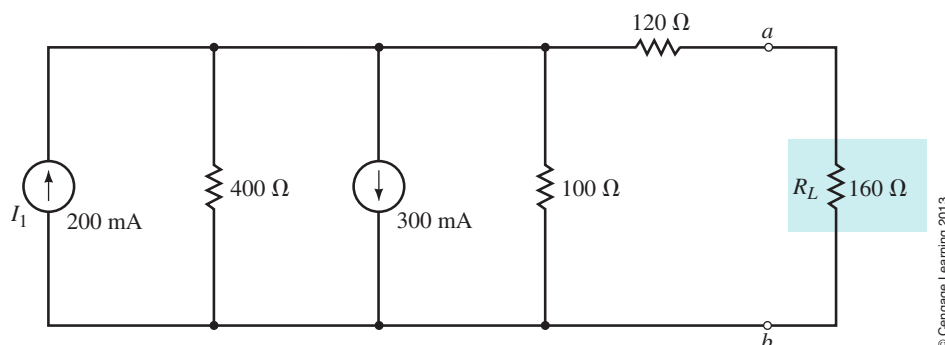


FIGURE 9–97

24. Repeat Problem 22 for the circuit of Figure 9–98.

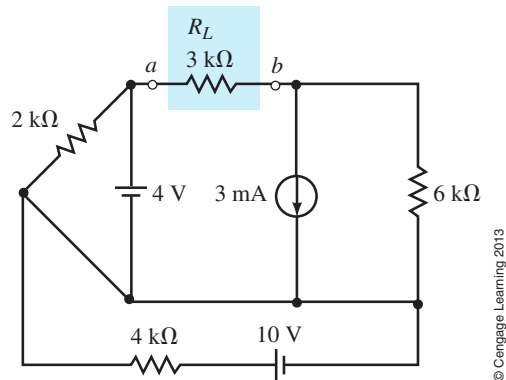


FIGURE 9–98


### 9.3 Norton's Theorem

25. Find the Norton equivalent circuit external to  $R_L$  in the circuit of Figure 9–81. Use the equivalent circuit to find  $I_L$  for the circuit.
26. Repeat Problem 25 for the circuit of Figure 9–82.
27. Repeat Problem 25 for the circuit of Figure 9–83.
28. Repeat Problem 25 for the circuit of Figure 9–84.
29. Refer to the circuit of Figure 9–85:
  - a. Find the Norton equivalent circuit external to  $R_L$ .
  - b. Use the equivalent circuit to determine  $I_L$  when  $R_L = 20\ \Omega$  and when  $R_L = 50\ \Omega$ .
30. Refer to the circuit of Figure 9–86:
  - a. Find the Norton equivalent circuit external to  $R_L$ .
  - b. Use the equivalent circuit to determine  $I_L$  when  $R_L = 10\ \text{k}\Omega$  and when  $R_L = 20\ \text{k}\Omega$ .
31. a. Find the Norton equivalent circuit external to the indicated terminals of Figure 9–87.
  - b. Convert the Thévenin equivalent circuit of Problem 13 to its Norton equivalent.
32. a. Find the Norton equivalent circuit external to  $R_L$  in the circuit of Figure 9–88.
  - b. Convert the Thévenin equivalent circuit of Problem 14 to its Norton equivalent.
33. Repeat Problem 31 for the circuit of Figure 9–91.
34. Repeat Problem 31 for the circuit of Figure 9–92.
35. Repeat Problem 31 for the circuit of Figure 9–95.
36. Repeat Problem 31 for the circuit of Figure 9–96.

### 9.4 Maximum Power Transfer Theorem


37. a. For the circuit of Figure 9–91, determine the value of  $R_L$  so that maximum power is delivered to the load.
  - b. Calculate the value of the maximum power which can be delivered to the load.
  - c. Sketch the curve of power versus resistance as  $R_L$  is adjusted from  $0\ \Omega$  to  $50\ \text{k}\Omega$  in increments of  $5\ \text{k}\Omega$ .

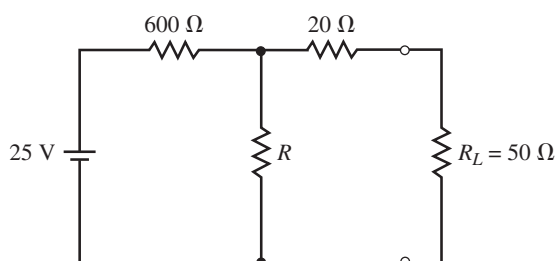38. Repeat Problem 37 for the circuit of Figure 9–94.
39. a. For the circuit of Figure 9–99, find the value of  $R$  so that  $R_L = R_{Th}$ .  
 b. Calculate the maximum power dissipated by  $R_L$ .
40. Repeat Problem 39 for the circuit of Figure 9–100.



© Cengage Learning 2013


FIGURE 9–99

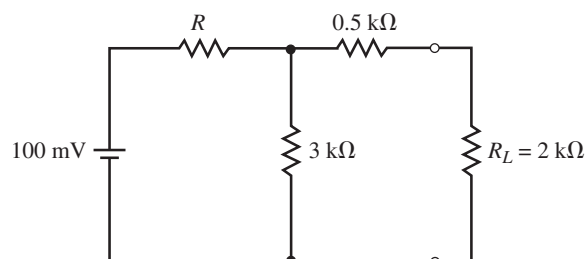

© Cengage Learning 2013

FIGURE 9–100

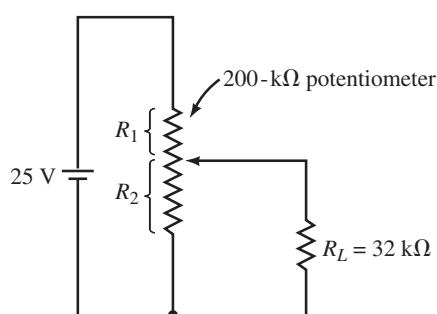41. a. For the circuit of Figure 9–101, determine the values of  $R_1$  and  $R_2$  so that the 32-kΩ load receives maximum power.  
 b. Calculate the maximum power delivered to  $R_L$ .




© Cengage Learning 2013

FIGURE 9–101

42. Repeat Problem 41 if the load resistor has a value of  $R_L = 25 \text{ k}\Omega$ .

## 9.5 Substitution Theorem

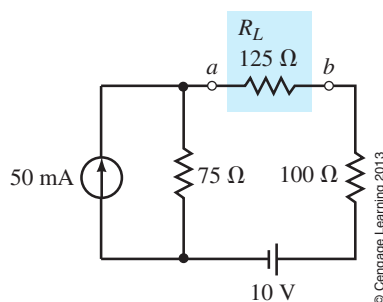43. If the indicated portion of the circuit in Figure 9–102 is to be replaced with a voltage source and a 50-Ω series resistor, determine the magnitude and polarity of the resulting voltage source.
44. If the indicated portion of the circuit in Figure 9–102 is to be replaced with a current source and a 200-Ω shunt resistor, determine the magnitude and direction of the resulting current source.



© Cengage Learning 2013

FIGURE 9–102



## 9.6 Millman's Theorem

45. Use Millman's theorem to find the current through and the power dissipated by  $R_L$  in the circuit of Figure 9–103.
46. Repeat Problem 45 for the circuit of Figure 9–104.
47. Repeat Problem 45 for the circuit of Figure 9–105.
48. Repeat Problem 45 for the circuit of Figure 9–106.

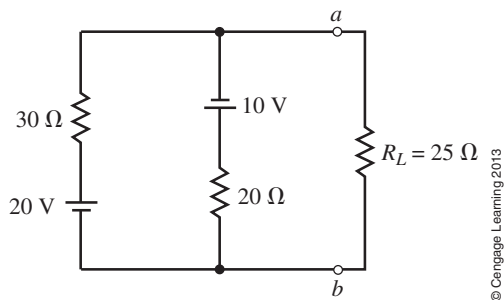


FIGURE 9–103

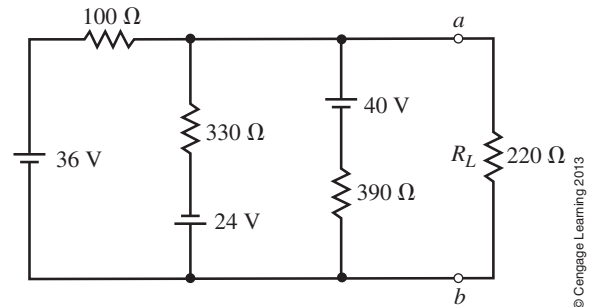


FIGURE 9–104

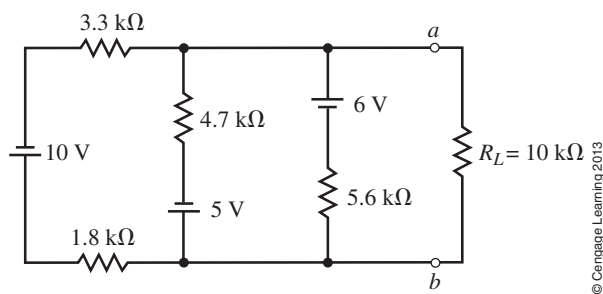


FIGURE 9–105

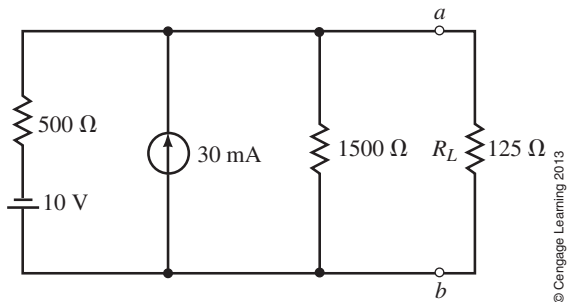


FIGURE 9–106

## 9.7 Reciprocity Theorem

49. a. Determine the current  $I$  in the circuit of Figure 9–107.  
b. Show that reciprocity applies for the given circuit.
50. Repeat Problem 49 for the circuit of Figure 9–108.

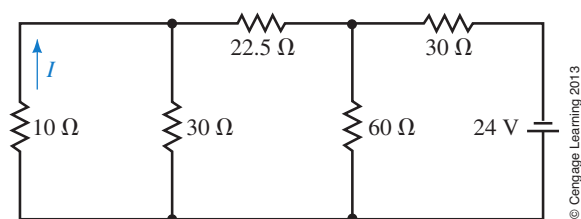


FIGURE 9–107

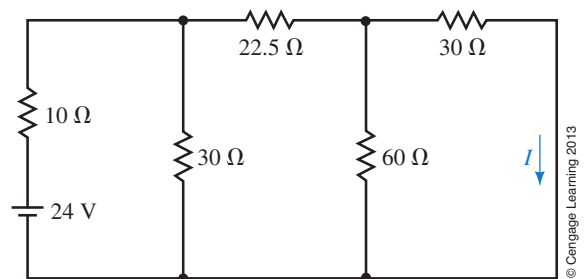


FIGURE 9–108