

1) A)

a	b	c	A
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth Table


$$A = \bar{a}bc + abc + ab\bar{c} + abc$$

Adding abc will not change result.

$$A = \bar{a}bc + \bar{a}bc + ab\bar{c} + abc + abc + abc$$

$$A = ac(\bar{b} + b) + ab(\bar{c} + c) + bc(\bar{a} + a)$$


$$A = ac + ab + bc$$

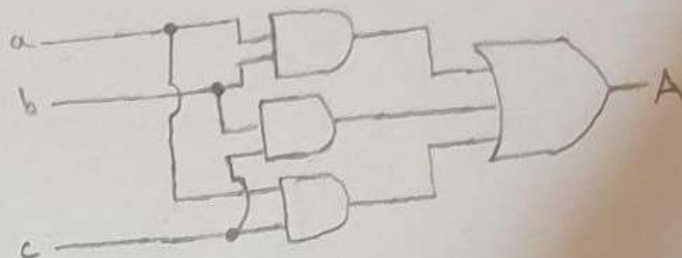

1) B)


$$A = ac + ab + bc$$

A \ BC	00	01	11	10
0	0	0	1	0
1	0	1	1	1

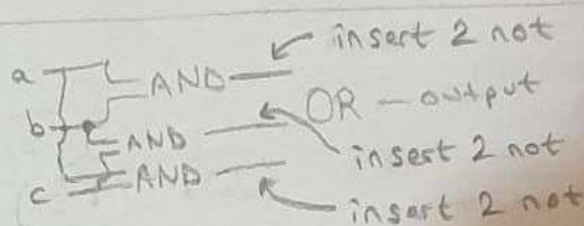

If we insert those NOTs, AND gates have become NAND gates. We have 3 NOT and 1 OR left. $A + B = (A'B')$ using de Morgan's law.

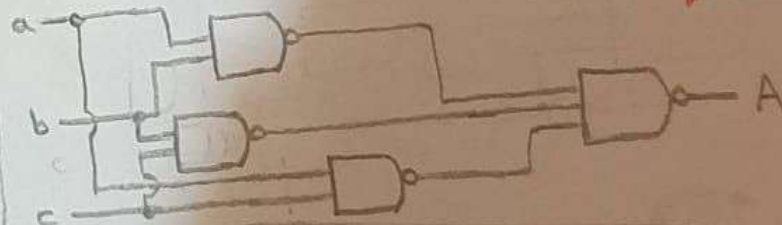The relation between OR gate and NAND gate has been shown.



Truth table of G

a	b	c	d	G
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Truth table of F

a	b	c	d	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

As seen, G and F are output columns and are not equal to each other.

Therefore, the two circuits are not equivalent circuits.

2) A)

cd \ ab	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	0	0	0	0
10	1	1	0	1

Karnaugh map belongs to the circuit whose output is G.

There are four 1s groups.

$$G = \bar{a}\bar{c} + \bar{a}\bar{d} + \bar{b}\bar{c} + \bar{b}\bar{d}$$

$$G = \bar{a}(\bar{c} + \bar{d}) + \bar{b}(\bar{c} + \bar{d})$$

$$G = (\bar{c} + \bar{d})(\bar{a} + \bar{b})$$

cd \ ab	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	1	1	1	1
10	0	0	1	0

Karnaugh map belongs to the circuit whose output is F.

There are two 1s groups.

$$F = cd + ab$$

$$G \neq F$$

They are opposite of each other. They are not equivalent circuits.

3)

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Truth Table of circuit

$$(c \oplus d)(\bar{a}\bar{b} + \bar{a}b) + (\bar{c} \oplus \bar{d})(\bar{a}b + ab)$$

$$(c \oplus d)(\bar{a} \oplus b) + (\bar{c} \oplus \bar{d})(\bar{a} \oplus b)$$

$$XY + X'Y' = (X \oplus Y) \oplus 1 = X \oplus Y'$$

$$F = (a \oplus b) \oplus (c \oplus d)$$

cd \ ab	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1

Karnaugh map belongs to the circuit.

XOR boolean expression $\bar{a}b + \bar{b}a$

XNOR boolean expression $\bar{a}\bar{b} + ab$

$$F = \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d$$

$$F = \bar{a}\bar{b}(\bar{c}\bar{d} + cd) + \bar{a}b(\bar{c}d + c\bar{d}) + \bar{a}b(\bar{c}d + c\bar{d}) + ab(\bar{c}\bar{d} + cd)$$

$$F = \bar{a}\bar{b}(\bar{c} \oplus d) + \bar{a}b(c \oplus d) + \bar{a}b(c \oplus d) + ab(\bar{c} \oplus d)$$

$$F = ((a \oplus b) \oplus (c \oplus d)) \oplus 1$$

