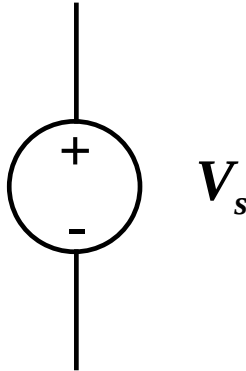


Basic Circuit Elements

“Developing models, which provide an understanding that is imperfect, but adequate, for solving practical problems lies at the heart of engineering.”


Sources: 'Ideal Sources'

Ideal Voltage Source



Maintains **constant** V across terminals regardless of current


Ideal Current Source

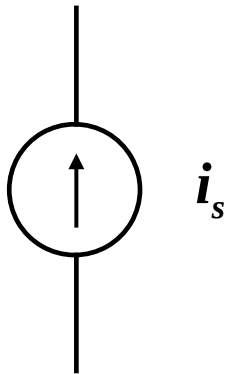

Maintains **constant** I through terminals regardless of voltage across them

- These are **Independent** sources! Their value does not depend on anything.
- Specifications: **Value** and **Polarity**

Sources: Dependent Sources

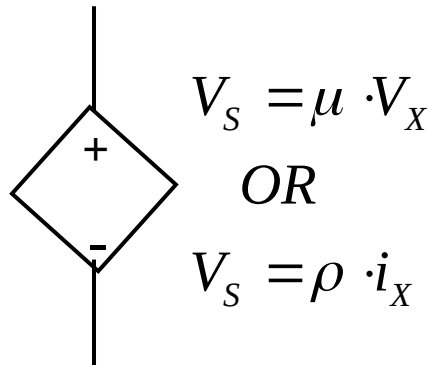


Four variations:

μ and β are dimensionless

ρ is in (V/A)


α is in (A/V)

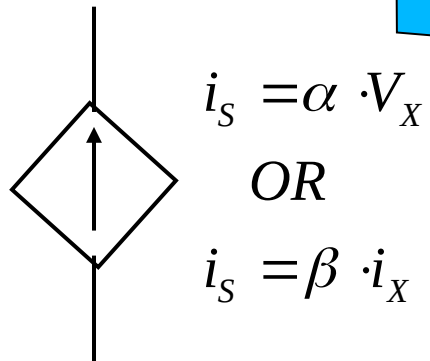


Value depends
on **V** or **i**
elsewhere in
the circuit

Transistors and operational
amplifiers (op amps) are
modeled with this

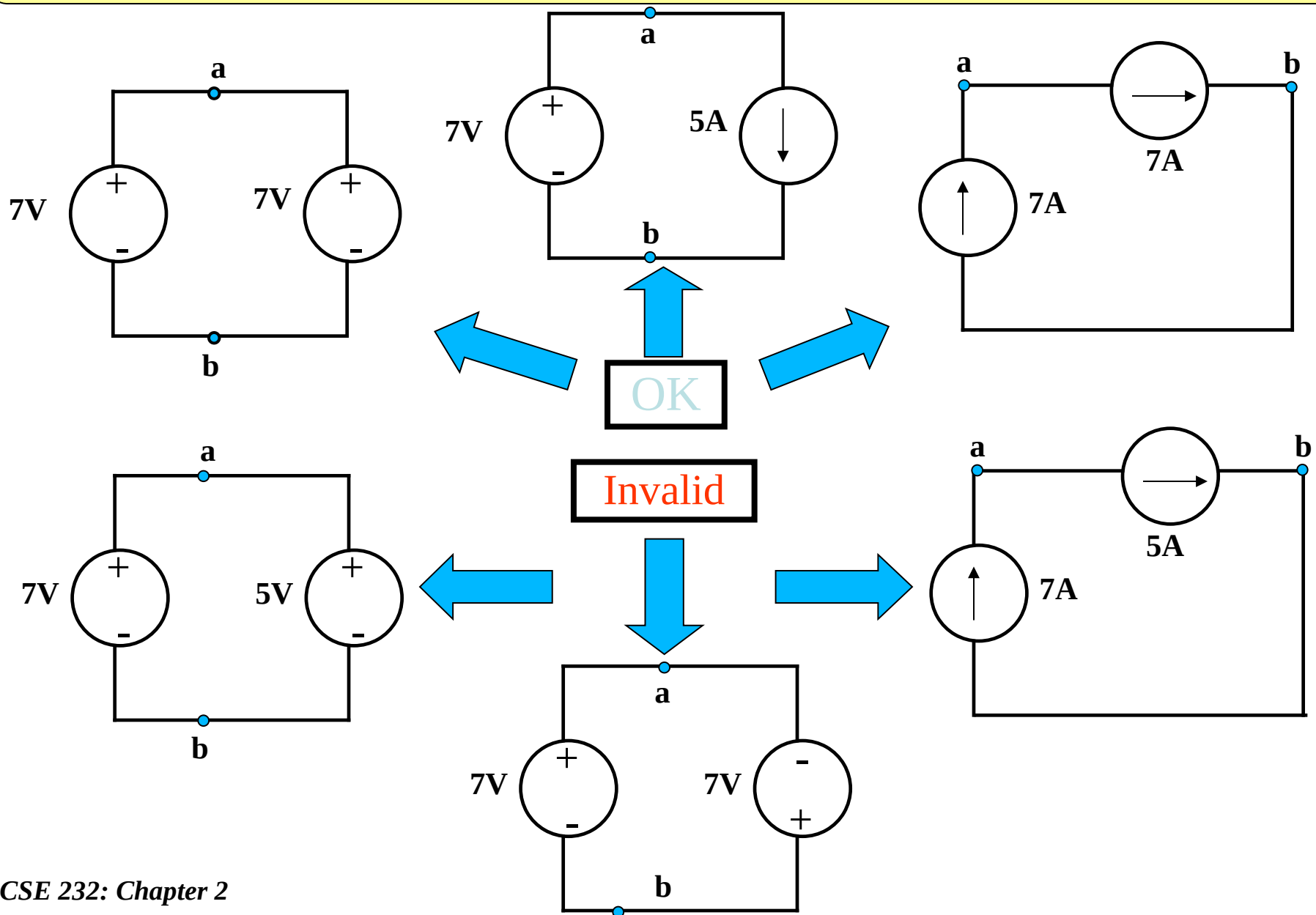
Limited Interconnections – Independent Sources



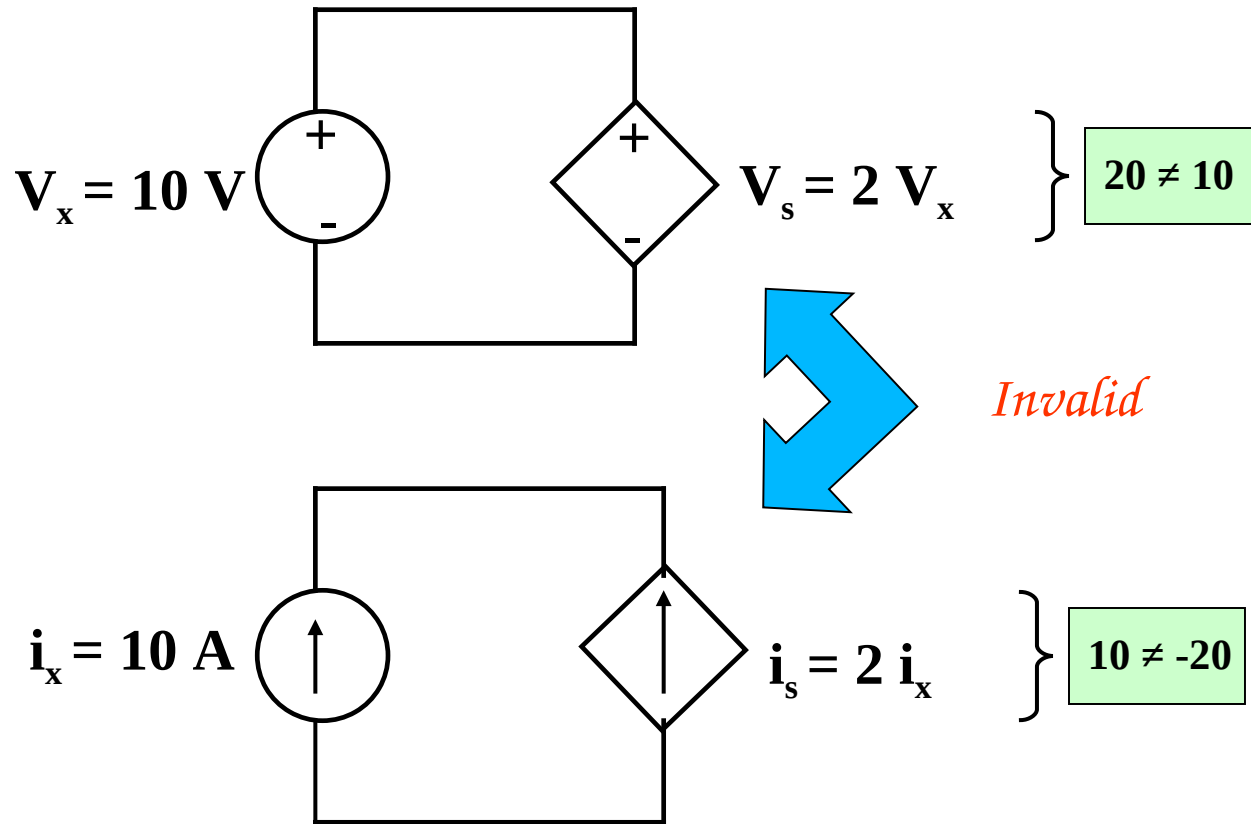
Limited Interconnections – Dependent Sources




Which are valid connections?

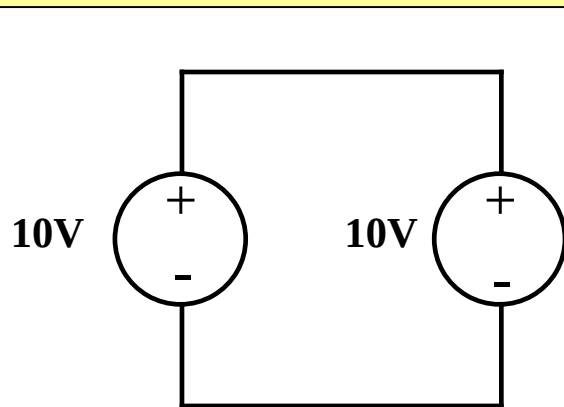


(a)

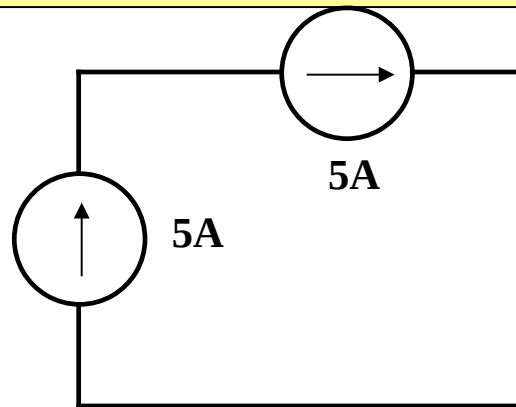


(b)

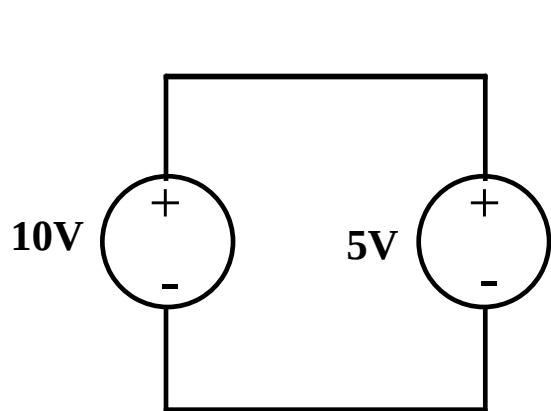

(c)

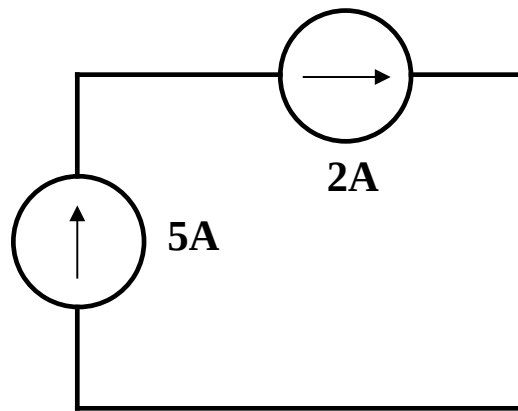


(d)

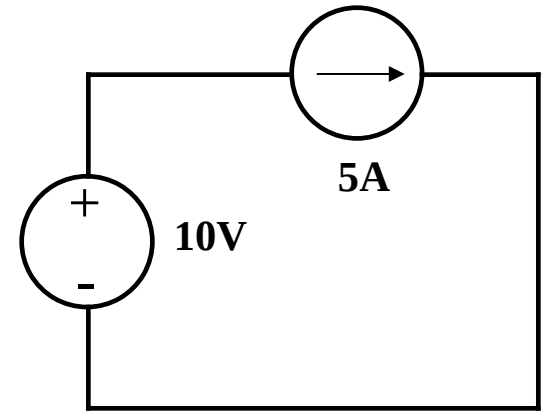



(e)


Which are valid connections?

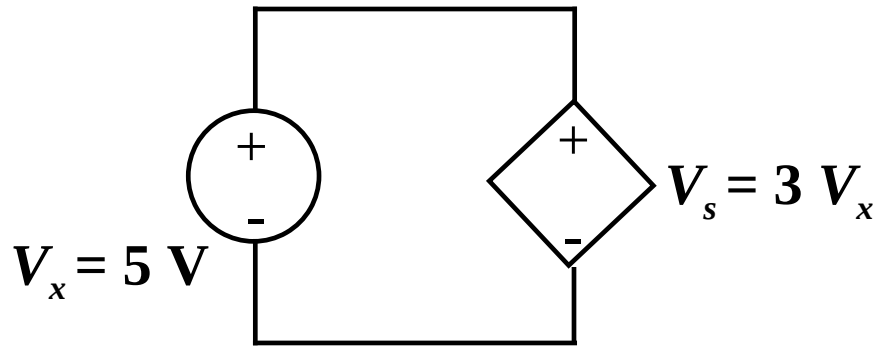

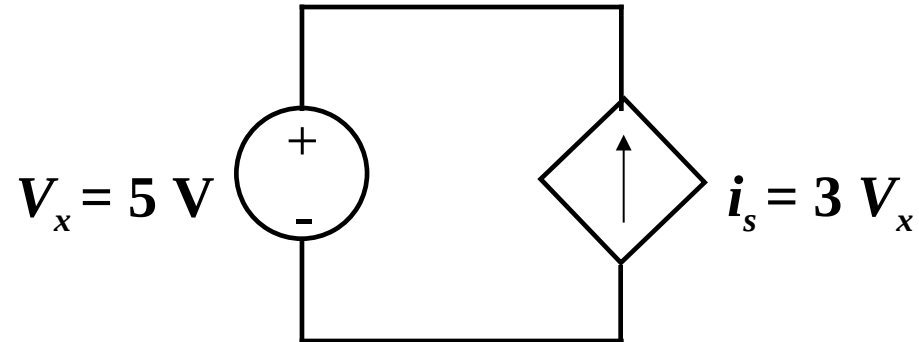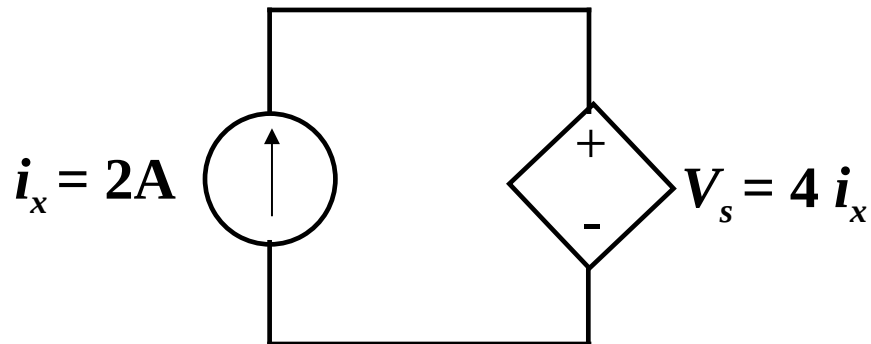
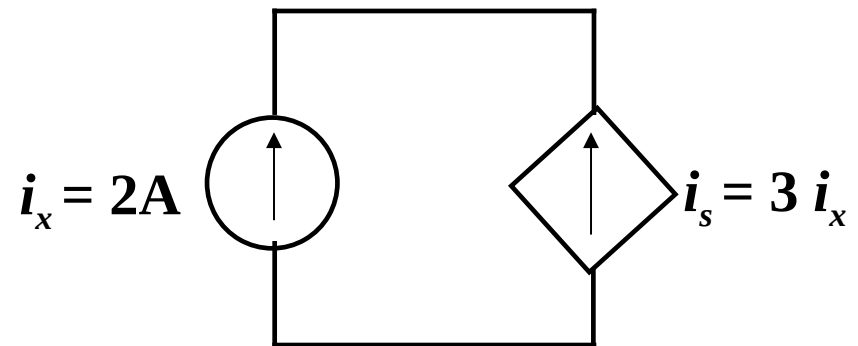
(a) **X**



(b) 




(c) 




(d) **X**

Ohm's Law

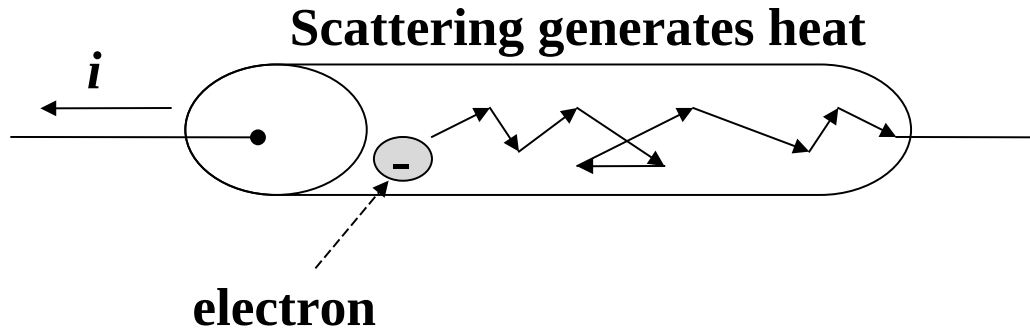


Resistance

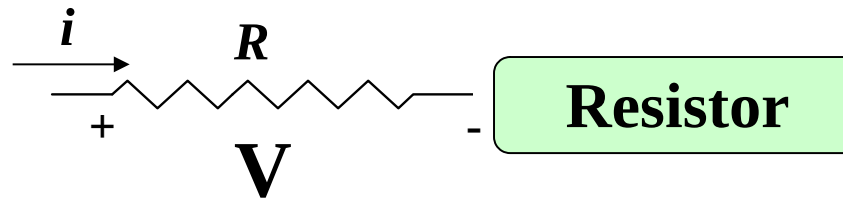Capacity of a material
to impede flow of
current



Resistor

i - v characteristic of Resistor

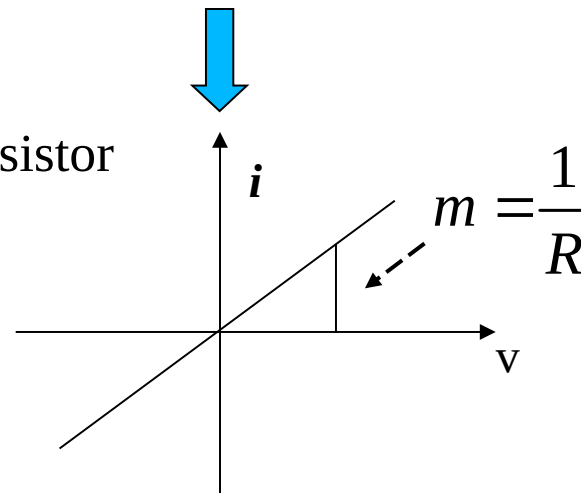


Ohm's Law

$$i = \left(\frac{1}{R} \right) \cdot V$$

V in Volts (V)
 i in Amps (A)
 R in Ohms (Ω)

$$V = i \cdot R$$

Resistance and Conductance

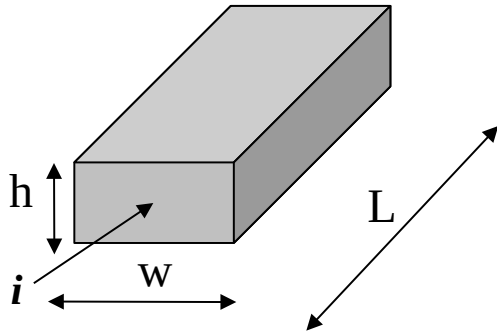

Ideal R is **constant**

R can vary with time (t) and temperature (T)

Not in this class

$$R = \rho \cdot \frac{L}{A}$$

ρ is Resistivity ($\Omega \cdot \text{cm}$)

Conductance


Unit: Siemens (S) or mhos (\mathfrak{U})

If $R = 10\Omega$ then $G = 0.1 \mathfrak{U}$

$$G = \frac{1}{R}$$

Power at Terminals of Resistor

Passive sign convention

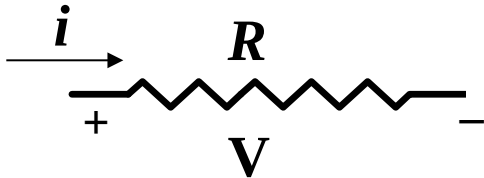


Ohm's Law

$$V = i R$$

$$p = V i$$

$$p = (iR) i$$

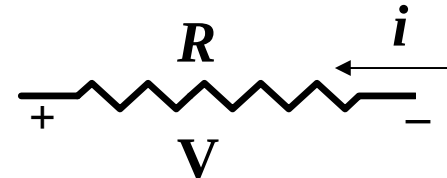

Ohm's Law

$$V = -i R$$

$$p = -V i$$

$$p = -(-iR) i$$

Find Power

In either case,

$$p = i^2 R = i^2 / G$$

Side Note

$$p = V i$$

$$p = V (V/R)$$

$$p = V^2/R = V^2 G$$


Always positive

R always **absorbs** power

Therefore, it is **passive**.


Side Note

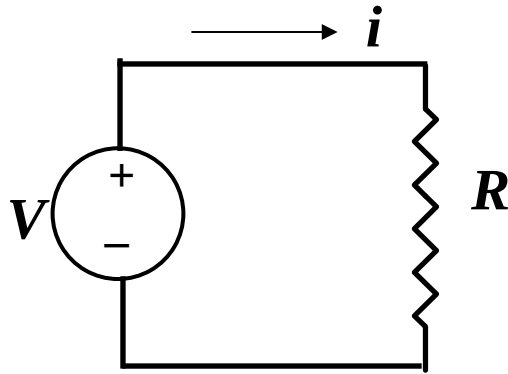Example: Find Power absorbed by the resistor



$$V = 100 \text{ (V)} \quad \longrightarrow \quad i = V / R = 100 / 10 = 10 \text{ (A)}$$
$$R = 10(\Omega)$$
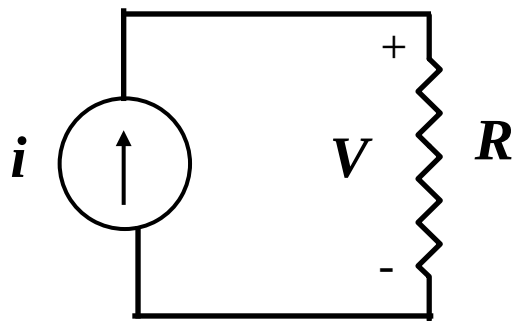
$$p = V i = i^2 R = V^2 / R$$
$$= (100)(10) = 10^2(10) = 100^2/10$$
$$= \mathbf{1000 \text{ (W)}}$$
$$= \mathbf{1 \text{ (kW)}}$$



$$i = 5 \text{ (A)} \quad \longrightarrow \quad V = i R = 5 (10) = 50 \text{ (V)}$$
$$R = 10(\Omega)$$

$$p = V i = i^2 R = V^2 / R$$
$$= (50)(5) = 5^2(10) = 50^2/10 = \mathbf{250 \text{ (W)}}$$

Models for Actual Circuit Components


- **Battery:** Voltage Source
- **Lamp:** Resistor
- **Wire:** Resistor or Ignore
- **Conducting Path:** Resistor or Ignore
- **Not Necessarily a Unique Answer**

Kirchhoff's Laws

Gustav Robert Kirchhoff

Published in 1845 as a student

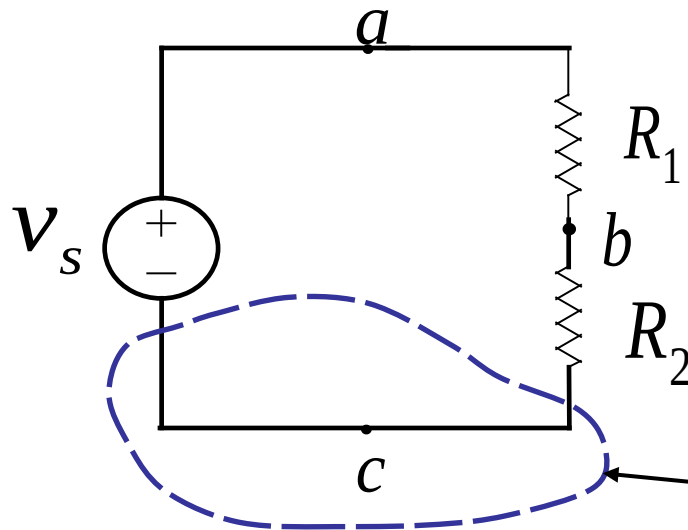Node: Point where 2 or more circuit elements meet




Nodes are a, b, and c

whole section of wire is a node !

Kirchhoff's Current Law: (KCL)

“Algebraic” Relationship is Important

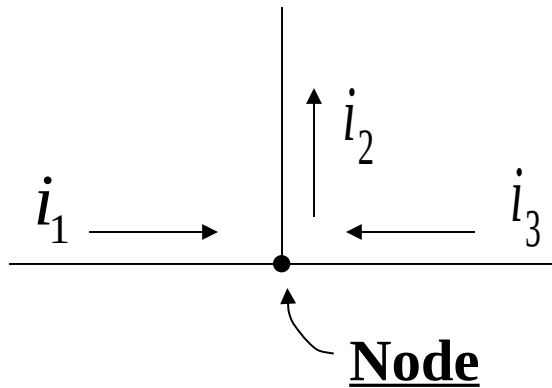

i_1 and i_3 are “entering” the node.

i_2 is “leaving” the node.

Currents leaving a node are “Algebraically” opposite in “sign” to currents entering a node.

i Conventions *i*

(a) $i_2 - i_1 - i_3 = 0$ } i leaving considered positive


(b) $i_1 + i_3 - i_2 = 0$ } i entering considered positive

(c) $i_2 = i_1 + i_3$ } (c) is equivalent to (a) and (b)

Note a “considered” positive current could be negative

Kirchhoff's Voltage Law: (KVL)

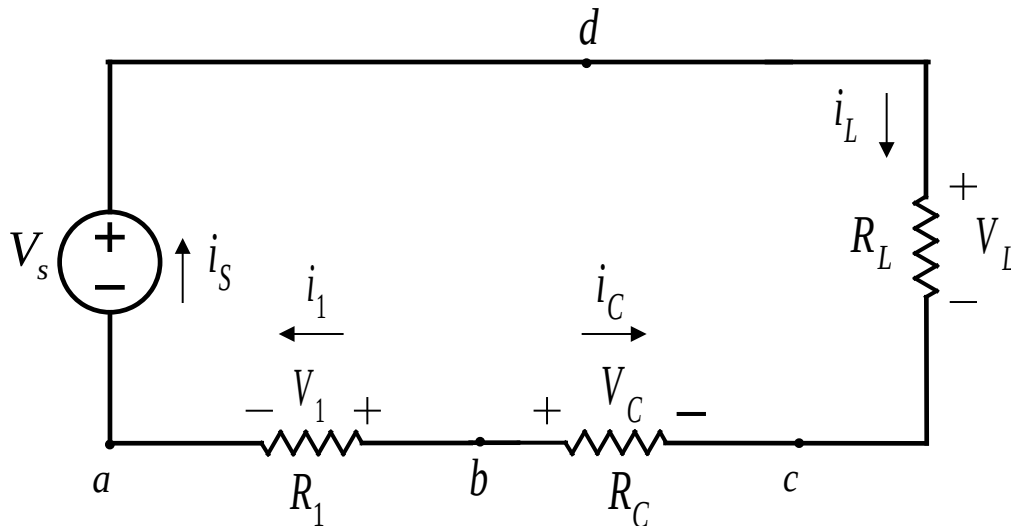
The algebraic sum of all the voltages around any closed path in a circuit equals zero.



$$\underbrace{-V_S + V_L - V_C + V_1 = 0}_{\text{KVL}}$$

Voltages and Currents have been defined in the circuit

Sign Convention

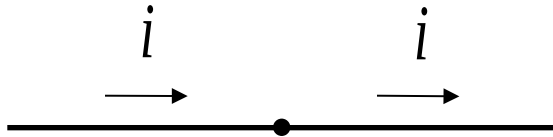

Is i entering or leaving the node ?


$$i - i = 0$$

$$\Rightarrow i = i$$

KCL Stated Another Way

$$\sum i'_s \text{ entering node} = \sum i'_s \text{ leaving node}$$

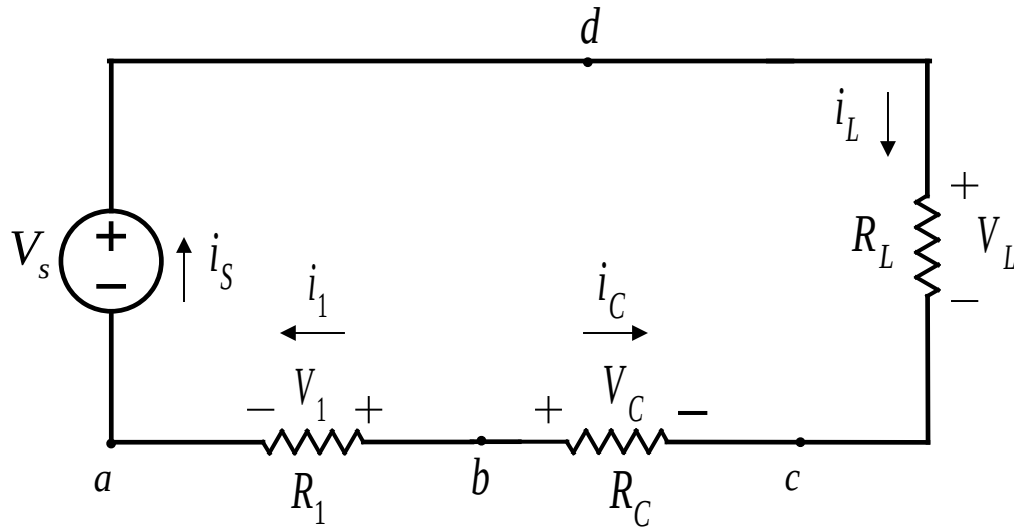Flashlight Circuit: Find the currents in the circuit



Voltages and Currents have been defined in the circuit


Ohm's Law

$$V_1 = i_1 R_1 \quad (1)$$

$$V_C = i_C R_C \quad (2)$$


$$V_L = i_L R_L \quad (3)$$

(contd.)

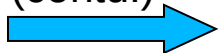

Flashlight Circuit (Contd.)

Circuit can be redrawn as:

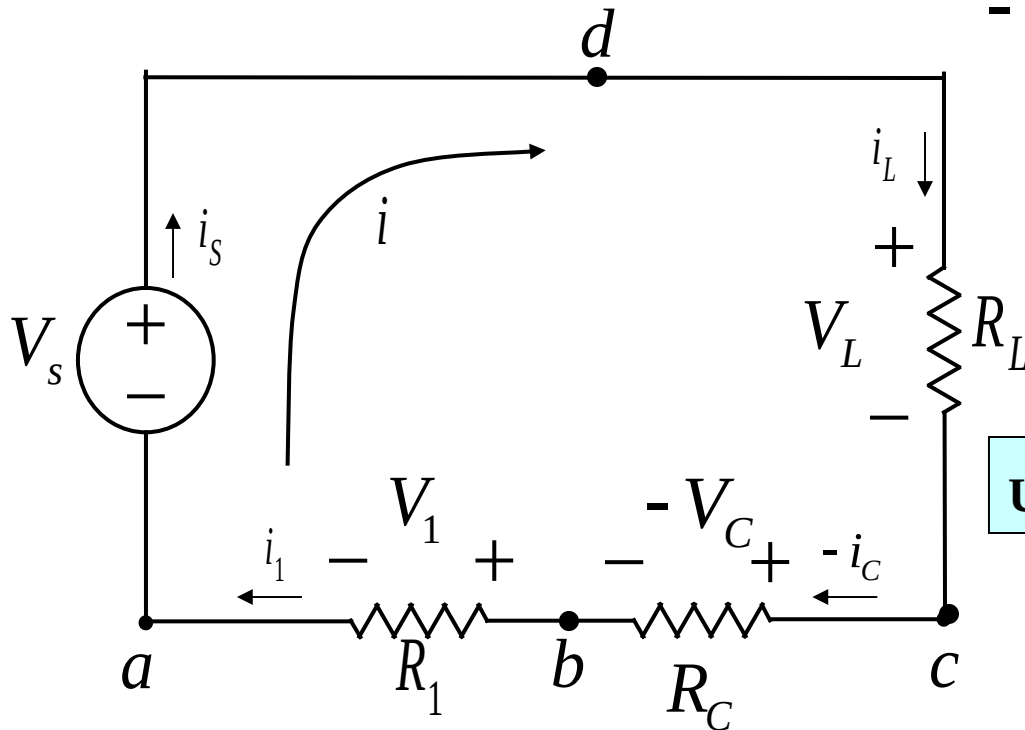

Start from node @

$$-V_S + V_L - V_C + V_1 = 0 \quad \text{KVL}$$

$$\textcircled{1} \quad V_S = V_L + V_1 - V_C$$

Currents are all the same; so define:

$$\textcircled{2} \quad i \equiv i_S = i_1 = i_L = -i_C$$

Using Ohm's Law and $\textcircled{2}$, $\textcircled{1}$ becomes

$$V_S = iR_L + \overbrace{iR_C}^{-V_C} + iR_1$$

$$\textcircled{3} \quad V_S = i(R_L + R_C + R_1) \quad \text{After Simplifying}$$

(Contd.)
➡

Flashlight Circuit (Contd.)


$$i = \frac{V_s}{R_L + R_C + R_1} \quad \left. \vphantom{\frac{V_s}{R_L + R_C + R_1}} \right\} \text{Solve } \textcircled{3} \text{ for } i$$

Using Ohm's Law and calculated i , we obtain V_1 , V_C , and V_L

$$V_1 = iR_1 \quad - \quad V_C = iR_C \quad V_L = iR_L$$

$$i = i_s = i_1 = i_L = -i_C$$

Example: Find Current in the Circuit

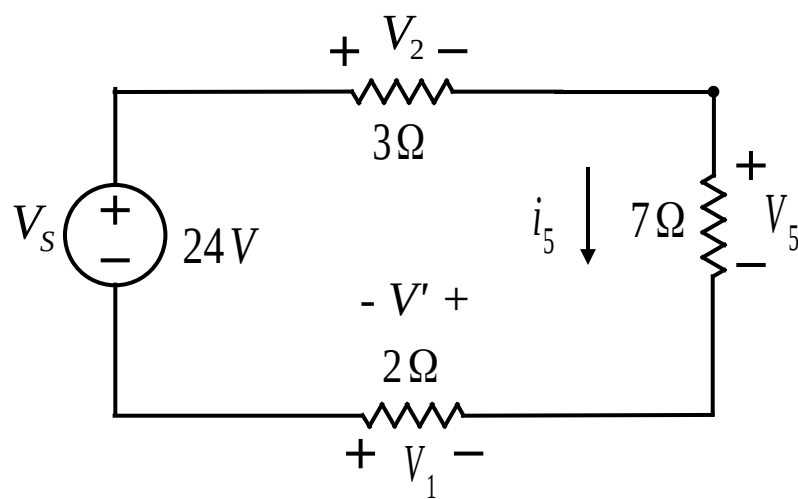

V_1 , V_2 , V_5 , and i_5
have been defined in the
circuit

a) Find i_5 (current is the same in all elements.)

$$\begin{aligned}
 \text{KVL} \left\{ \begin{aligned} V_S &= V_2 + V_5 + V' \\ V_S &= 3i_5 + 7i_5 + 2i_5 \\ V_S &= i_5(3 + 7 + 2) = 12i_5 \end{aligned} \right. \left\{ \begin{aligned} V_1 &= -V' \\ V_2 &= 3i_5, V_S = 7i_5, V' = 2i_5 \end{aligned} \right. \left\{ \begin{aligned} \text{forget "V}_1\text{" for now} \\ \text{Simplify} \\ i_5 &= \frac{24}{12} = 2 \text{ (A)} \end{aligned} \right. \left\{ \begin{aligned} \text{Solve for } i_5 \end{aligned} \right.
 \end{aligned}$$


Example: Find Voltages and Power of the Supply (Contd.)

b) $V_1 = -2i_5 = -2(2)$

$$V_1 = -4(V)$$

c) $V_2 = 3i_5 = 3(2)$

$$V_2 = 6(V)$$

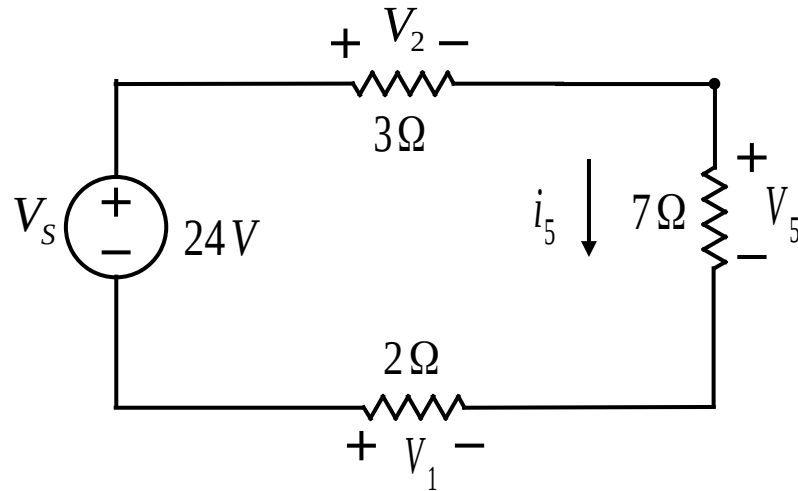

d) $V_5 = 7i_5 = 7(2)$

$$V_5 = 14(V)$$


Note: $V_s = V_2 + V_5 - V_1$
 $= 6 + 14 - (-4) = 24(V)$

Sign
Convention

e) $p_{24V} = -V_s i_5 = -24(2) = -48(W)$

Thus power is extracted from the supply

Example: Find Current i

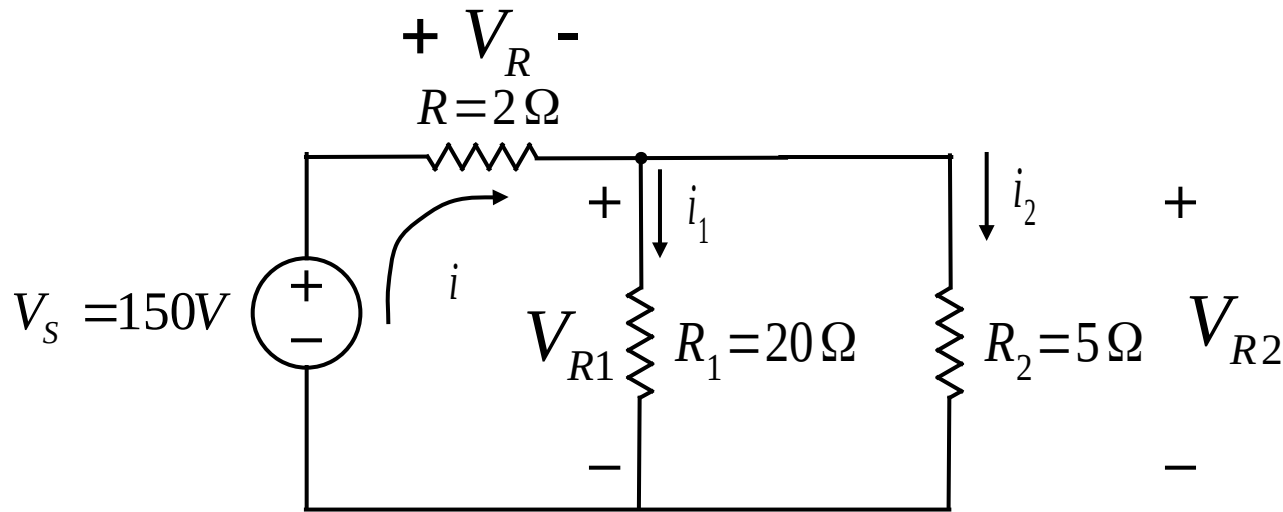

$$\textcircled{1} \quad V_S = Ri + R_1 i_1 \quad \left. \vphantom{V_S = Ri + R_1 i_1} \right\} \text{KVL and Ohm's Law}$$

$$\textcircled{2} \quad R_1 i_1 = R_2 i_2 \quad \left. \vphantom{R_1 i_1 = R_2 i_2} \right\} \text{KVL and Ohm's Law}$$

$$\textcircled{3} \quad i = i_1 + i_2 \quad \left. \vphantom{i = i_1 + i_2} \right\} \text{KCL}$$

$$\text{Substitute } \textcircled{3} \longrightarrow \textcircled{1} \Rightarrow V_S = R(i_1 + i_2) + R_1 i_1 \quad \textcircled{4}$$

$$V_S = (R + R_1) i_1 + R i_2 \quad \textcircled{4} \left. \vphantom{V_S = (R + R_1) i_1 + R i_2} \right\} \text{Collect terms}$$

Example (Contd.)

Solve (2) for i_2 then substitute into (4)

$$R_1 i_1 = R_2 i_2 \Rightarrow i_2 = \frac{R_1}{R_2} i_1 \quad (2)$$

$$V_s = (R + R_1) i_1 + R \left(\frac{R_1}{R_2} \right) i_1 = (R + R_1 + \frac{R_1}{R_2} \cdot R) i_1 \quad (4)$$

$$i_1 = \frac{V_s}{R + R_1 + \frac{R \cdot R_1}{R_2}} = \frac{150}{2 + 20 + \frac{2 \cdot (20)}{5}} = \frac{150}{22 + 8} = \frac{150}{30} \quad \left. \vphantom{\frac{150}{30}} \right\} \text{Solve (4) for } i_1$$


$$i_1 = 5(A) \quad i_2 = \frac{R_1}{R_2} i_1 = \frac{20}{5} \cdot 5 \quad i_2 = 20(A) \quad \left. \vphantom{\frac{20}{5} \cdot 5} \right\} \text{Use (2) for } i_2$$

$$(3) \longrightarrow i = i_1 + i_2 = 5 + 20 \Rightarrow i = 25(A) \quad \left. \vphantom{i = 25(A)} \right\} \text{Use (3) for } i$$

$$V_{R1} = V_{R2} = i_1 R_1 = i_2 R_2 = 100(V)$$

$$V_R = R \cdot i = 2(25) = 50(V)$$

Example: Find Resistance R

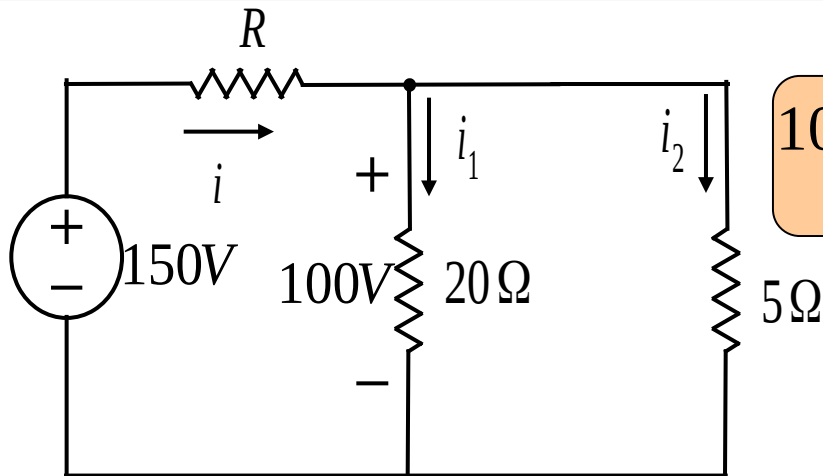

100V dropped across the 20Ω and 5Ω Resistors

Step 1

Ohm's Law

$$i_1 = \frac{100V}{20\Omega} = 5(A)$$
$$i_2 = \frac{100V}{5\Omega} = 20(A)$$

Step 2


KCL $\{ i = i_1 + i_2 = 5(A) + 20(A) = 25(A) \}$

KVL $\{ 150V = iR + 100(V) \}$ Solve for R

$$R = \frac{150(V) - 100(V)}{i} = \frac{50(V)}{25(A)} \Rightarrow R = 2(\Omega)$$

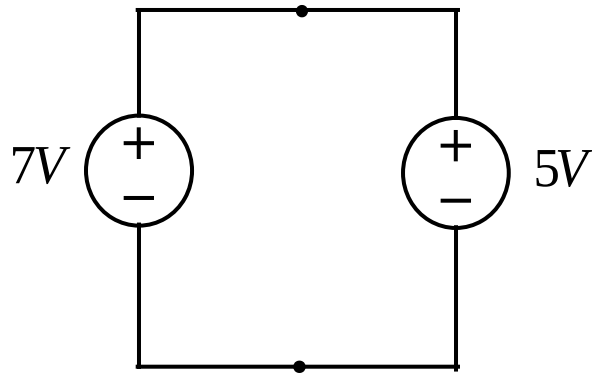
Example: Voltage Source

What would happen experimentally if we hooked two voltage sources in parallel with different voltages?



For ideal sources, this is simply not possible

Model Practical Sources

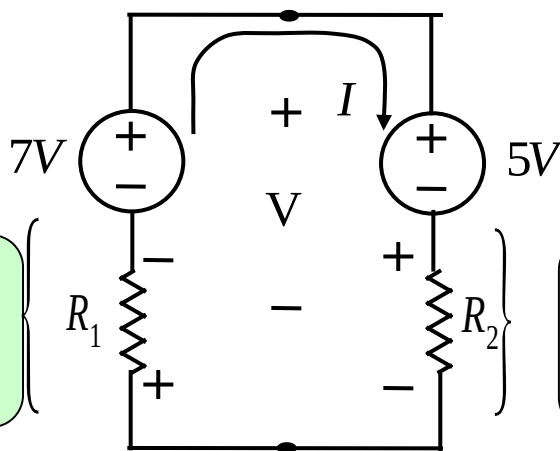

Source Resistance

Source Resistance

$$\text{KVL} \begin{cases} V = 7 - IR_1 = 5 + IR_2 \end{cases} \quad (1)$$

$$\text{Solve for } I \begin{cases} 7 - 5 = IR_1 + IR_2 \\ 2 = I(R_1 + R_2) \end{cases}$$

$$\therefore I = \frac{2}{R_1 + R_2} \quad (2)$$

Example (Contd.)

Substitute


②

into

①

$$\left\{ \begin{array}{l} V = 7 - IR_1 = 7 - \frac{2R_1}{R_1 + R_2} \\ V = 5 + IR_2 = 5 + \frac{2R_2}{R_1 + R_2} \end{array} \right.$$

Voltage is distributed according to KVL

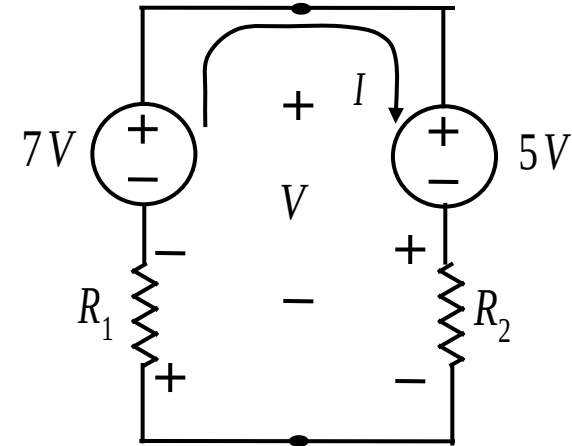

if $R_1 = R_2$

$$I = \frac{2}{2R} = \frac{1}{R}$$

③

Substitute

③


into

①

$$\left\{ \begin{array}{l} V = 7 - \left(\frac{1}{R} \right) R = 6 \\ V = 5 + \left(\frac{1}{R} \right) R = 6 \end{array} \right.$$

$V = 6(V)$
(mid-point)

Redo Example with No Numerical Values

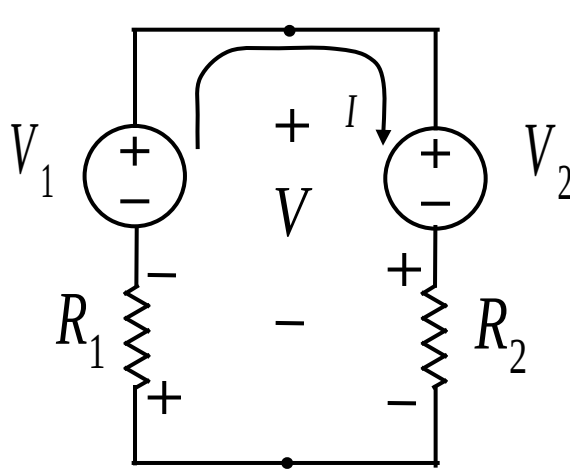

$$V \equiv V_1 - IR_1 = V_2 + IR_2 \quad \left. \vphantom{V \equiv V_1 - IR_1 = V_2 + IR_2} \right\} \text{KVL}$$

$$V_1 - V_2 = I(R_1 + R_2) \quad \left. \vphantom{V_1 - V_2 = I(R_1 + R_2)} \right\} \text{Subtract (2) from (1)}$$

$$I = \frac{V_1 - V_2}{R_1 + R_2} \quad \left. \vphantom{I = \frac{V_1 - V_2}{R_1 + R_2}} \right\} \text{Solve for } I$$

Substitute

(3)

into

(1) and (2)

$$\left\{ \begin{aligned} V &= V_1 - (V_1 - V_2) \frac{R_1}{R_1 + R_2} \\ V &= V_2 + (V_1 - V_2) \frac{R_2}{R_1 + R_2} \end{aligned} \right\}$$


If $R_1 = R_2 = R$

$$V = V_1 - \frac{V_1 - V_2}{2}$$

$$V = V_2 + \frac{V_1 - V_2}{2}$$

Average
of 2
voltage
sources

Example: Circuit with Dependent Sources

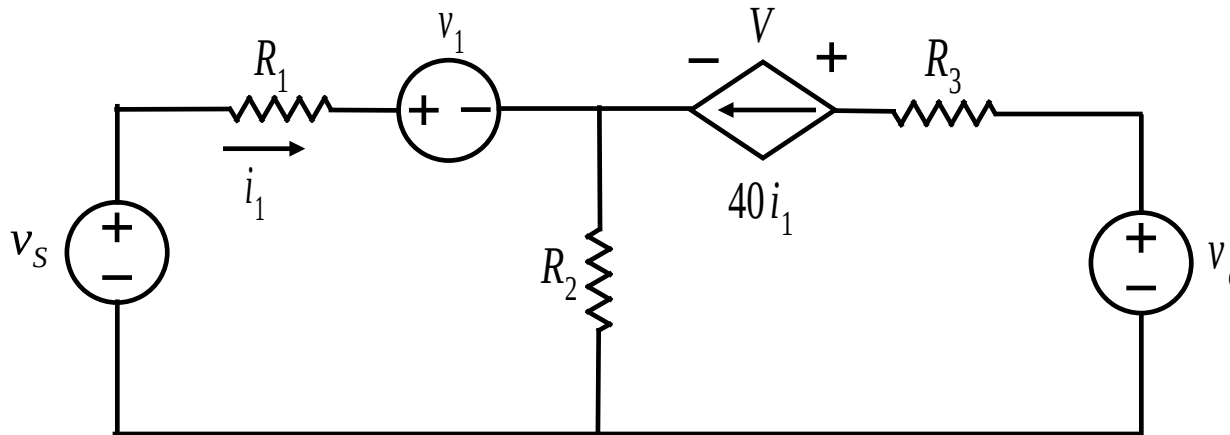


Find i_1 and V

$$\left. \begin{aligned} v_s &= 3(V), \quad v_1 = 0.5(V), \quad v_o = 10(V), \\ R_1 &= 29.5(k\Omega), \quad R_2 = 500(\Omega), \\ R_3 &= 2.4(k\Omega) \end{aligned} \right\}$$

**Given in
the
Problem**

Example: Find i_1 (Contd.)

Two Loops

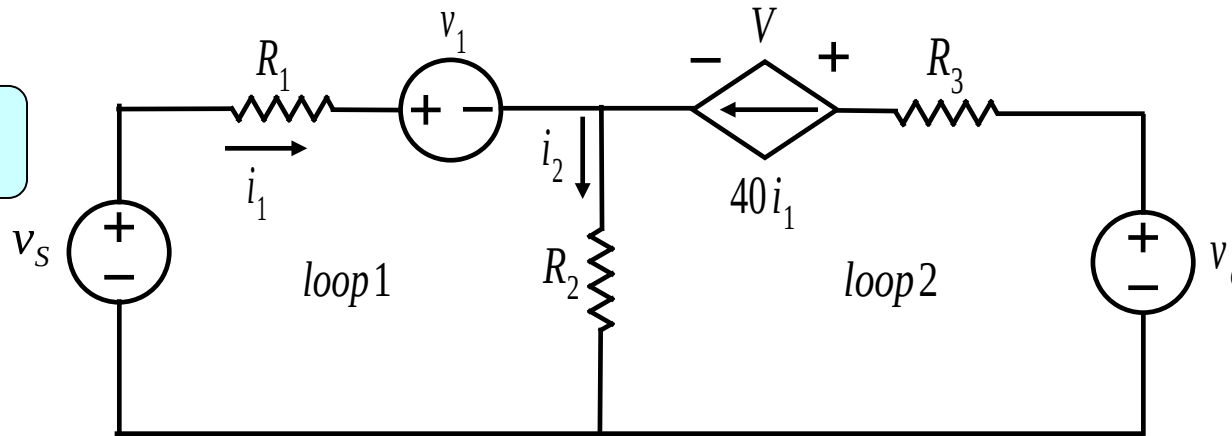

Given

$$v_s = 3(V)$$

$$v_1 = 0.5(V)$$

$$v_o = 10(V)$$

$$R_1 = 29.5(k\Omega)$$

$$R_2 = 500(\Omega)$$

$$R_3 = 2.4(k\Omega)$$

Loop 1

$$v_s = i_1 R_1 + v_1 + i_2 R_2 \quad (1) \quad \left. \begin{array}{l} \text{KVL} \end{array} \right\}$$


$$i_2 = i_1 + 40i_1 = 41i_1 \quad (2) \quad \left. \begin{array}{l} \text{KCL} \end{array} \right\}$$

$$v_s = i_1 (R_1 + 41R_2) + v_1 \quad \left. \begin{array}{l} \text{Substitute (2) into (1)} \end{array} \right\}$$

$$i_1 = \frac{v_s - v_1}{R_1 + 41R_2} = \frac{3 - 0.5}{29.5K + 41(500)} = \frac{2.5}{50K} \quad \left. \begin{array}{l} \text{Solve for } i_1 \end{array} \right\}$$

$$i_1 = 50(\mu A) \quad \text{and} \quad i_2 = 41i_1 = 2.05(mA)$$

Example: Find V (Contd.)

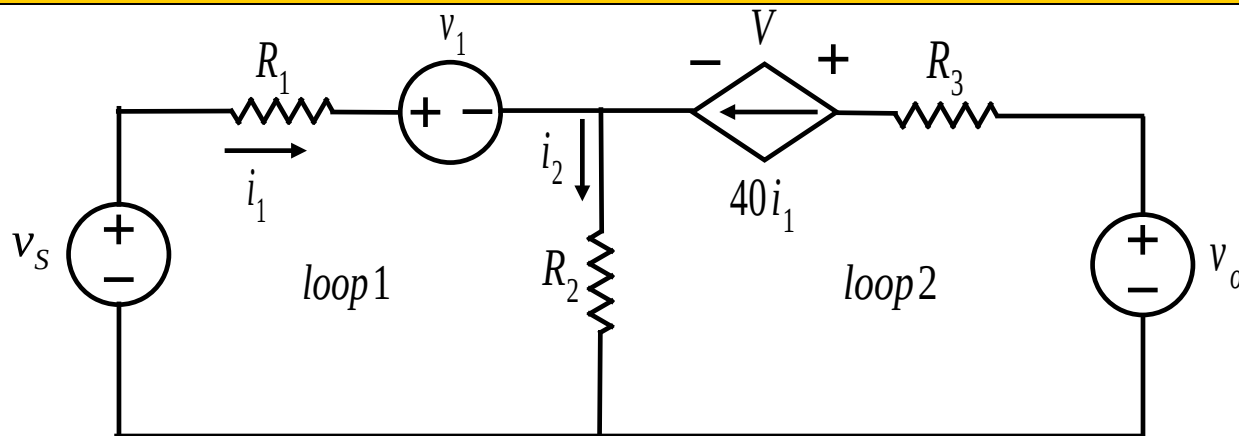

Given

$$v_s = 3(V)$$

$$v_1 = 0.5(V)$$

$$v_o = 10(V)$$

$$R_1 = 29.5(k\Omega)$$

$$R_2 = 500(\Omega)$$

$$R_3 = 2.4(k\Omega)$$

Loop 2

$$v_o = 40i_1R_3 + V + i_2R_2 \quad (3)$$

$$v_o = i_1(40R_3 + 41R_2) + V \quad \left. \begin{array}{l} \text{Substitute } i_2 = 41i_1 \text{ into } (3) \end{array} \right\}$$

$$V = v_o - i_1(40R_3 + 41R_2) \quad \left. \begin{array}{l} \text{Solve for } V \end{array} \right\}$$

$$= 10 - 50 \times 10^{-6} (40[2.4K] + 41[500])$$

$$= 10 - 5.825$$


$$V = 4.175(V)$$

Sign
Convention

$$p > 0$$

$$p_{\diamond} = +V(40i_1) = 4.175(40)(50 \times 10^{-6}) = +8.35(mW) \quad \{absorbed\}$$

Example: Find Power of v_s

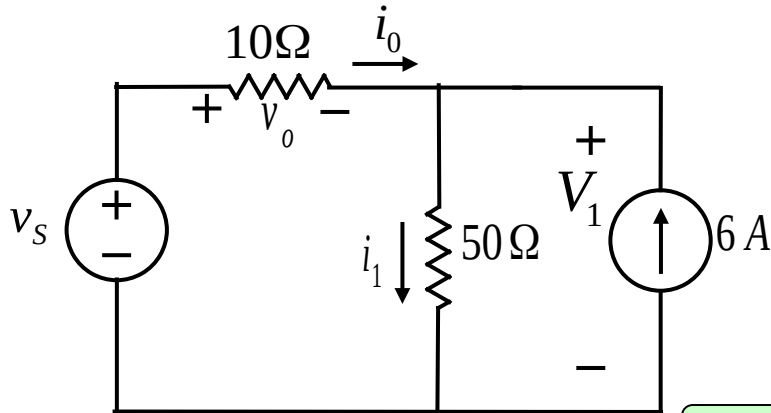

$$v_s = 120(V) \quad \left. \vphantom{v_s} \right\} \text{ Given}$$

$$\text{KCL} \left\{ i_1 = i_0 + 6 \right.$$

$$\text{KVL} \left\{ v_s = 10i_0 + 50i_1 \right.$$

Solve for i_1
and i_0

Result

$$i_1 = 3(A)$$
$$i_0 = -3(A)$$

$$p_{120} = -120i_0 = -120(-3(A))$$


$$p_{120} = +360(W)$$

$$p > 0$$

Sign
Convention

Power is Absorbed by the 120(V) source.

Same Example: Find Power of 6A source

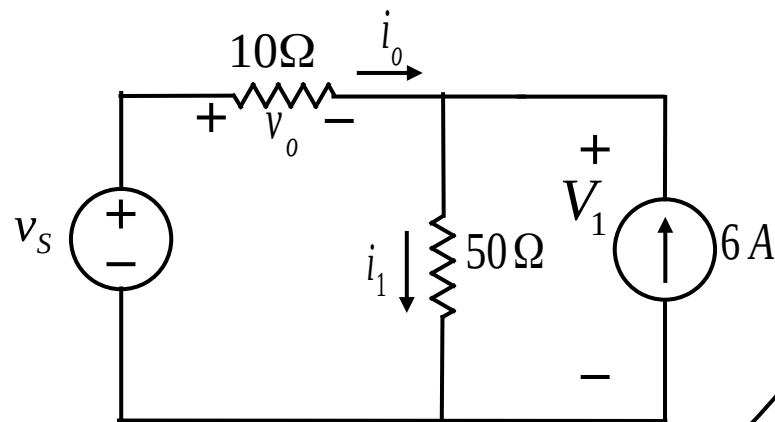

Sign
Convention

$$p_6 = -V_1 \cdot 6$$

$$V_1 = +i_1 \cdot 50$$

$$V_1 = +150$$

$$p_6 = -900(W)$$

Ohm's
Law

From the
previous slide

$$i_1 = 3(A)$$

$$i_o = -3(A)$$

$$p_{120} = +360(W)$$


$$p < 0$$

Power is delivered
by 6A source

Conclusion:

In original circuit, the 6A source
“overwhelms” the 120V source, and
actually supplies power to it!

Note on Voltages and Currents

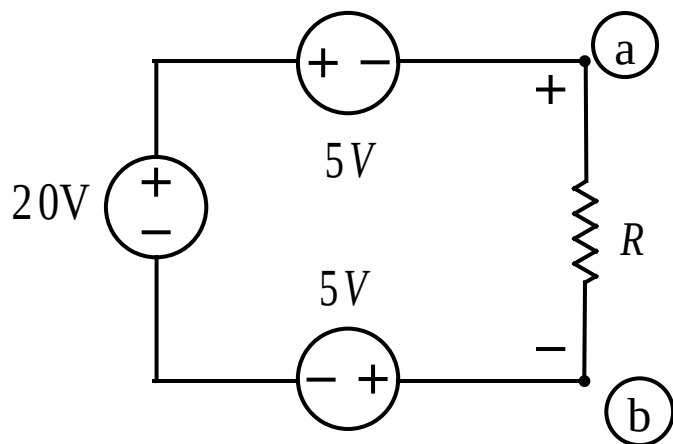


Voltage Across R

$$V_{ab} = -5(V) + 20(V) - 5(V) = 10(V)$$

Voltages in series add

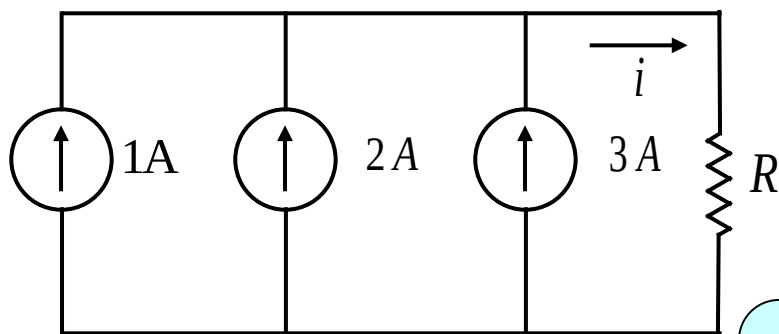“k” Voltages in parallel must be the same




Current Through R

$$i = 1(A) + 2(A) + 3(A) = 6(A)$$

Currents in parallel add

“k” Currents in series must be the same

Example: Find i_g and V_g

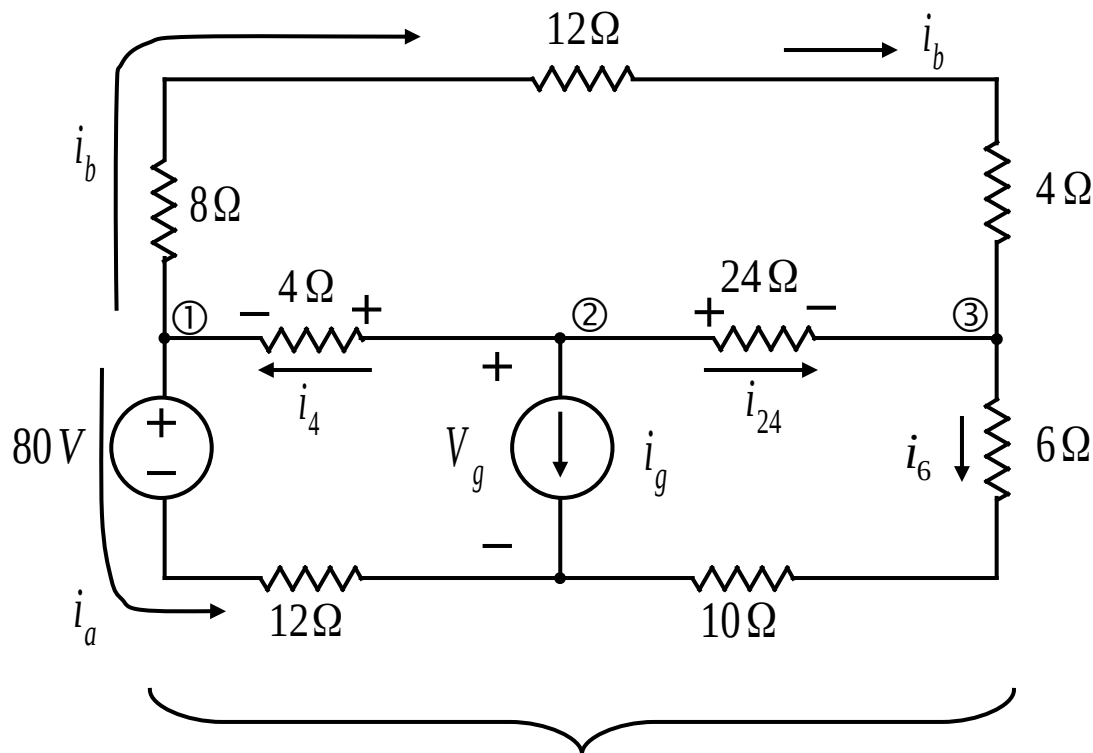

Given

$$i_a = 4 \text{ (A)}$$

$$i_b = 2 \text{ (A)}$$


Currents have been defined
in the circuit

Example: Find i_g (Contd.)

Given

$$i_a = 4(A)$$

$$i_b = 2(A)$$

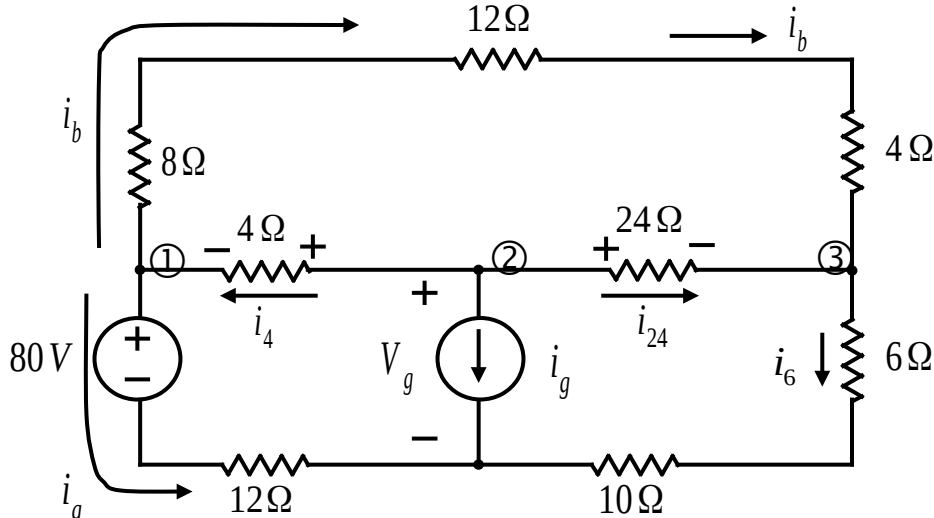

a) KCL at node ① $i_4 = i_a + i_b = 4 + 2 \Rightarrow i_4 = 6(A)$

b) KVL around upper loop

$$i_b(8 + 12 + 4) - 24i_{24} + 4i_4 = 0$$

$$i_{24} = \frac{24i_b + 4i_4}{24} = \frac{24(2) + 4(6)}{24} = \frac{72}{24}$$

$$i_{24} = 3(A)$$

Substitute for i_b and i_4


Solve
for i_{24}

Example: Find i_g (Contd.)

$$i_b = 2(A)$$

$$i_4 = 6(A)$$

$$i_{24} = 3(A)$$

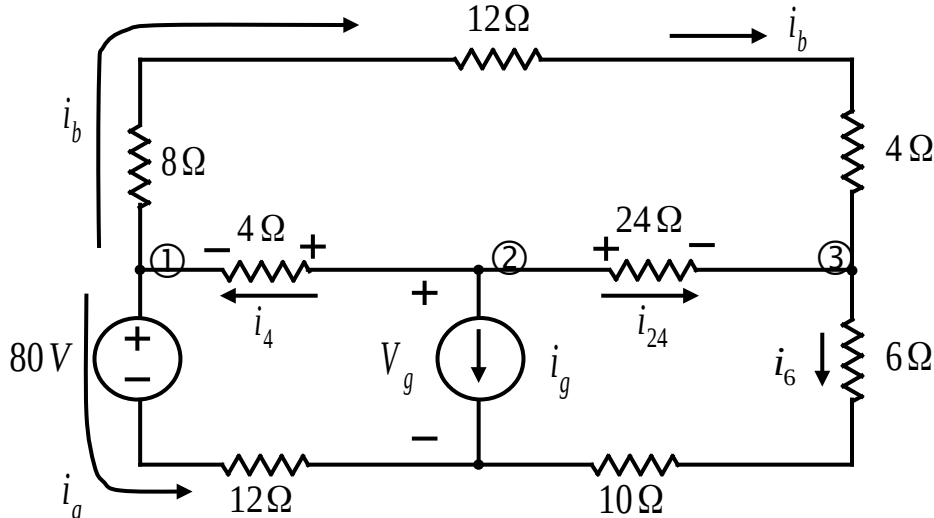

c) KCL at node ②

$$i_4 + i_{24} + i_g = 0$$

$$i_g = -i_4 - i_{24} = -6 - 3 \quad \left. \vphantom{i_g = -i_4 - i_{24} = -6 - 3} \right\} \text{Solve for } i_g$$

$$i_g = -9(A) \quad i_g \text{ “really” flows “up”}$$

d) KCL at node ③

$$i_b + i_{24} = i_6; \quad 2 + 3 = i_6 = 5(A) \quad \left. \vphantom{i_b + i_{24} = i_6; \quad 2 + 3 = i_6 = 5(A)} \right\} \text{Solve for } i_6$$

we know all currents now

Example: Find V_g (Contd.)

$$i_a = 4(A)$$

$$i_4 = 6(A)$$

e) KVL

$$V_g = 4i_4 + 80 + 12i_a \quad \text{Bottom LHS}$$

$$= 4(6) + 80 + 12(4) \quad \text{Substitute Currents}$$

$$= 24 + 80 + 48 = 152(V)$$

Sign
Convention

f) $p_{80V} = V \cdot i_a = 80(4) = 320(W)$

$$p > 0$$

80V source “absorbs” power
so do all resistors

