

Problems

8.1 Constant-Current Sources

1. Find the voltage V_S for the circuit shown in Figure 8–64.
2. Find the voltage V_S for the circuit shown in Figure 8–65.

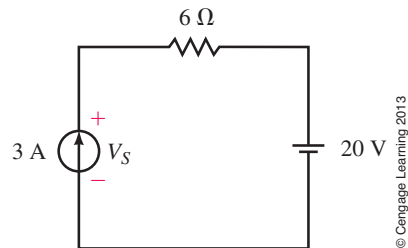


FIGURE 8–64

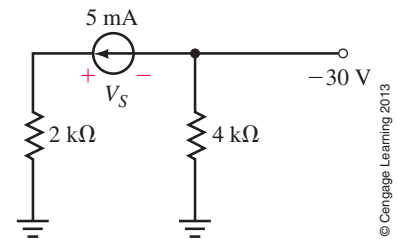


FIGURE 8–65

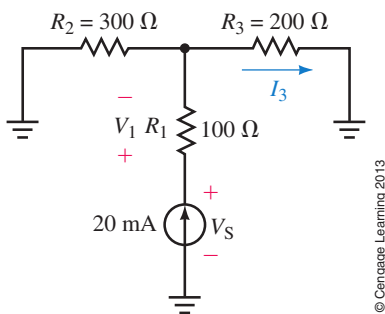


FIGURE 8–66

3. Refer to the circuit of Figure 8–66:
 - a. Find the current I_3 .
 - b. Determine the voltages V_S and V_1 .
4. Consider the circuit of Figure 8–67:
 - a. Calculate the voltages V_2 and V_S .
 - b. Find the currents I and I_3 .

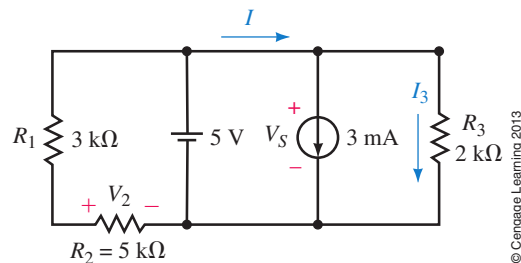


FIGURE 8–67

5. For the circuit of Figure 8–68, find the currents I_1 and I_2 .
6. Refer to the circuit of Figure 8–69:
 - a. Find the voltages V_S and V_2 .
 - b. Determine the current I_4 .

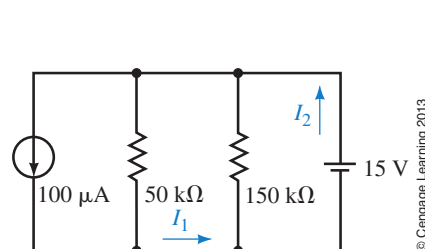


FIGURE 8–68

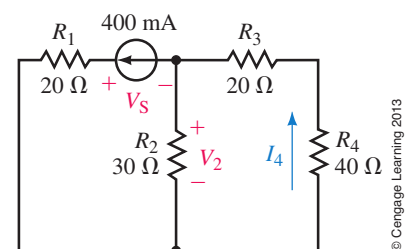


FIGURE 8–69

7. Verify that the power supplied by the sources is equal to the summation of the powers dissipated by the resistors in the circuit of Figure 8–68.
8. Verify that the power supplied by the source in the circuit of Figure 8–69 is equal to the summation of the powers dissipated by the resistors.

8.2 Source Conversions

9. Convert each of the voltage sources of Figure 8–70 into its equivalent current source.
10. Convert each of the current sources of Figure 8–71 into its equivalent voltage source.

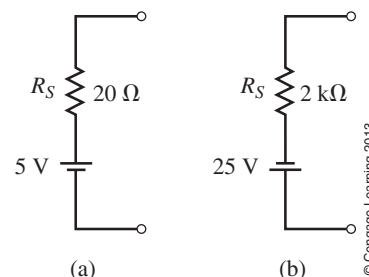


FIGURE 8–70

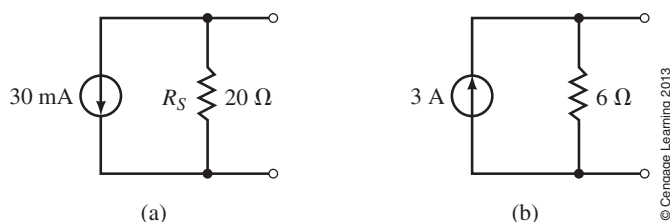


FIGURE 8–71

11. Refer to the circuit of Figure 8–72:
 - a. Solve for the current through the load resistor using the current divider rule.
 - b. Convert the current source into its equivalent voltage source and again determine the current through the load.
12. Find V_{ab} and I_2 for the network of Figure 8–73.

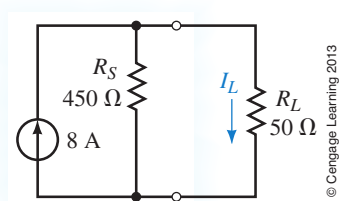


FIGURE 8–72

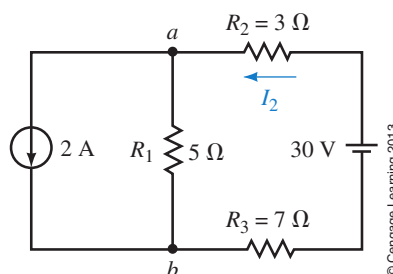


FIGURE 8–73

13. Refer to the circuit of Figure 8–74:
 - a. Convert the current source and the 330-Ω resistor into an equivalent voltage source.
 - b. Solve for the current I through R_L .
 - c. Determine the voltage V_{ab} .

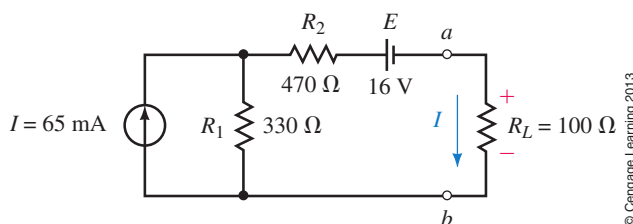


FIGURE 8–74

14. Refer to the circuit of Figure 8–75:
- Convert the voltage source and the $36\text{-}\Omega$ resistor into an equivalent current source.
 - Solve for the current I through R_L .
 - Determine the voltage V_{ab} .

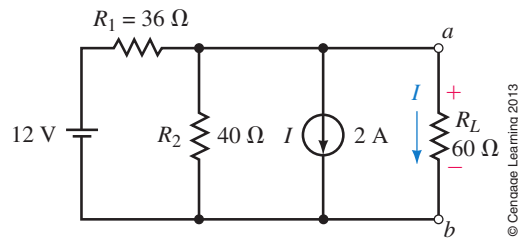


FIGURE 8–75

8.3 Current Sources in Parallel and Series

15. Find the voltage V_2 and the current I_1 for the circuit of Figure 8–76.

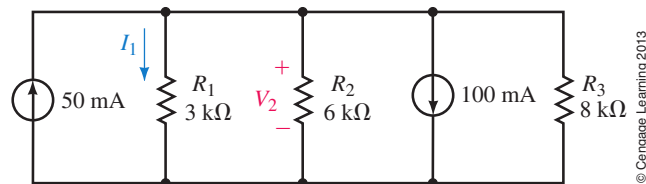


FIGURE 8–76

- Convert the voltage sources of Figure 8–77 into current sources and solve for the current I_1 and the voltage V_{ab} .
- For the circuit of Figure 8–78, convert the current source and the $2.4\text{-k}\Omega$ resistor into a voltage source and find the voltage V_{ab} and the current I_3 .
- For the circuit of Figure 8–78, convert the voltage source and the series resistors into an equivalent current source.
 - Determine the current I_2 .
 - Solve for the voltage V_{ab} .

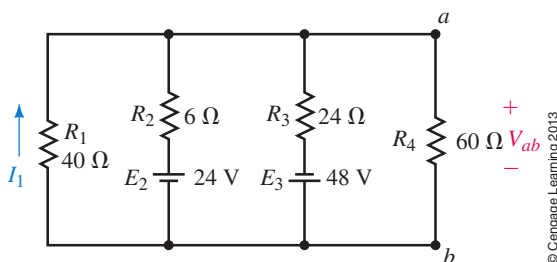


FIGURE 8–77

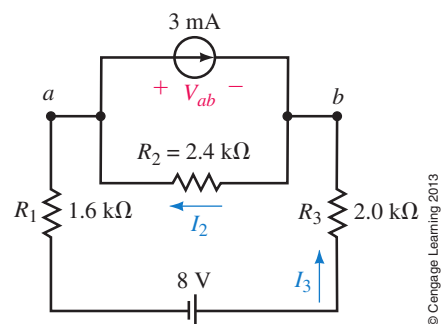


FIGURE 8–78

8.4 Branch-Current Analysis

19. Write the branch-current equations for the circuit shown in Figure 8–79 and solve for the branch currents using determinants.
20. Refer to the circuit of Figure 8–80:
 - a. Solve for the current I_1 using branch-current analysis.
 - b. Determine the voltage V_{ab} .

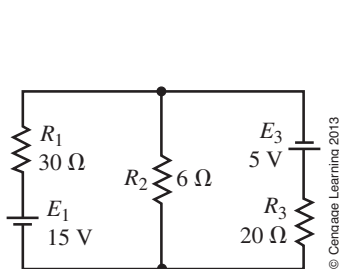


FIGURE 8–79

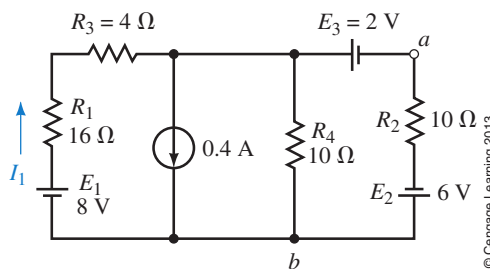


FIGURE 8–80

21. Write the branch-current equations for the circuit shown in Figure 8–81 and solve for the current I_2 .

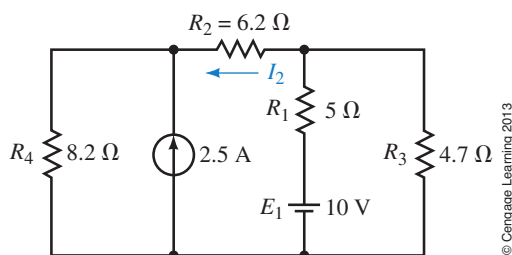


FIGURE 8–81

22. Refer to the circuit shown in Figure 8–82:
 - a. Write the branch-current equations.
 - b. Solve for the currents I_1 and I_2 .
 - c. Determine the voltage V_{ab} .
23. Refer to the circuit shown in Figure 8–83:
 - a. Write the branch-current equations.
 - b. Solve for the current I_2 .
 - c. Determine the voltage V_{ab} .

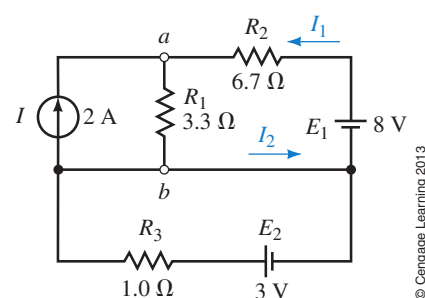


FIGURE 8–82

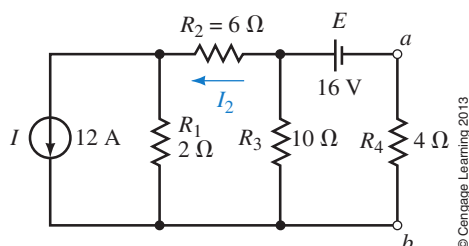


FIGURE 8–83

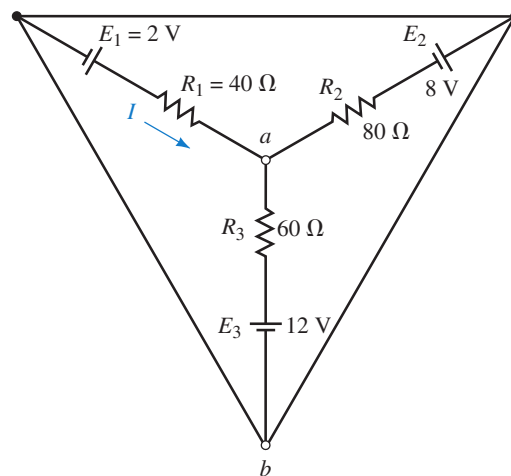


FIGURE 8-84

24. Refer to the circuit shown in Figure 8–84:
 - a. Write the branch-current equations.
 - b. Solve for the current I .
 - c. Determine the voltage V_{ab} .

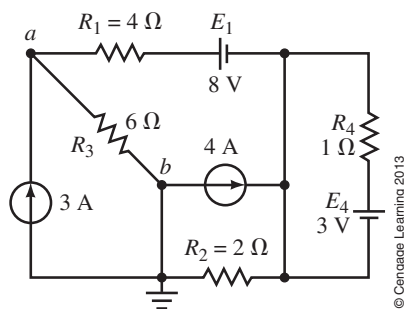


FIGURE 8-85

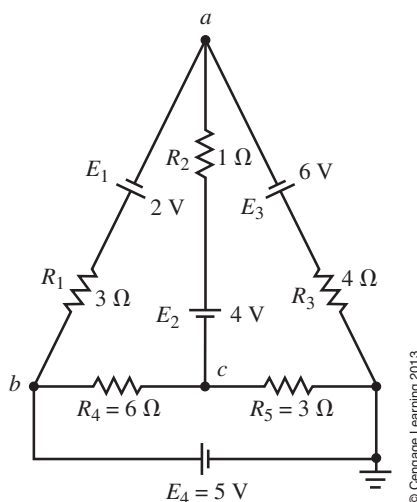


FIGURE 8-86

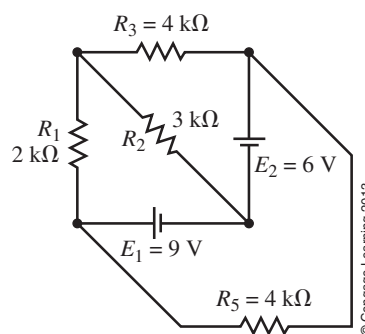


FIGURE 8-87

25. Write the mesh equations for the circuit shown in Figure 8–79 and solve for the loop currents.
26. Use mesh analysis for the circuit of Figure 8–80 to solve for the current I_1 .
27. Use mesh analysis to solve for the current I_2 in the circuit of Figure 8–81.
28. Use mesh analysis to solve for the loop currents in the circuit of Figure 8–83. Use your results to determine I_2 and V_{ab} .
29. Use mesh analysis to solve for the loop currents in the circuit of Figure 8–84. Use your results to determine I and V_{ab} .
30. Using mesh analysis, determine the current through the 6-Ω resistor in the circuit of Figure 8–85.
31. Write the mesh equations for the network in Figure 8–86. Solve for the loop currents using determinants.
32. Repeat Problem 31 for the network in Figure 8–87.

8.6 Nodal Analysis

33. Write the nodal equations for the circuit of Figure 8–88 and solve for the nodal voltages.
34. Write the nodal equations for the circuit of Figure 8–89 and determine the voltage V_{ab} .
35. Repeat Problem 33 for the circuit of Figure 8–90.

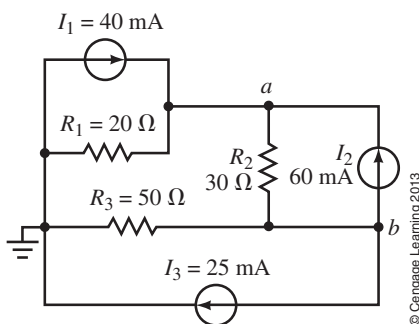


FIGURE 8–89

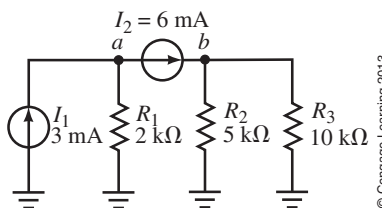


FIGURE 8–90

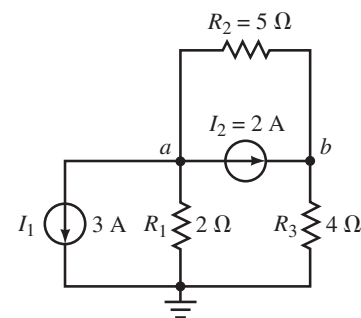


FIGURE 8–88

36. Repeat Problem 34 for the circuit of Figure 8–91.
37. Write the nodal equations for the circuit of Figure 8–86 and solve for V_6 .
38. Write the nodal equations for the circuit of Figure 8–85 and solve for V_6 .

8.7 Delta-Wye (Pi-Tee) Conversion

39. Convert each of the Δ networks of Figure 8–92 into its equivalent Y configuration.
40. Convert each of the Δ networks of Figure 8–93 into its equivalent Y configuration.

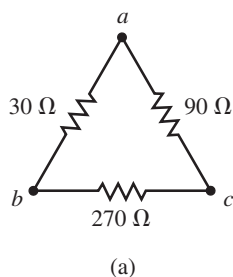


FIGURE 8–92


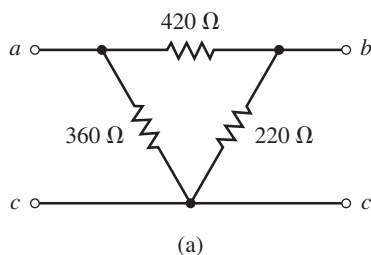
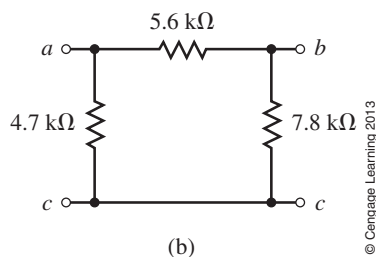


FIGURE 8–93

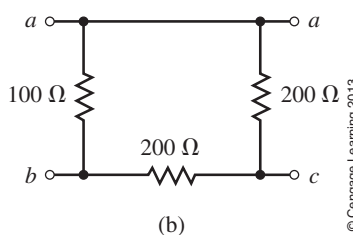

41. Convert each of the Y networks of Figure 8–94 into its equivalent Δ configuration.

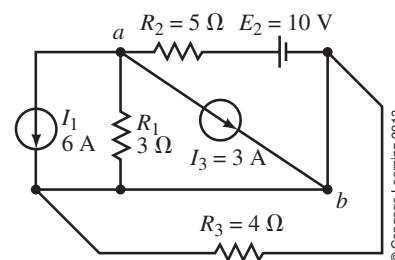


FIGURE 8–91

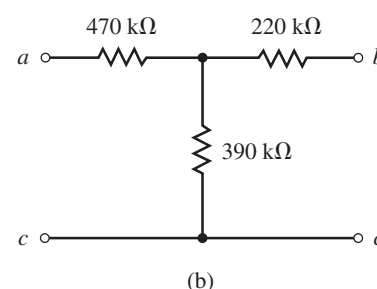
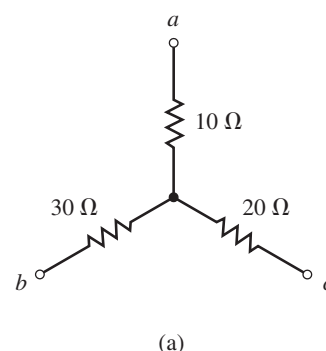


FIGURE 8–94

42. Convert each of the Y networks of Figure 8–95 into its equivalent Δ configuration.

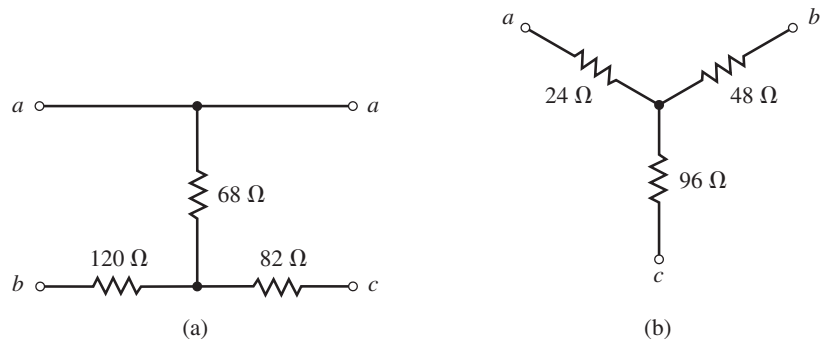


FIGURE 8–95

43. Using Δ -Y or Y- Δ conversion, find the current I for the circuit of Figure 8–96.
44. Using Δ -Y or Y- Δ conversion, find the current I and the voltage V_{ab} for the circuit of Figure 8–97.

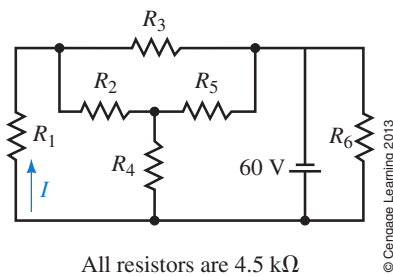


FIGURE 8–96

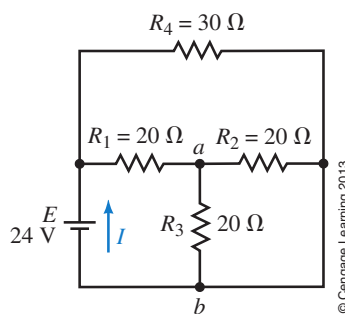


FIGURE 8–97

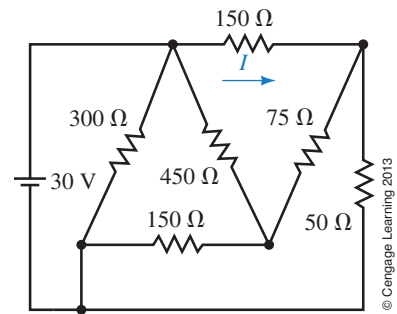


FIGURE 8–98

45. Repeat Problem 43 for the circuit of Figure 8–98.
46. Repeat Problem 44 for the circuit of Figure 8–99.

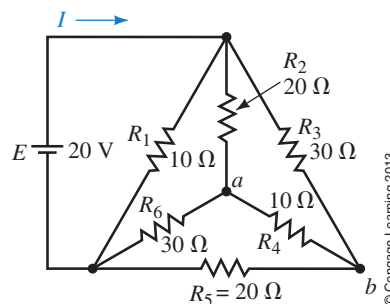


FIGURE 8–99

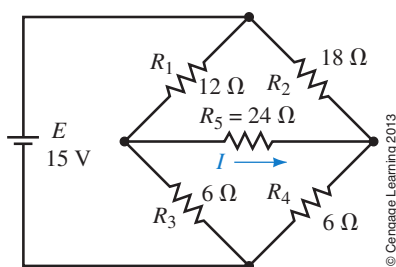


FIGURE 8–100

8.8 Bridge Networks

47. Refer to the bridge circuit of Figure 8–100:
- Is the bridge balanced? Explain.
 - Write the mesh equations.
 - Calculate the current through R_5 .
 - Determine the voltage across R_5 .

48. Consider the bridge circuit of Figure 8–101:
- Is the bridge balanced? Explain.
 - Write the mesh equations.
 - Determine the current through R_5 .
 - Calculate the voltage across R_5 .
49. Given the bridge circuit of Figure 8–102, find the current through each resistor.
50. Refer to the bridge circuit of Figure 8–103:
- Determine the value of resistance R_x such that the bridge is balanced.
 - Calculate the current through R_5 when $R_x = 0\ \Omega$ and when $R_x = 10\ \text{k}\Omega$.

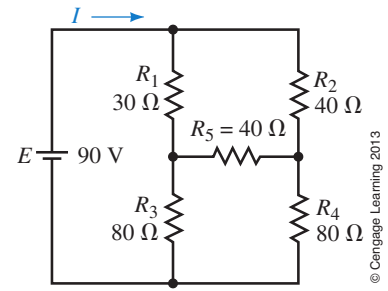


FIGURE 8-101

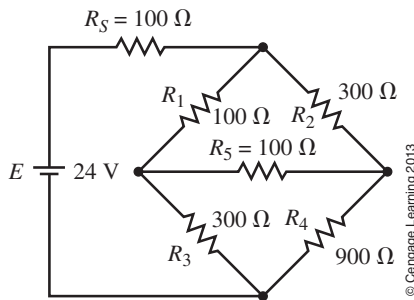


FIGURE 8-102

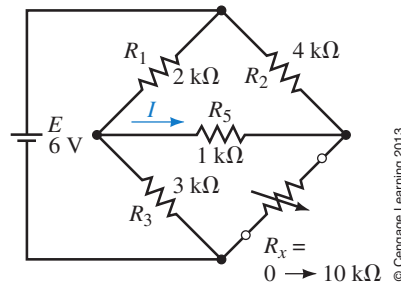


FIGURE 8-103

8.9 Circuit Analysis Using Computers

- Use Multisim to solve for the currents through all resistors of the circuit shown in Figure 8–86.
- Use Multisim to solve for the voltage across the 5-k Ω resistor in the circuit of Figure 8–87.
- Use PSpice to solve for the currents through all resistors in the circuit of Figure 8–96.
- Use PSpice to solve for the currents through all resistors in the circuit of Figure 8–97.



ANSWERS TO IN-PROCESS LEARNING CHECKS

IN-PROCESS LEARNING CHECK 1

- A voltage source E in series with a resistor R is equivalent to a current source having an ideal current source $I = E/R$ in parallel with the same resistance, R .
- Current sources are never connected in series.

IN-PROCESS LEARNING CHECK 2

- Voltage is zero.
- Current is zero.
- R_5 can be replaced with either a short circuit or an open circuit.