

1. For the Circuit given below, Find the values of v_1 , v_2 , v_{ab} , v_{bc} , and v_{ca} .

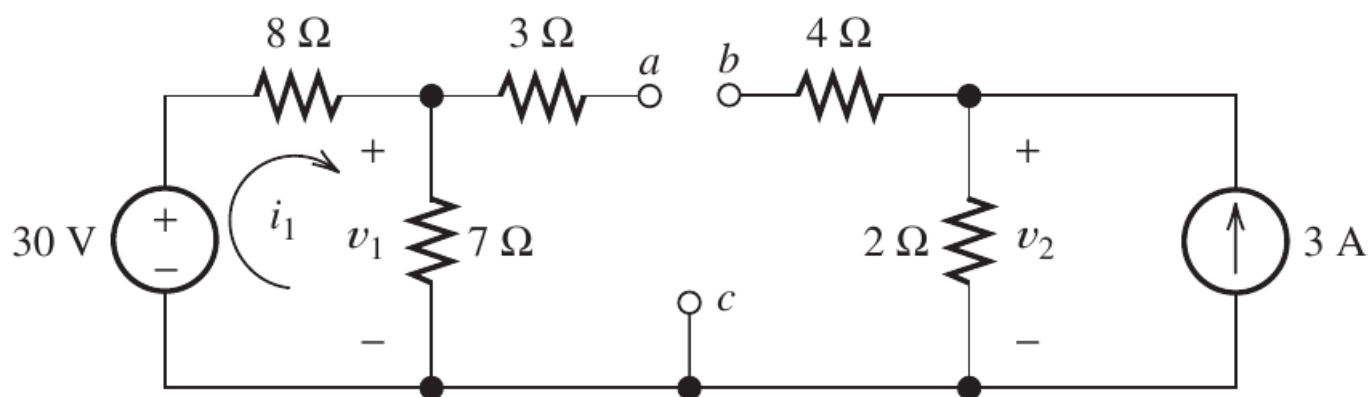


Figure 1

2. Write equations and solve for the node voltages shown in Figure 2 . Then find the value of i_1

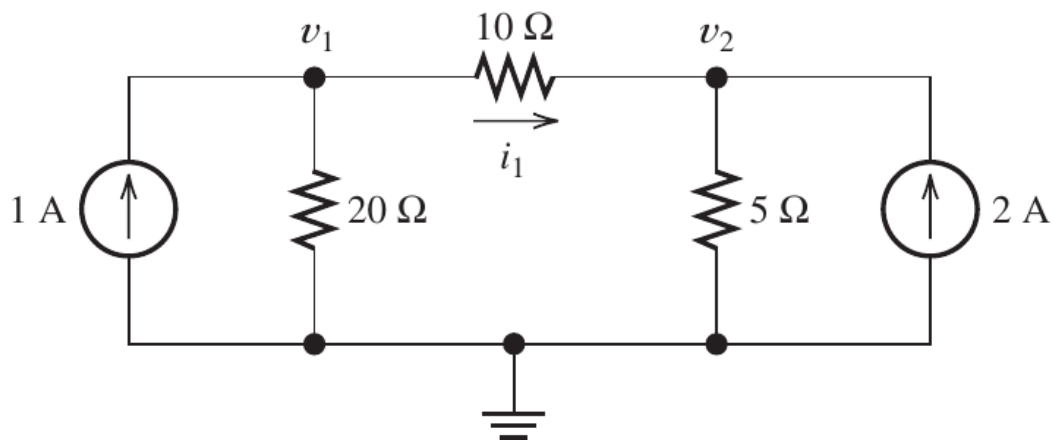


Figure 2

3. In the circuit of Figure 3, calculate V_1 , and determine the Thevenin Voltage with respect to the terminals a & b.

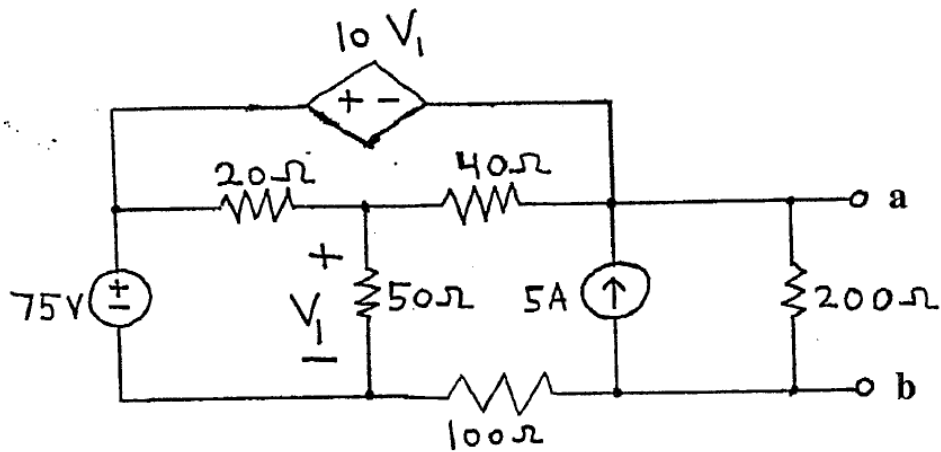


Figure 3

4. Solve for the power delivered to the 8 ohm resistor and solve for the node voltages for the circuit given in Figure 4

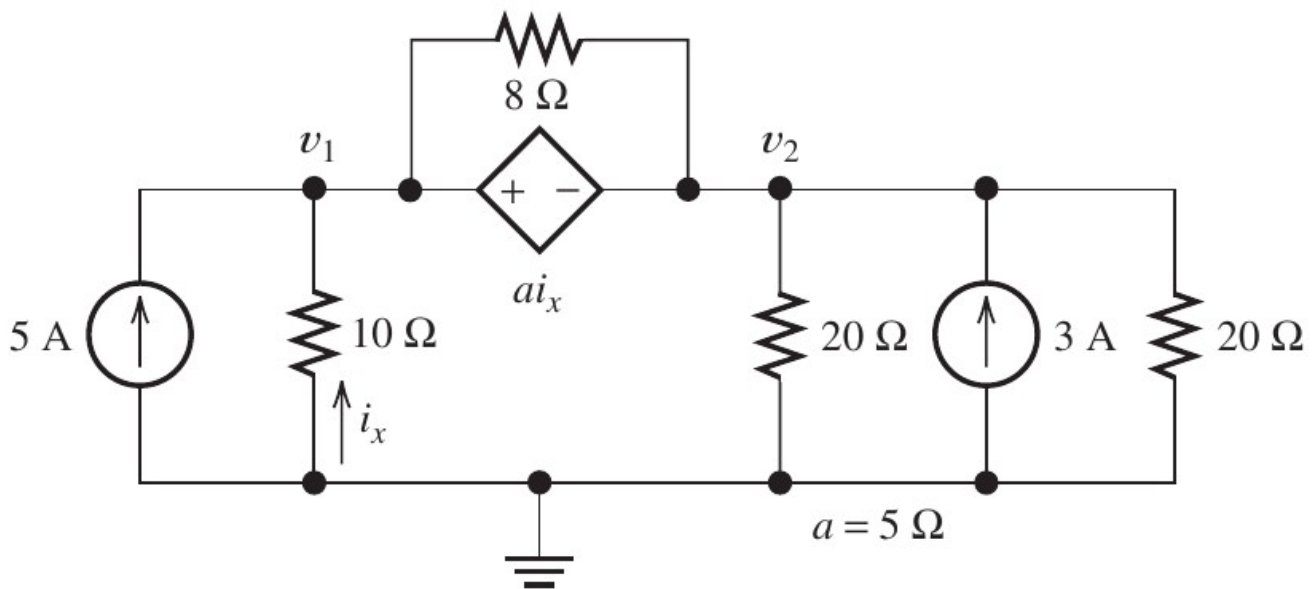


Figure 4

5. Solve for

i) the mesh currents i_1 , i_2 , i_3 and i_4 (using mesh analysis)

ii) node voltages v_1 , v_2 , v_3 , and v_4 (using node analysis)

for the circuit given in Figure 5 .

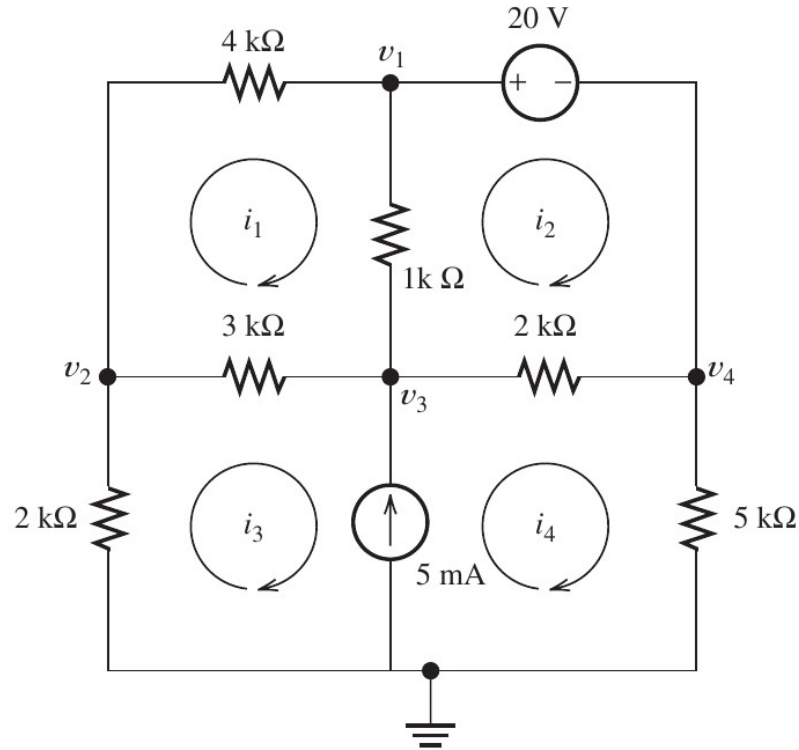


Figure 5

6. Solve for the power delivered by the voltage source for the circuit given below using the mesh – current method.

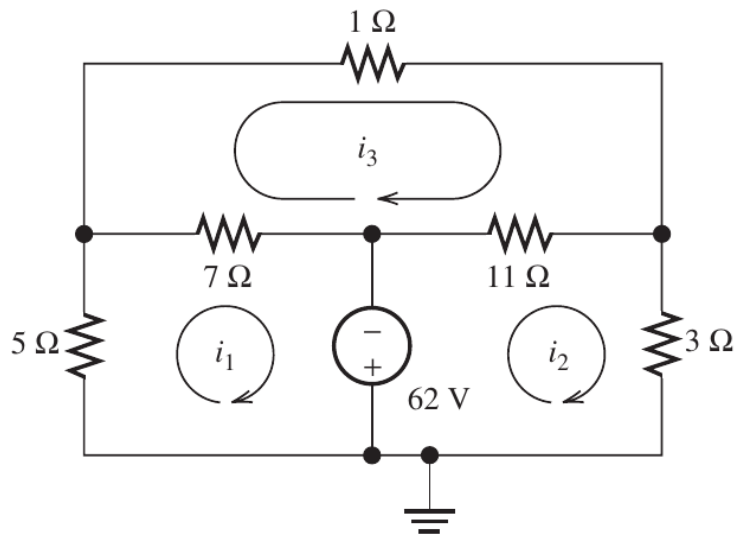


Figure 6